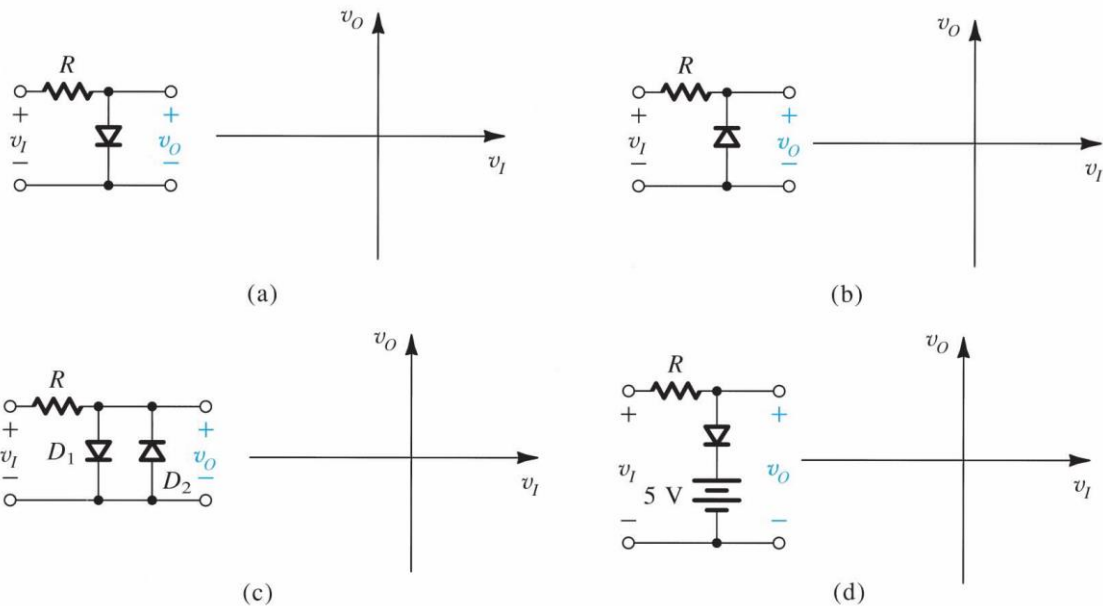
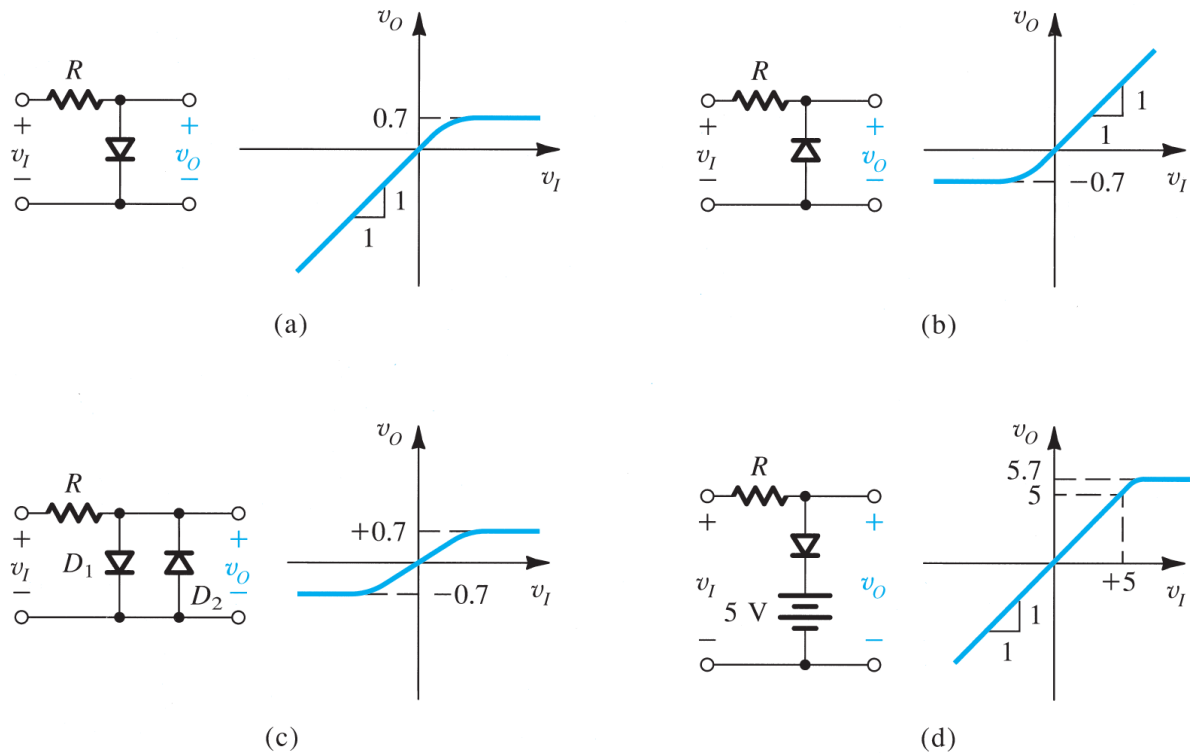

EHB222E INTRODUCTION TO ELECTRONICS (10745, 10747, 10748, 11201)**MT1 Exam 16 November 2021 🕒 18:00-19:30****Bora DÖKEN, Bülent YAĞCI, İbrahim ÇATALKAYA, İnci ÇİLESİZ**

- Assume you are to create p⁺n


transistor using n- and p-typed doped silicon with the following doping concentrations, $2 \cdot 10^{18} / \text{cm}^3$, $10^{14} / \text{cm}^3$, and $4 \cdot 10^{16} / \text{cm}^3$, for emitter, base and collector regions, respectively. You also know $L_n = 8 \mu\text{m}$, $L_p = 4 \mu\text{m}$, $\mu_n = 1500 \text{ cm}^2/\text{Vs}$, $\mu_p = 500 \text{ cm}^2/\text{Vs}$, $n_i = 1,5 \cdot 10^{10} / \text{cm}^3$, $q = 1,602 \cdot 10^{-19} \text{ C}$, $\epsilon_r = 12$, $\epsilon_o = 8,85 \cdot 10^{-12} \text{ F/m}$, $V_T = 25 \text{ mV}$. Calculate (26 points total)
 - barrier potentials for EB and BC junctions. (2x 4 points) ($V_{B1} = 688 \text{ mV}$, $V_{B2} = 590 \text{ mV}$)
 - saturation current for a junction area of $0,15 \text{ mm}^2$ assuming $h_{FE} = \beta$ is very large. (6 points) ($16,9 \text{ pA}$)
 - depletion zone widths of both junctions in unbiased state. (2x 4 points) state ($w_{EB} = 3,02 \mu\text{m}$, $w_{BC} = 2,80 \mu\text{m}$)
 - What is the minimum V_{CE} for operation in active mode? (4 points) ($V_{CEmin} = 688 \text{ mV}$)
- v_I is a sinusoidal wave source. Sketch the $v_o - v_I$ diagrams by using modified ideal diode model ($V_D=0.7\text{V}$: voltage drop on a diode) (4x 6 points)

**GOOD LUCK EVERYONE**


Solution:



3. Measurement on the circuit of figure produce labelled voltage as indicated. Find the value of I_C , I_B , I_E , V_E and β for transistor. ($|V_{BE}| = 0.7$ V) (5x 5 points)

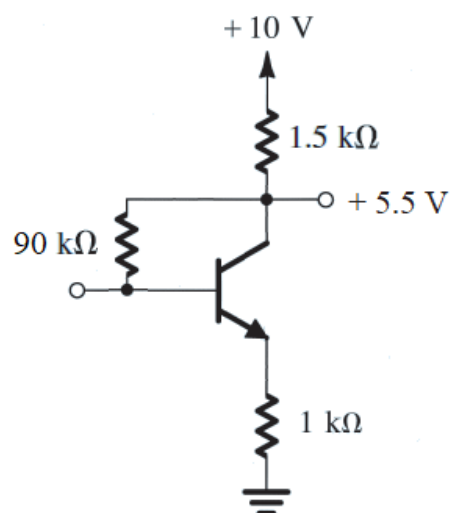

Solution:

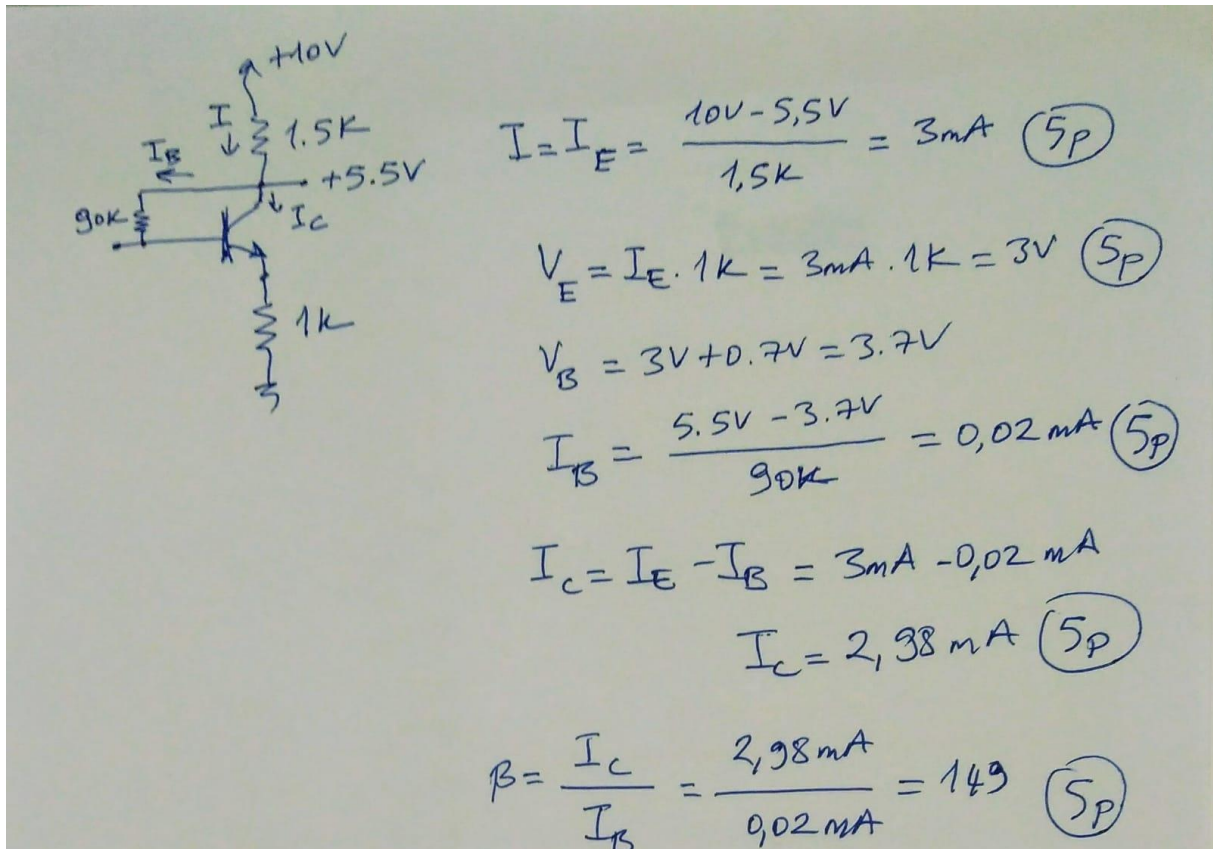

The handwritten solution shows a circuit diagram of a BJT in common-emitter configuration. The base is biased with a voltage divider consisting of a 1.5k resistor connected to +10V and a 90k resistor connected to +5.5V. The emitter is connected to ground through a 1k resistor. The collector is connected to +10V through a 1.5k resistor. The calculations are as follows:

$$I = I_E = \frac{10V - 5.5V}{1.5k} = 3mA \quad (5P)$$

$$V_E = I_E \cdot 1k = 3mA \cdot 1k = 3V \quad (5P)$$

$$V_B = 3V + 0.7V = 3.7V$$

$$I_B = \frac{5.5V - 3.7V}{90k} = 0.02mA \quad (5P)$$


$$I_C = I_E - I_B = 3mA - 0.02mA$$

$$I_C = 2.98mA \quad (5P)$$

$$\beta = \frac{I_C}{I_B} = \frac{2.98mA}{0.02mA} = 149 \quad (5P)$$

4. In the figure below, the resistor values are given as the follows:

$R_1 = 36\text{ k}\Omega$, $R_2 = 160\text{ k}\Omega$, $R_3 = 9.2\text{ k}\Omega$, $R_4 = 39\text{ k}\Omega$, $R_5 = 5\text{ k}\Omega$. $h_{FE} = \beta = 250$ and $|V_{BE}| = 0.6V$ for both BJT's. Please calculate collector currents, I_{C1} and I_{C2} ? (25 points total)

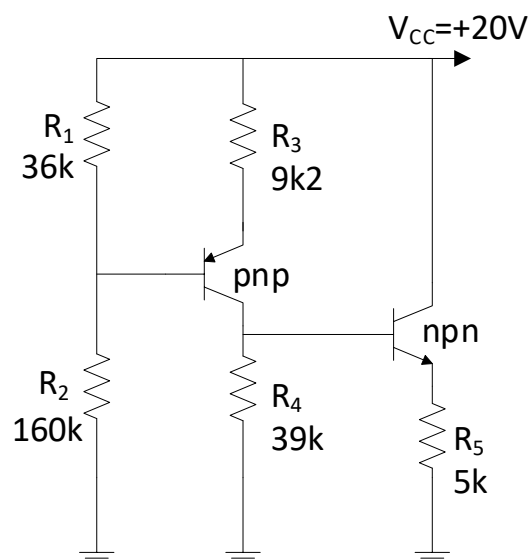

Solution:

$V_{CC} = 20V$

$h_{FE} = \beta = 250$
 $|V_{BE}| = 0.6V$
 $I_{C1} = ? \quad I_{C2} = ?$

Sol.ⁿ

$R_{th} = R_1 \parallel R_2 = 29.38k$
 $V_{th} = \frac{R_2}{R_1 + R_2} V_{CC} = 16.32V$

$V_{CC} - I_{E1}R_3 - |V_{BE}| - I_{B1}R_{th} = V_{th}$
 $I_{E1} = (\beta + 1)I_{B1}$
 $\Rightarrow 20V - I_{B1} \times 251 \times 9.2k - 0.6V - I_{B1} \times 29.38k = 16.32V$
 $I_{B1} = 1.31 \mu A$
 $I_{C1} = \beta I_{B1} = 0.329 mA$

$\Rightarrow V_{C1} = (I_{C1} - I_{B2})R_4$
 $V_{C1} - V_{BE2} - I_{E2}R_5 = 0$
 $V_{C1} = V_{BE} + I_{E2}R_5$
 $(I_{C1} - I_{B2})R_4 = V_{BE} + I_{E2}R_5$
 $\Rightarrow I_{B2} = 9.46 \mu A$
 $I_{C2} = \beta I_{B2} = 2.36 mA$