

$$i_1 + i_2 + I_{VS} = 0 \quad (1)$$


$$i_2 + i_3 - i_4 = 0 \quad (2)$$

$$i_3 + I_{RU} - i_1 = 0 \quad (3)$$

$$V_1 = V_S \quad \text{ext(4)}$$

$$V_3 = r \cdot i_1 \quad \text{ext(5)}$$

$$i_4 = \frac{V_1 - V_3}{R_1}$$

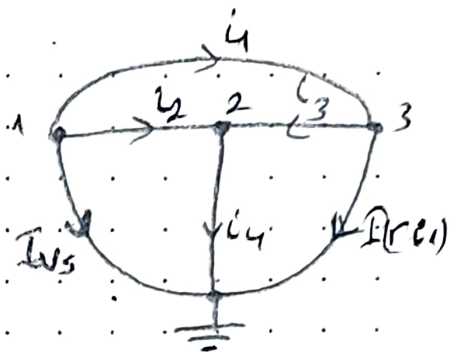


$$\frac{V_1 - V_3}{R_1} + \frac{V_1 - V_2}{R_2} + I_{VS} = 0$$

$$\frac{V_1 - V_2}{R_2} + \frac{V_3 - V_2}{R_3} - \frac{V_2}{R_4} = 0$$

$$\frac{V_3 - V_2}{R_3} - \frac{V_1 - V_3}{R_1} + I_{RU} = 0$$

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} & -\frac{1}{R_1} & 1 & 0 \\ \frac{1}{R_2} & -(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}) & \frac{1}{R_3} & 0 & 0 \\ -\frac{1}{R_1} & -\frac{1}{R_3} & \frac{1}{R_1} + \frac{1}{R_3} & 0 & 1 \\ 1 & 0 & 0 & 0 & 0 \\ \frac{1}{R_1} & 0 & -(\frac{1}{R_1} + 1) & 0 & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ I_{VS} \\ I_{RU} \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ V_S \\ 0 \end{bmatrix}$$

Sena ERS04  
040200434  
Sena

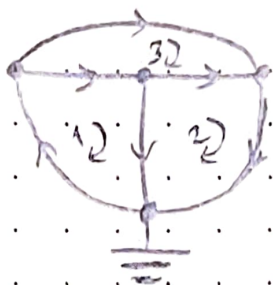

$$V_2 + V_4 + V_{I5} = 0$$

$$V_3 + V_{gvi} - V_4 = 0$$

$$V_1 - V_3 - V_2 = 0$$

$$I_{m2} = g V_1 = g R_1 I_{m3}$$

$$I_{m1} = I_5$$

$$R_2 (I_{m1} - I_{m3}) + R_4 (I_{m1} - I_{m2}) + V_{I5} = 0$$

$$R_3 (I_{m2} - I_{m3}) + V_{gvi} - R_4 (I_{m2} - I_{m1}) = 0$$

$$R_1 I_{m3} - R_3 (I_{m3} - I_{m2}) - R_2 (I_{m3} - I_{m1}) = 0$$

$$(R_2 + R_4) I_{m1} - R_4 I_{m2} - R_2 I_{m3} + V_{I5} = 0$$

$$R_4 I_{m1} + (R_3 - R_4) I_{m2} - R_3 I_{m3} + V_{gvi} = 0$$



$$R_2 I_{m1} + R_3 I_{m2} + (R_1 - R_2 - R_3) I_{m3} = 0$$


$$I_{m2} - g R_1 I_{m3} = 0$$

$$I_{m1} = I_5$$

$$\begin{bmatrix} R_2 + R_4 & -R_4 & -R_2 & 1 & 0 \\ R_4 & R_3 - R_4 & -R_3 & 0 & 1 \\ R_2 & R_3 & (R_1 - R_2 - R_3) & 0 & 0 \\ 0 & 1 & -g R_1 & 0 & 0 \\ 1 & 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_{m1} \\ I_{m2} \\ I_{m3} \\ V_{I5} \\ V_{gvi} \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ I_5 \end{bmatrix}$$

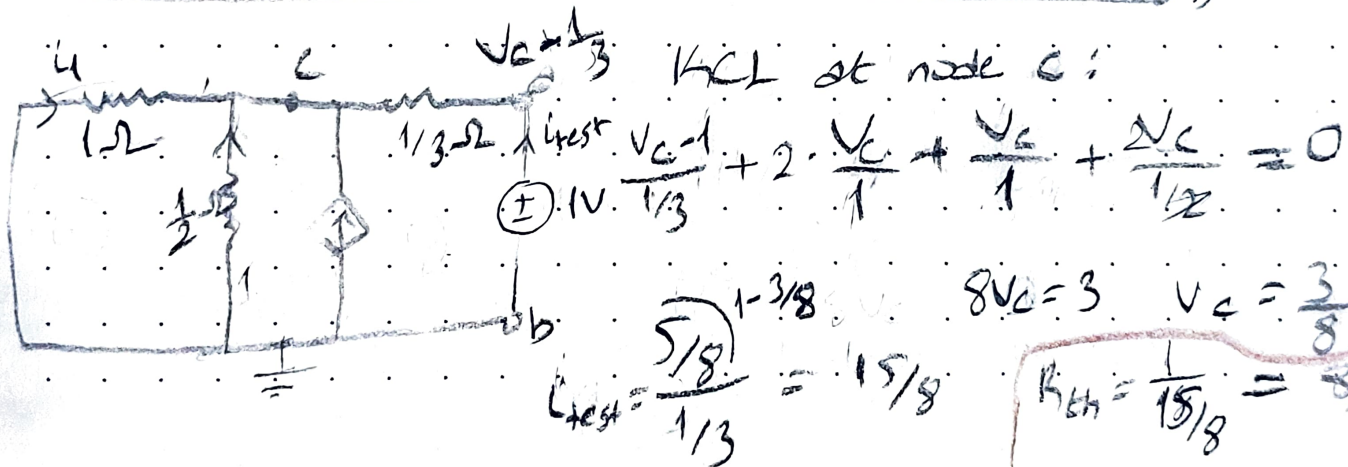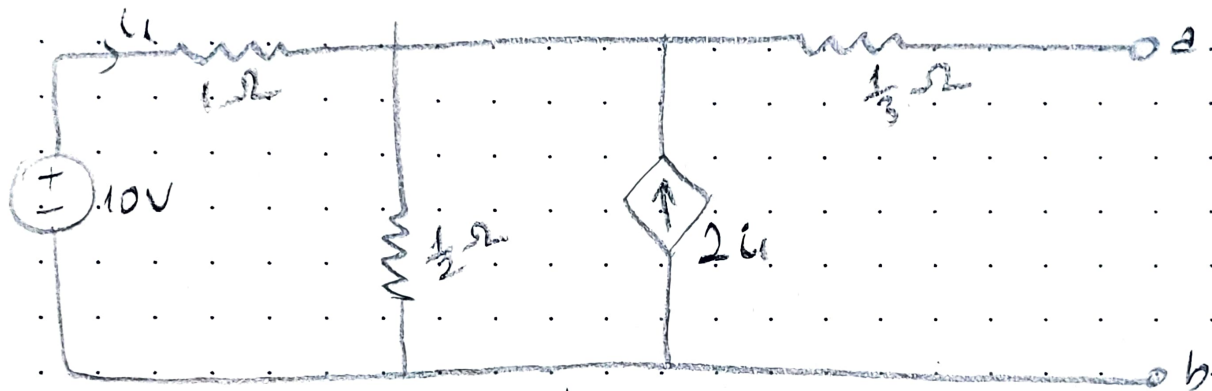Find Thévenin equivalent of the 2-terminal a-b.



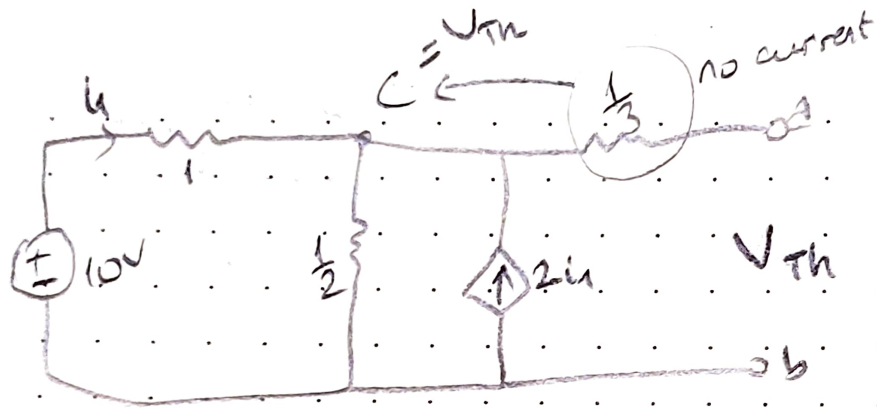


KCL at node C:

$$\frac{V_C - 10}{1} + \frac{V_C}{\frac{1}{2}} + 2 \frac{V_C - 10}{\frac{1}{3}} = 0$$

$$V_C - 10 + 2V_C + 2V_C - 20 = 0$$

$$5V_C = 30$$

$$V_{Th} = V_C = 6$$

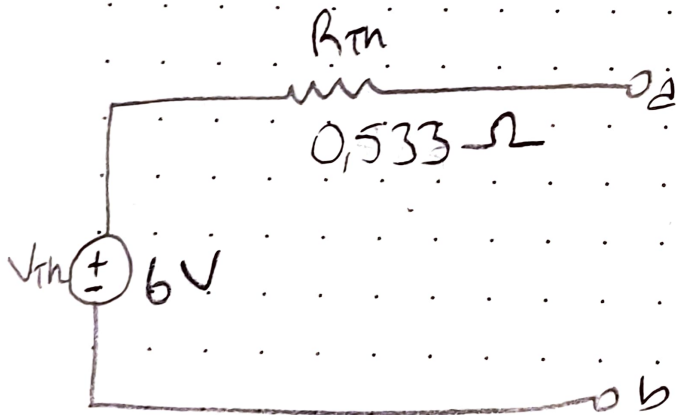

Sens ERS04  
040200434

Sens