

$$P_1 = 40 \times 4 = 160 \text{ W (supply)}$$

$$P_5 = 5 \times (0.5 \times 4)i = 10 \text{ W (supply)}$$

$$P_4 = 20 \times 2 = 40 \text{ W (supply)}$$


$$P_2 = 15 \times 4 = 60 \text{ W (absorb)}$$

$$P_3 = 25 \times \overbrace{(i + 0.5i)}^k = 150 \text{ W (absorb)}$$

$$P_5 = P_0 = 210 \text{ W} \quad \checkmark$$

Q₁

Q2

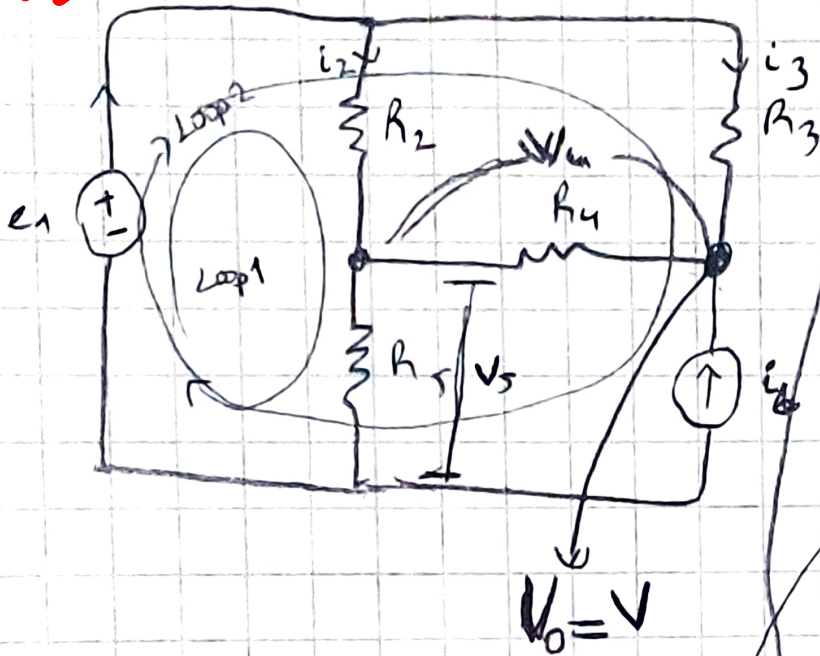

$$\text{Loop 1} \quad e_1 = i_2 R_2 + (i_2 + i_3 + i_6) R_5$$

$$\text{Loop 2} \quad e_1 = i_3 R_3 + (i_3 + i_6) R_4 + (i_2 + i_3 + i_6) R_5$$

$$e_1 = i_3 (R_3 + R_4 + R_5) + i_6 R_4 + i_2 R_5 + i_6 R_5$$

$$V_5 - V = V_4$$

$$\frac{V_5 - e_1}{R_2} + \frac{V_5}{R_5} + \frac{V_5 - V}{R_4} = 0$$

$$\frac{V - e_1}{R_3} - i_6 + \frac{V - V_5}{R_4} = 0$$

$$-V_4 \left(\frac{1}{R_3} + \frac{1}{R_4} \right) + \frac{V_5}{R_3} = \frac{e_1}{R_2} + i_6$$

Node 1

Q₃

$$\frac{V_1 - V_4}{R_5} + \frac{V_1 - V_2}{R_1} + \beta \underset{\substack{\downarrow \\ V_1 - V_2}}{V_2} = 0$$

$$\frac{V_1 - V_4}{R_5} + \frac{V_1 - V_2}{R_1} + \beta (V_1 - V_2) = 0$$

$$V_1 \left[\frac{1}{R_5} + \frac{1}{R_1} + \beta \right] - V_2 \left[\frac{1}{R_1} + \beta \right] - \frac{V_4}{R_5} = 0$$

Node 2

$$\frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_2 - V_3}{R_3} = 0$$

$$-\frac{V_1}{R_1} + V_2 \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] - \frac{V_3}{R_3} = 0$$

Node 3

$$V_3 = e$$

Node 4

$$-I + \frac{V_4 - V_1}{R_5} + \frac{V_4 - V_3}{R_4} = 0$$

$$-\frac{V_1}{R_5} - \frac{V_3}{R_4} + V_4 \left[\frac{1}{R_4} + \frac{1}{R_5} \right] = I$$

$$\begin{bmatrix} \left(\frac{1}{R_1} + \frac{1}{R_5} + \beta \right) & \left(-\frac{1}{R_1} - \beta \right) & 0 & -\frac{1}{R_5} \\ -\frac{1}{R_1} & \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) & -\frac{1}{R_3} & 0 \\ 0 & 0 & 1 & 0 \\ -\frac{1}{R_5} & 0 & -\frac{1}{R_4} & \left(\frac{1}{R_4} + \frac{1}{R_5} \right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ e \\ I \end{bmatrix}$$

Mesh on i_1 and i_3 loop

$$-1 + 7(i_1 - i_2) - 3(i_3 - i_2) + 2i_3 = 0$$

$$i_3 \text{ loop} = 2$$

$$7i_1 - 4i_2 - i_3 = 1$$

$$7i_1 - 4i_2 - 2 - i_1 = 1$$

$$i_1 = \frac{3 + 4i_2}{6}$$

Q₄

Mesh on i_2 loop

$$i_2 + 3(i_2 - i_3) + 7(i_2 - i_1) = 0$$

$$11i_2 - 3i_3 - 7i_1 = 0 \rightarrow i_3 = 2 + i_1$$

$$11i_2 - 10i_1 = 6$$

$$11i_2 - 10 \frac{3 + 4i_2}{6} = 6$$

$$\underline{i_2 = 0.6226 \text{ A}}$$




$$i_1 = \frac{3 + 4i_2}{6}$$

$$\underline{i_1 = 0.915 A}$$


$$i_3 = 2 + i_1$$



$$\underline{i_3 = 2.915 A}$$

~~Q~~₅

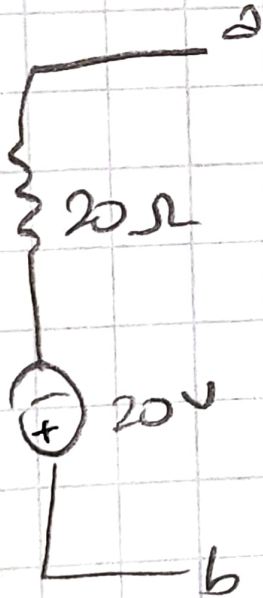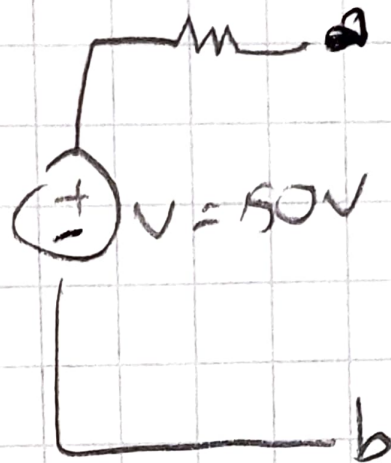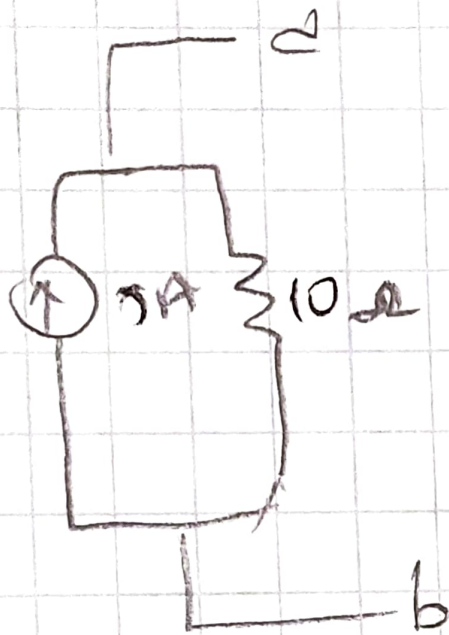

→ 1A

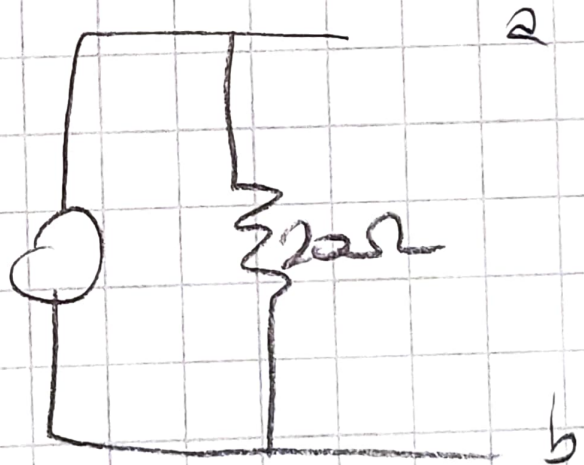

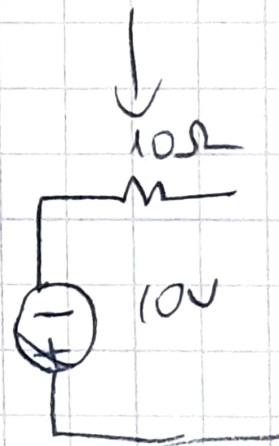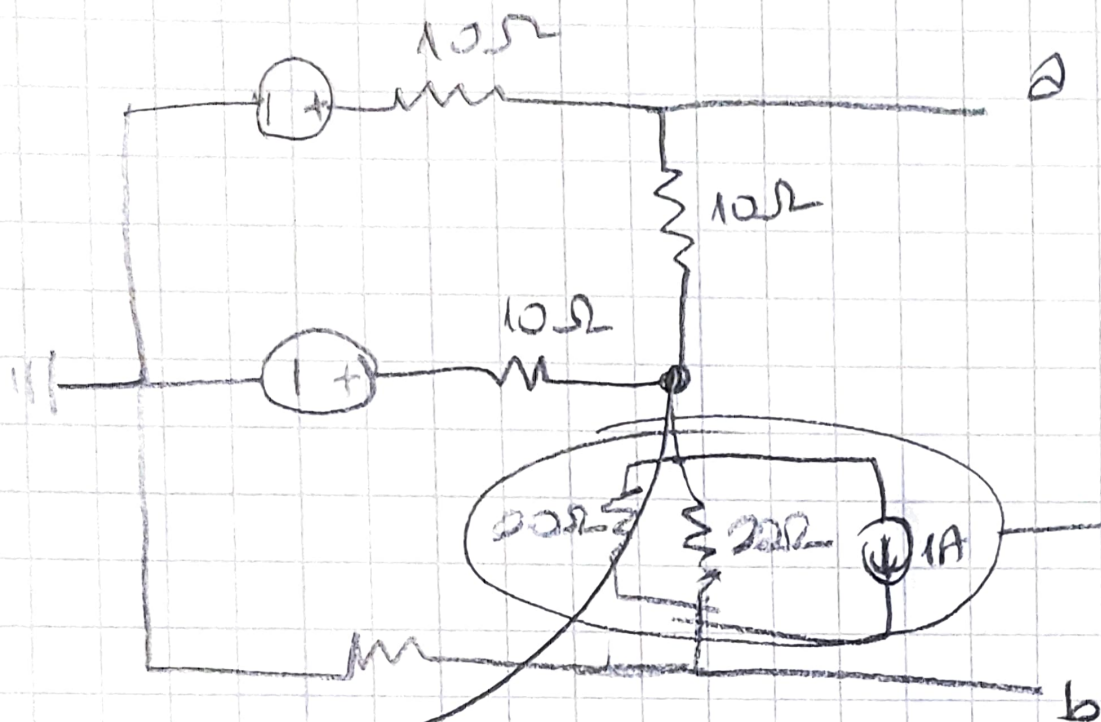

KCL

$$I_1 + I_2 + I_3 = 0$$

$$\frac{V - 30}{20} + \frac{V - 50}{10} + \frac{V + 10}{20} = 0$$

$$4V = 120$$

$$V = 30 \text{ V}$$

$$I_1 = \frac{V - 30}{20} = \underline{\underline{0 \text{ A}}}$$

$$I_3 = \frac{30 + 10}{20} = \underline{\underline{2 \text{ A}}}$$

Then apply KVL to the loop on the right


$$10 - 10I_3 + 10I_1 + V_{th} = 0$$

$$V_{th} = 10I_3 - 10I_1 - 10$$


$$V_{th} = 10 \text{ Volt}$$




To find R_{Th}

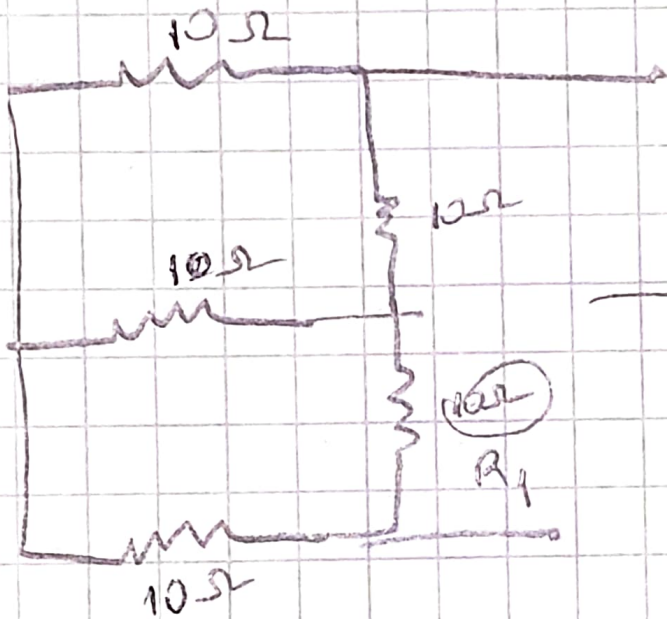

→




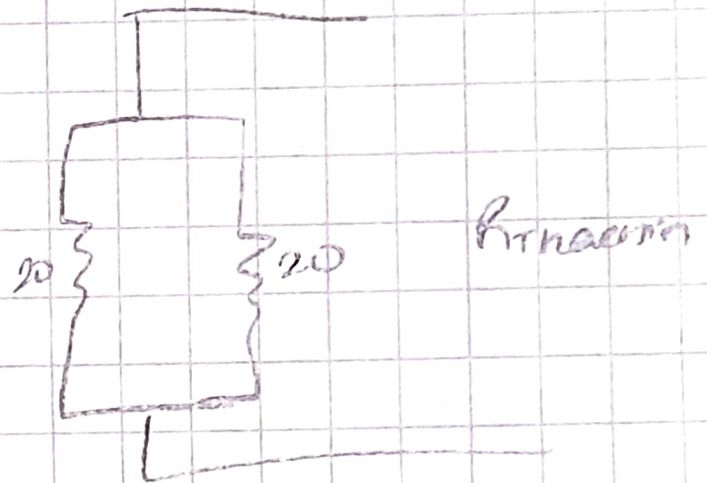


$$R_{Th} = 10\ \Omega$$

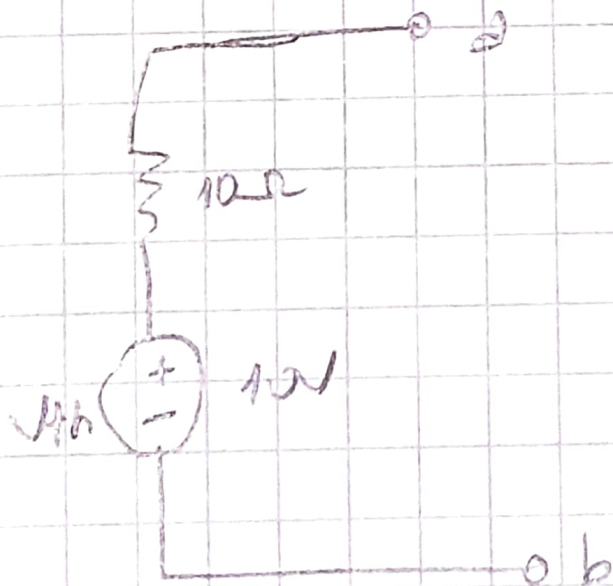


$$V_{Th} = 10\text{V}$$



$$R_{Th} = 10\ \Omega$$

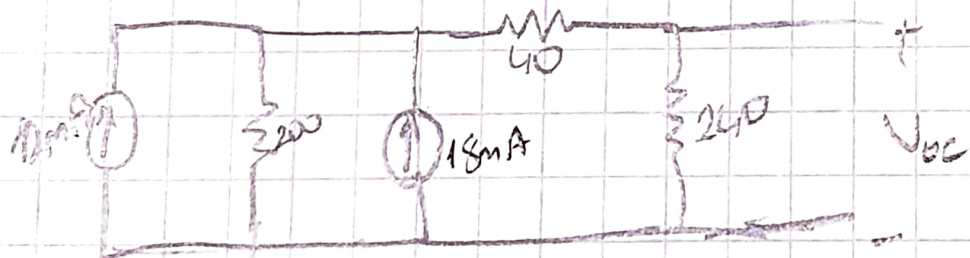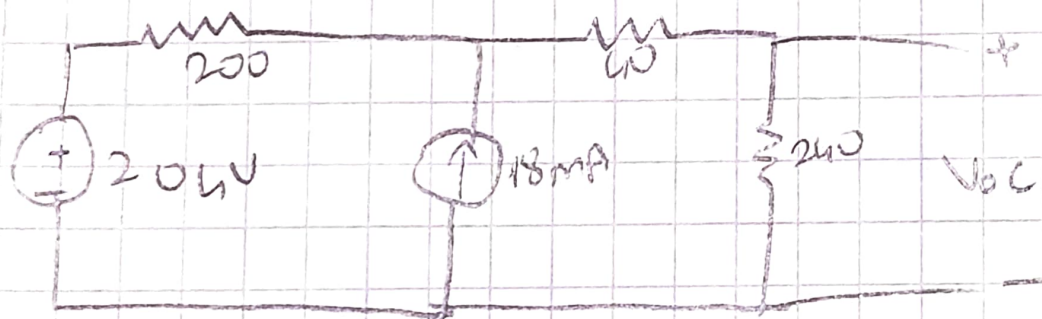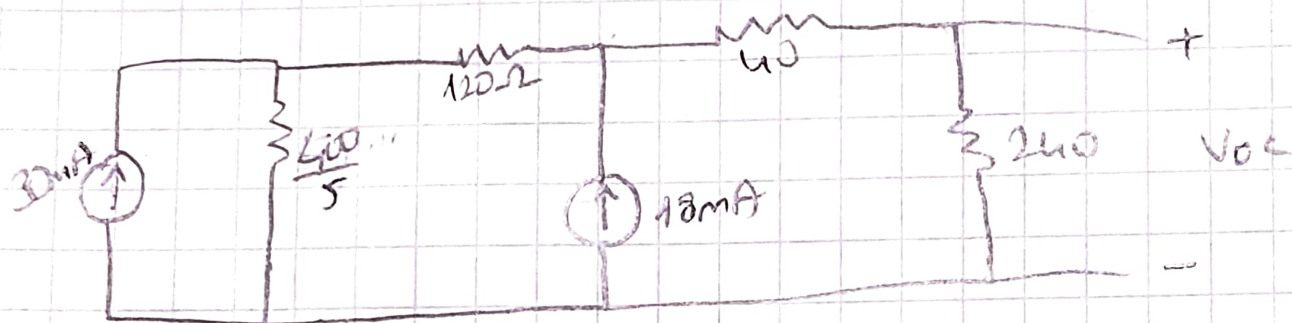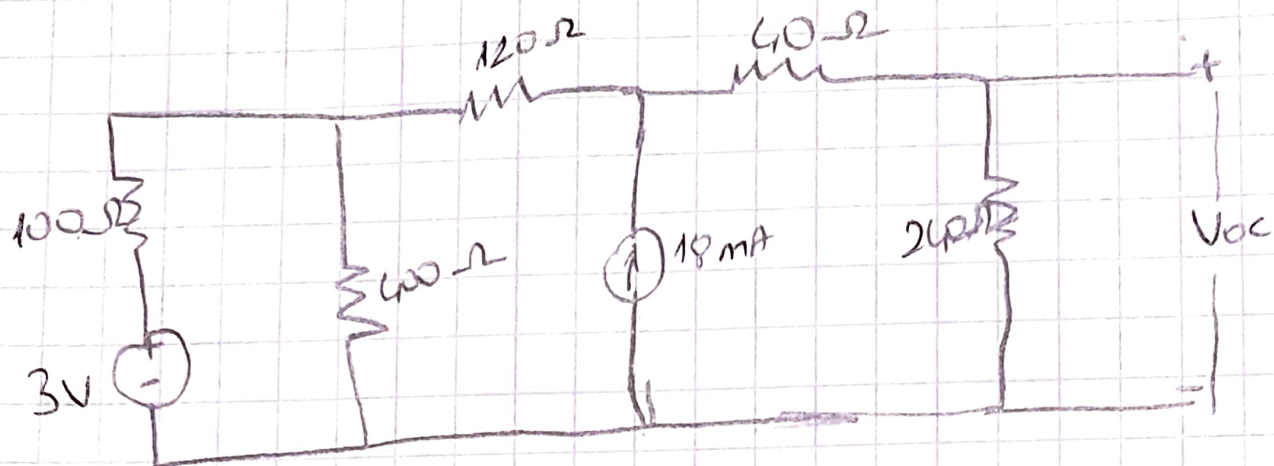


Q₆

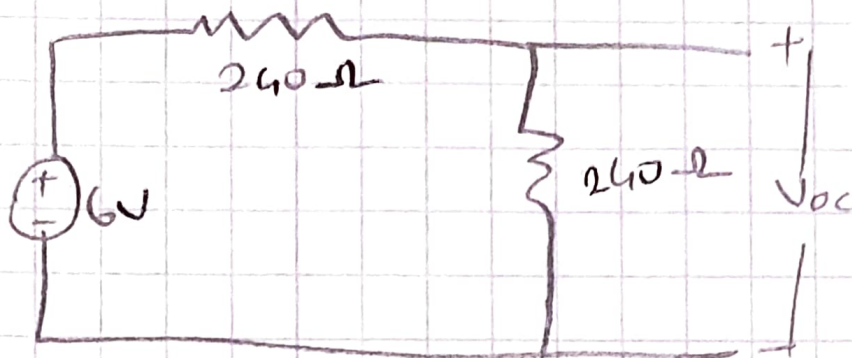
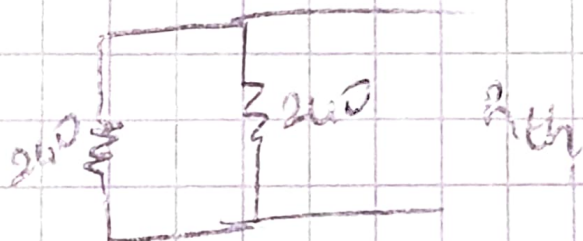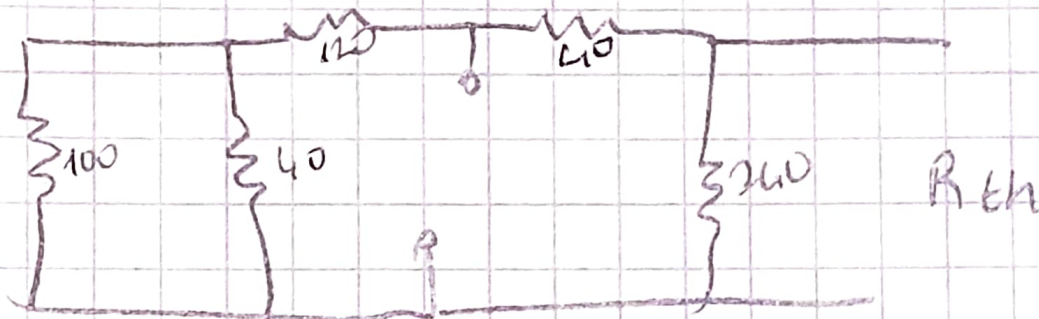
$$V_{oc} = \frac{6 \times 240}{240 + 200 + 40} = 3V$$



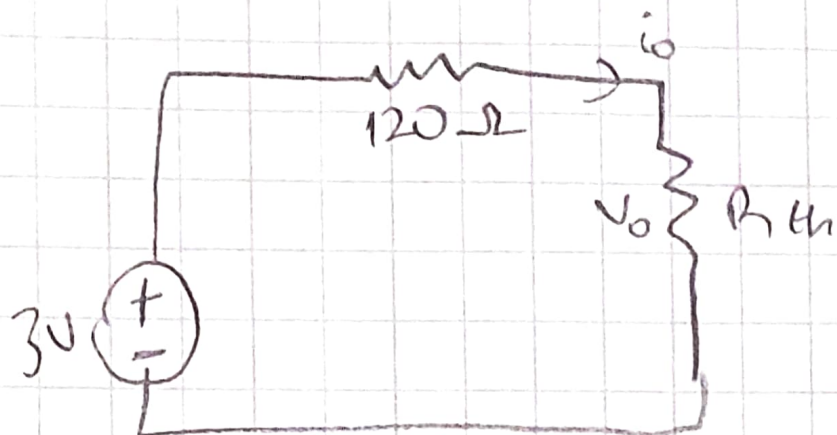

$$i_o = \frac{3}{120 + R_o}$$

$$V_o = \frac{3R_o}{120 + R_o}$$

for $R_o = 100 \Omega$

$$i_o = 13.636 \text{ mA}$$

$$V_o = 1.363 \text{ V}$$

Serie JERSO4
04.02.004.34
SMA

for $R_o = 200 \Omega$

$$i_o = 9.375 \text{ mA}$$

$$V_o = 1.875 \text{ V}$$