
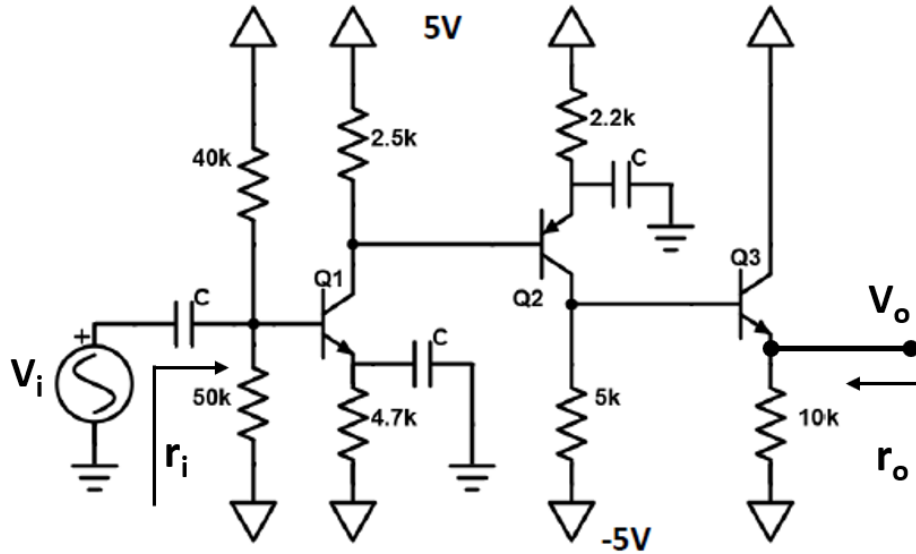


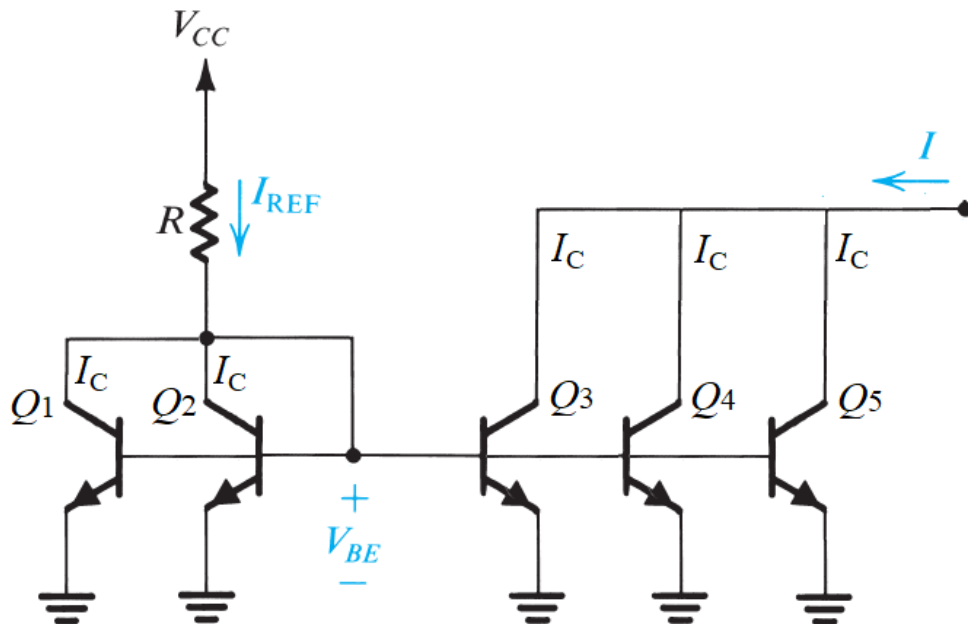1. For the circuit shown find the small-signal voltage gain (V_o/V_i), input impedance (r_i) and output impedance expressions (r_o) in terms of g_m , r_{π} , and resistance (like g_{m1} , g_{m2} , $r_{\pi1}$, $r_{\pi2}$, and etc). It is assumed that DC analyses has been completed ($V_A = \infty$ for all transistors). (30 points)




2. All transistors in the given figure are identical. Find the I_{REF} , I_C and I currents in terms of V_{CC} , V_{BE} , β and R . (30 points)



GOOD LUCK EVERYONE

3. Analyze the circuit below for $|V_{BE}| = 0,6 \text{ V}$, $\beta = h_{fe} = h_{FE} = 100$, $V_T = 25 \text{ mV}$: (40 points)
- Design the current source of 0,5 mA. Use meaningful resistor values. (10 points)
 - What should be the value of R_{E4} so that clipping at the output of the circuit is minimal and symmetrical? If you cannot find the value of I_{C3} current, assume 1 mA. (15 points)
 - Find the input and output resistances (r_i and r_o). (10 points)
 - If this circuit is driven with a small signal source with an internal resistance of 1k and a load resistor of 1k is connected to the output, find the gain. (5 points)

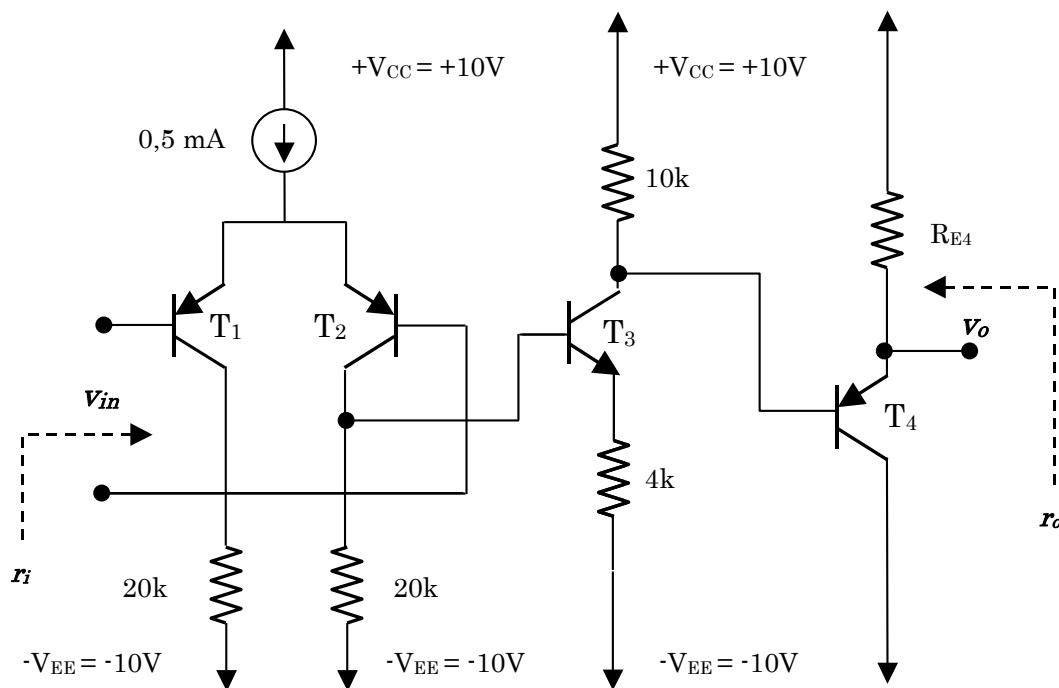

Solution 1:

$$r_{\pi} = \frac{\beta}{g_m} \quad r_e = \frac{V_T}{I_C} \quad r_e = \frac{1}{g_m} \quad h_{fe} = \beta$$

3rd stage : Common collector (or emitter follower):

$$A_v = \frac{R_e}{R_e + r_e} \quad r_i = h_{fe}(R_e + r_e) \quad r_o = R_e // r_e$$

$$A_{v3} = \frac{R_{e3}}{R_{e3} + r_{e3}} = \frac{10k}{10k + r_{e3}} \quad r_{i3} = h_{fe}(10k + r_{e3})$$

2nd stage : Common emitter:

$$A_v = -g_m(R_C // R_L) = -\frac{(R_C // R_L)}{r_e} \quad r_i = h_{fe}(R_e + r_e)$$

$$A_{v2} = -g_{m2}(5k // r_{i3}) \quad r_{i2} = h_{fe}r_{e2}$$

1st stage : Common emitter:

$$A_{v1} = -g_{m1}(2.5k // r_{i2}) \quad r_{i1} = h_{fe}r_{e1} = r_{\pi1}$$

Total gain:

$$A_v = A_{v1} \cdot A_{v2} \cdot A_{v3} = g_{m1}(2.5k // r_{i2}) \cdot g_{m2}(5k // r_{i3}) \cdot \frac{10k}{10k + r_{e3}}$$

Input impedance:

$$r_i = r_{i1} = r_{\pi1}$$

Output impedance:

$$r_o = r_{o3} = R_{e3} // r_{e3} = 10k // r_{e3}$$

Solution 2:

$$V_{CC} = I_{REF} \cdot R + V_{BE} \Rightarrow I_{REF} = \frac{V_{CC} - V_{BE}}{R} \quad (10p)$$
$$I_{REF} - 2I_C - 5I_B = 0$$
$$I_C = \frac{\beta I_{REF}}{(2\beta + 5)} = \frac{\beta (V_{CC} - V_{BE})}{(2\beta + 5)R} \quad (10p)$$
$$I = 3I_C = \frac{3\beta (V_{CC} - V_{BE})}{(2\beta + 5)R} \quad (10p)$$

Solution 3:

- a. Assuming you all know about current mirrors, we omit that part; do NOT forget to make sure that both transistors operate in active region

b. for $V_o = 0V$ $V_{B4} = V_{BE4} = V_{C3} = V_{CC} - R_{C3}(I_{C3} - I_{B4}) = 10V - 10k \cdot (I_{C3} - I_{B4})$

1st stage:

$$I_{C1} = I_{C2} = \underline{\underline{0.25mA.}}$$

2nd stage:

$$20k - T_3 - 4k \text{ loop} - 20k(I_{C2} - I_{B3}) + V_{BE3} + 4k \cdot I_{E3} = 0 \quad I_{C3} = h_{FE} \frac{20k \cdot I_{C2} - V_{BE3}}{(h_{FE} + 1)4k + 20k} \text{ and}$$

thus $I_{C3} = \underline{\underline{1,04mA}}$.

3rd stage:

$$V_{B4} = V_{BE4} = -0,6V = 10V - 10k \cdot (I_{C3} - I_{B4}) \text{ and here we made a mistake and found}$$

$$I_{C4} = \underline{\underline{2mA}}. \text{ In fact } I_{C4} = \underline{\underline{-1,05mA}}.$$

with that mistake we found

$$V_o = V_{CC} - R_{E4}I_{E4} = 10V - R_{E4}(h_{FE} + 1)I_{B4} = 0V \text{ thus } R_{E4} = \frac{10V}{(h_{FE} + 1)I_{B4}} = \underline{\underline{4k95}}$$

$$r_{e1} = r_{e2} = \frac{V_T}{0,25mA} = \underline{\underline{100\Omega}}; r_{e3} = \frac{V_T}{1,04mA} = \underline{\underline{24\Omega}}; r_{e4} = \frac{V_T}{2mA} = \underline{\underline{12,5\Omega}}$$

$$K_v = \frac{v_o}{v_{in}} = \frac{v_o}{v_{b4}} \cdot \frac{v_{b4}}{v_{b3}} \cdot \frac{v_{b3}}{v_{in}} = + \frac{R_{e4}}{r_{e4} + R_{e4}} \cdot \left[- \frac{R_{C3} \parallel r_{i4}}{r_{e3} + R_{e3}} \right] \cdot \left[- \frac{R_{C2} \parallel r_{i3}}{2r_{e1}} \right] \text{ where}$$

$$r_{i3} = h_{fe}(r_{e3} + R_{e3}) = 100(24 + 4k) = \underline{\underline{402k4}}; r_{i4} = h_{fe}(r_{e4} + R_{e4}) = 100(12,5 + 4k95) = \underline{\underline{496k25}}$$

$$K_v = \frac{v_o}{v_{in}} = \frac{4k95}{12,5 + 4k95} \cdot \left[- \frac{10k \parallel 496k25}{24 + 4k} \right] \cdot \left[- \frac{20k \parallel 402k4}{2 \cdot 100} \right] = 0,997 \cdot (-2,436) \cdot (-95,265) \cong \underline{\underline{231,5}}$$

$$r_i = 2h_{FE}r_{e1} = \underline{\underline{20k}} \text{ and}$$

$$r_o = R_{E4} \parallel (r_{e4} + \frac{R_{E4}}{h_{fe}}) = R_{E4} \parallel (r_{e4} + \frac{R_{C3}}{h_{fe}}) = 4k95 \parallel (12,5 + \frac{10k}{100}) = \underline{\underline{112,5\Omega}}$$

$$\frac{v_o}{v_{b4}} = \frac{R_{e4} \parallel 1k}{r_{e4} + R_{e4} \parallel 1k}$$

$$K_v^* = \frac{v_o}{v_{in}} = \frac{v_o}{v_{b4}} \cdot \frac{v_{b4}}{v_{b3}} \cdot \frac{v_{b3}}{v_{in}} = 0,985 \cdot (-2,436) \cdot (-95,265) = \underline{\underline{228,63}}.$$

$$K_{total} = \frac{v_o}{v_g} = \frac{r_i}{r_i + R_s} \cdot \frac{R_{e4} \parallel 1k}{r_{e4} + R_{e4} \parallel 1k} \cdot \left[- \frac{R_{C3} \parallel r_{i4}}{r_{e3} + R_{e3}} \right] \cdot \left[- \frac{R_{C2} \parallel r_{i3}}{2r_{e1}} \right] = \frac{20k}{20k + 1k} \cdot 228,63 = \underline{\underline{217,74}}$$