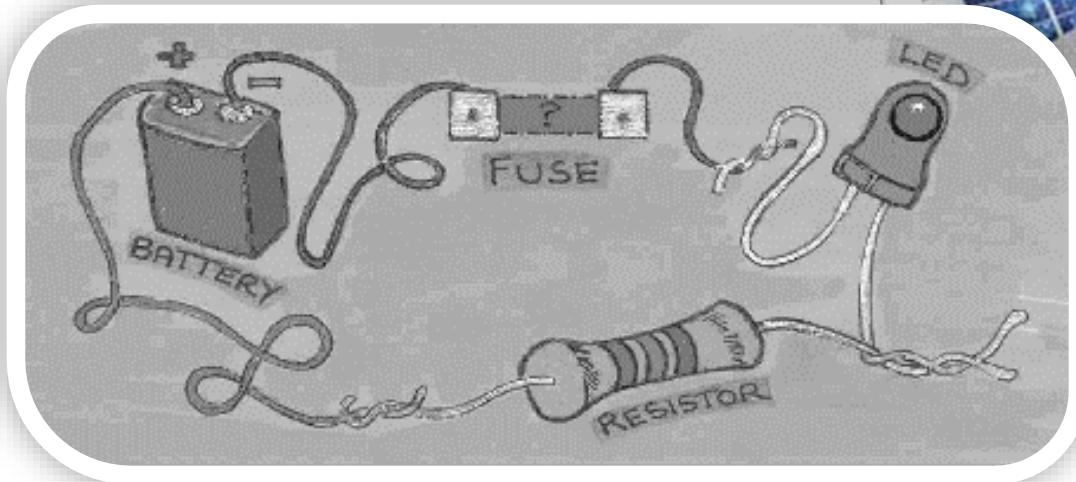



# EHB222E QUESTIONS

## 9<sup>th</sup> week



For the circuit shown, transistor parameters for identical  $T_1$  and  $T_2$  are  $V_A = \infty$ ,  $V_T = 25 \text{ mV}$ ,  $|V_{BE}| = 0,6 \text{ V}$ , and  $h_{fe} = h_{FE} = \beta = 100$ .

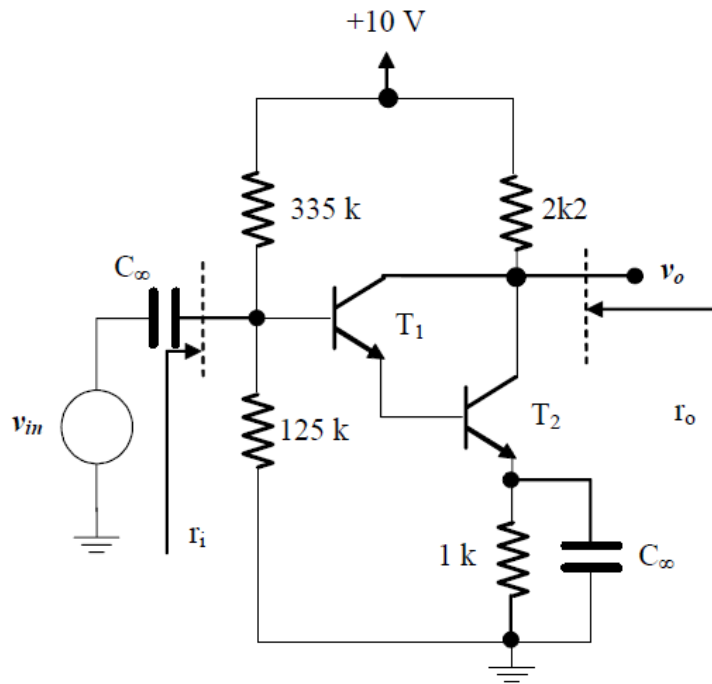
- Determine DC collector currents.
- Find the small signal voltage gain  $v_o/v_{in}$ .
- Determine the input and output resistances.



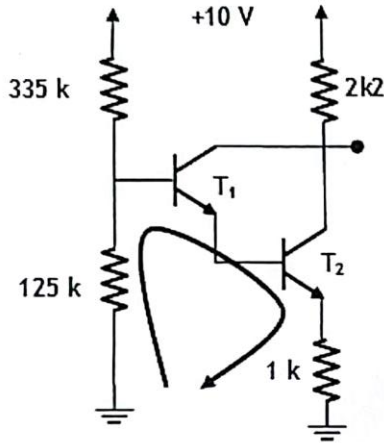1. Yandaki şekilde görüldüğü gibi

$$R_{BB} = 335k \parallel 125k = \underline{91k} \text{ ve}$$


$$V_{BB} = \frac{125k}{125k + 335k} V_{CC} = \underline{2,72V}$$



olarak  
bulunduktan sonra  
 $V_{BB}$ ,  $R_{BB}$ ,  $T_1$ ,  $T_2$  ve  
1k'lık  $R_E$ 'yi içeren  
çevremin  
denklemini yazılırsa

$$V_{BB} = (335k \parallel 125k)I_{B1} + V_{BE1} + V_{BE2} + 1k(h_{FE} + 1)I_{B2}, \text{ burada}$$

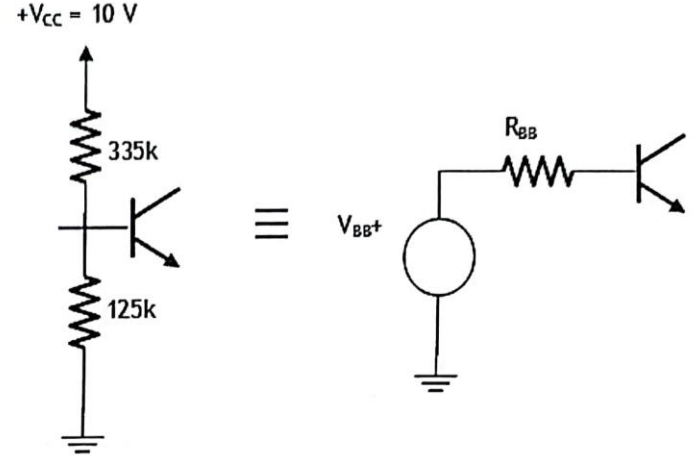
$$I_{B2} = (h_{FE} + 1)I_{B1} \text{ olduğu için}$$



$$I_{B1} = \frac{V_{BB} - V_{BE1} - V_{BE2}}{(335k \parallel 125k) + (h_{FE} + 1)^2 1k} = \frac{2,72V - 0,6V - 0,6V}{91k + 101^2 1k} = 0,147 \mu A \text{ dolayısıyla}$$

$$I_{C1} = h_{FE} * I_{B1} = \underline{14,7 \mu A}; I_{C2} = h_{FE} * I_{B2} = h_{FE} (h_{FE} + 1) I_{B1} = \underline{1,49 mA}$$
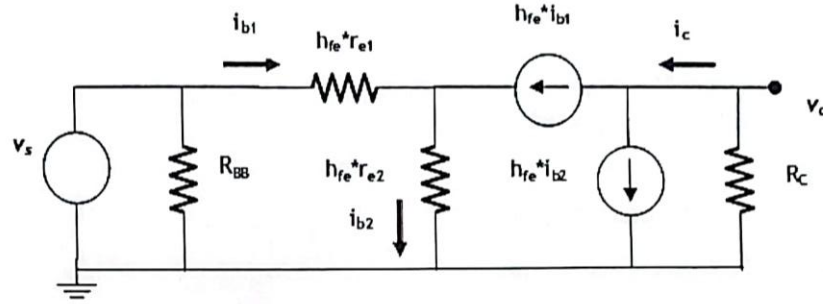
$$r_{e1} = \frac{V_T}{I_{C1}} = \underline{1k7}; r_{e2} = \frac{V_T}{I_{C2}} = \underline{16,8 \Omega} \text{ bulunur.}$$



Devrenin kazanç ifadeleri için önce küçük işaret devresini yandaki gibi çizmek gerekir.

$$v_o = -R_C i_c \text{ ve } i_c = h_{fe} i_{b1} + h_{fe} (h_{fe} + 1) i_{b1} = h_{fe} (h_{fe} + 2) i_{b1}$$

$$\text{aynca } v_s = h_{fe} r_{e1} i_{b1} + h_{fe} r_{e2} i_{b2} = h_{fe} r_{e1} i_{b1} + \frac{h_{fe} r_{e1}}{h_{fe} + 1} (h_{fe} + 1) i_{b1} = 2 h_{fe} r_{e1} i_{b1} \text{ olduğundan}$$


$$\frac{v_o}{v_s} = -\frac{R_C h_{fe} (h_{fe} + 2)}{2 h_{fe} r_{e1}} = -66,2 ; \text{ diğ er yandan } r_i = R_{BB} \parallel \frac{v_s}{i_{b1}}, r_i^* = \frac{v_s}{i_{b1}} = 2 h_{fe} r_{e1} = \underline{\underline{339k}} \text{ ve}$$

$$r_i = R_{BB} \parallel \frac{v_s}{i_{b1}} = \underline{\underline{71k8}} \text{ olarak bulunur.}$$

Devre kolektör çıkışlı olduğu için  $r_o = R_C = \underline{\underline{2k2}}$  dir.

For the circuit shown, transistor parameters for identical  $Q_1$  and  $Q_2$  are  $V_A = \infty$ ,  $V_T = 25 \text{ mV}$ ,  $|V_{BE}| = 0,6 \text{ V}$ , and  $\beta = 100$ .

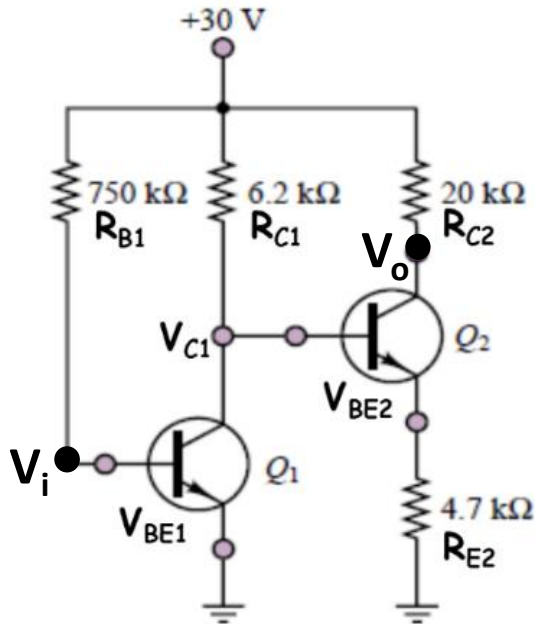- Determine DC collector currents.
- Find the small signal voltage gain  $v_o/v_{in}$ .
- Determine the input and output resistances.



**Problem BJT:** - For the circuit below assume both transistors are silicon-based with  $\beta = 100$ . Determine:  
**a)**  $I_{C1}$ ,  $V_{C1}$ ,  $V_{CE1}$ . **b)**  $I_{C2}$ ,  $V_{C2}$ ,  $V_{CE2}$ .

• **Soln:**


Assume  $V_{BE} = V_{BE1} = V_{BE2} = 0.7V$

• **Part (a):** - Apply KVL along the path (red line).

$$-30 + I_{B1} * R_{B1} + V_{BE1} = 0$$

$$I_{B1} = \frac{30 - 0.7}{750 * 10^3} = 39.07 \mu A$$

$$I_{C1} = \beta * I_{B1} = 3.907 mA$$

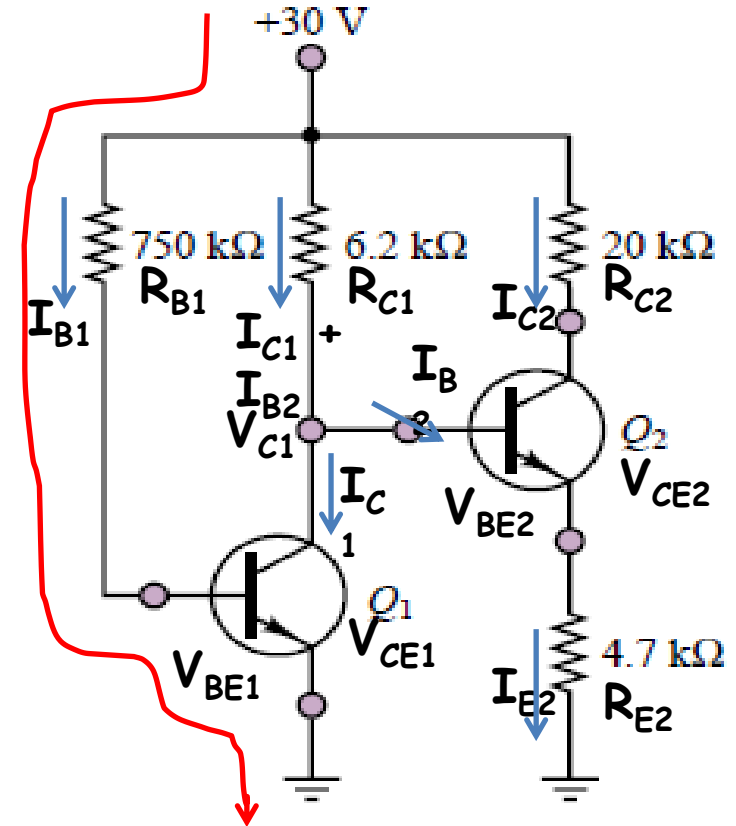

- **Part (a) contd.:** - Apply KVL along the path (red line).

We know that  $30 - (I_{C1} + I_{B2})R_{C1} - V_{BE2} - I_{E2}R_{E2} = 0$

substituting we get  $I_E = (\beta + 1)I_B$

$$30 - 24.2234 - I_{B2}R_{C1} - 0.7 - (\beta + 1)I_{B2}R_{E2} = 0$$

$$5.0766 - I_{B2}(R_{C1} + 101 * R_{E2}) = 0$$


$$\Rightarrow I_{B2} = 10.559 \mu A$$

$$V_{C1} = 30 - (I_{C1} + I_{B2}) * R_{C1}$$

$$V_{C1} = 30 - (3.907 + 0.010559) * 6.2$$

$$= 5.7111 \text{ [V]}$$

$$V_{CE1} = V_{C1} = 5.7111 \text{ V}$$

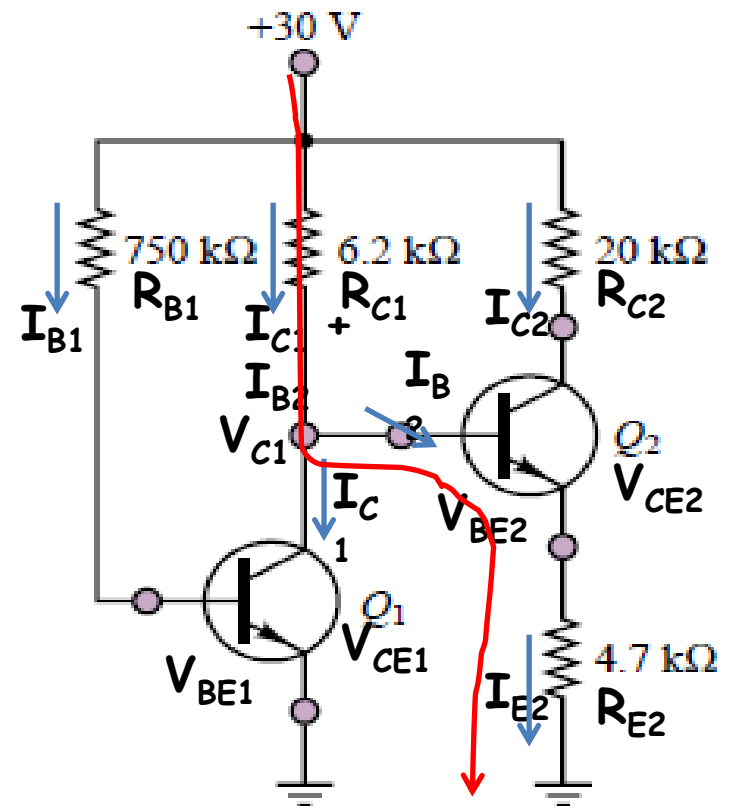

- **Part (b):** - Apply KVL along the path (red line).

$$I_{E2} = (1 + \beta)I_{B2} = 101 * 10.559 \mu A = 1.0662 mA$$


$$I_{C2} = I_{B2}\beta = 1.0556 mA$$

$$V_{C2} = 30 - I_{C2}R_{C2}$$

$$V_{C2} = 30 - 1.0556 * 20 = 8.888 V$$


$$V_{E2} = I_{E2}R_{E2} = 5.011 V$$

$$V_{CE2} = V_{C2} - V_{E2} = 3.8769 V$$

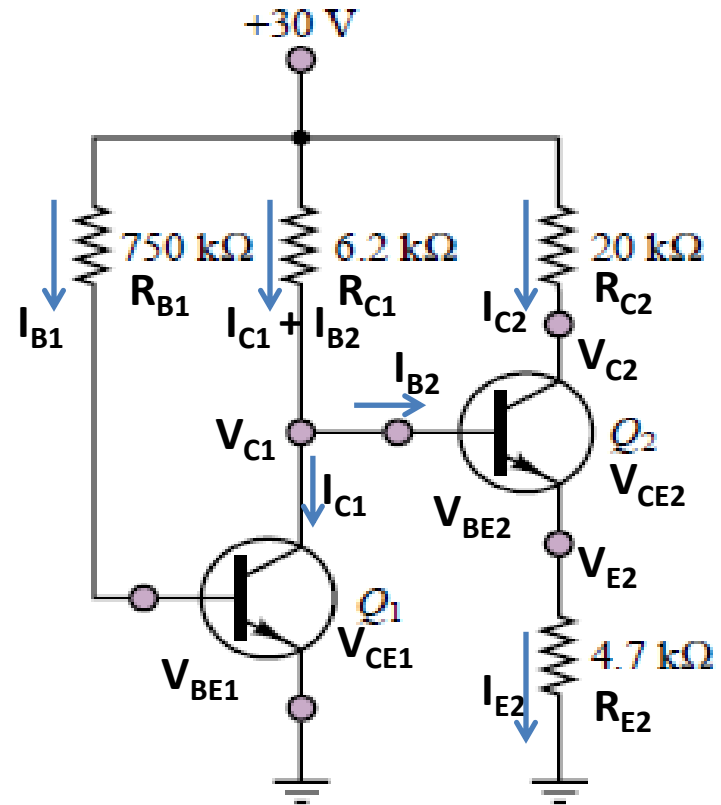





# Example

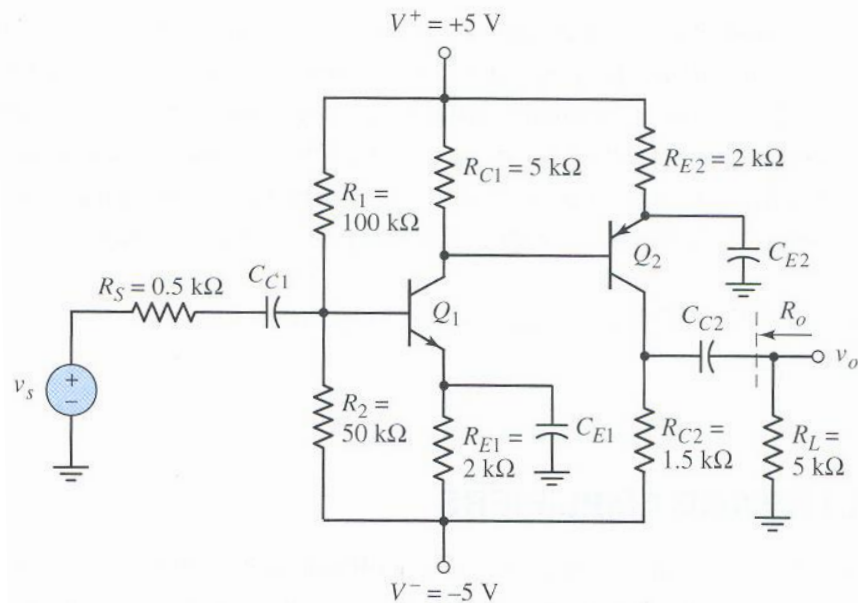

**Figure 4.60** A two-stage amplifier in a cascade configuration

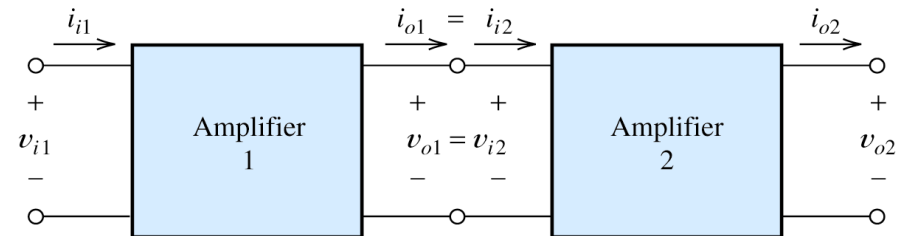

Cascade connection of two amplifiers.

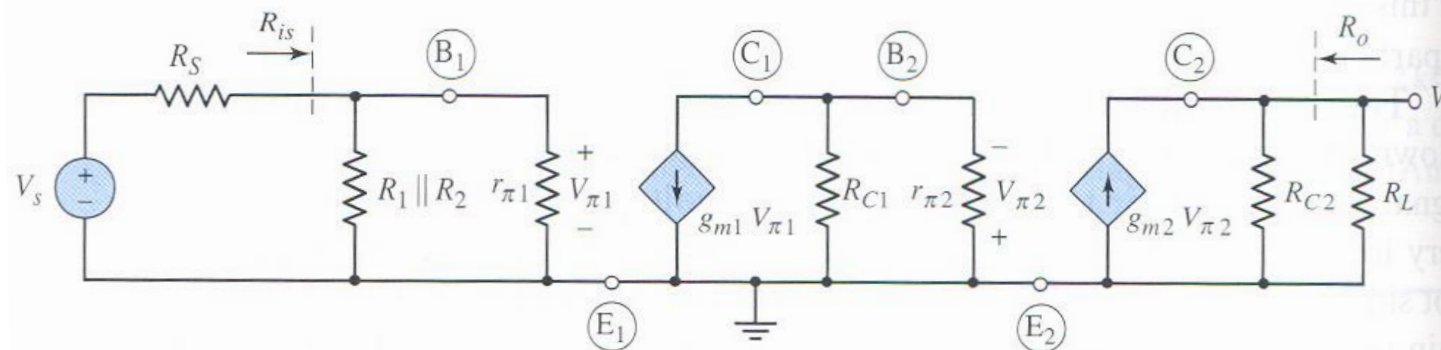

**Figure 4.61** Small-signal equivalent circuit of the cascade configuration

# Cascade Connection (cont.)

Small signal gain:  $A_V = A_{V1} A_{V2}$   $V_{\pi1} = V_i, V_{\pi2} = -V_{O1}$


$$V_{O1} = -g_{m1} V_i (R_{C1} // r_{\pi2}) \quad V_O = -g_{m2} V_{O1} (R_{C2} // R_L)$$

$$A_V = \frac{V_O}{V_i} = (-g_{m1} (R_{C1} // r_{\pi2})) (-g_{m2} (R_{C2} // R_L))$$

$$A_V = \frac{V_O}{V_S} = g_{m1} (R_{C1} // r_{\pi2}) g_{m2} (R_{C2} // R_L) \left( \frac{R_{is}}{R_{is} + R_S} \right)$$


Input resistance:  $R_{is} = R_1 // R_2 // r_{\pi1}$

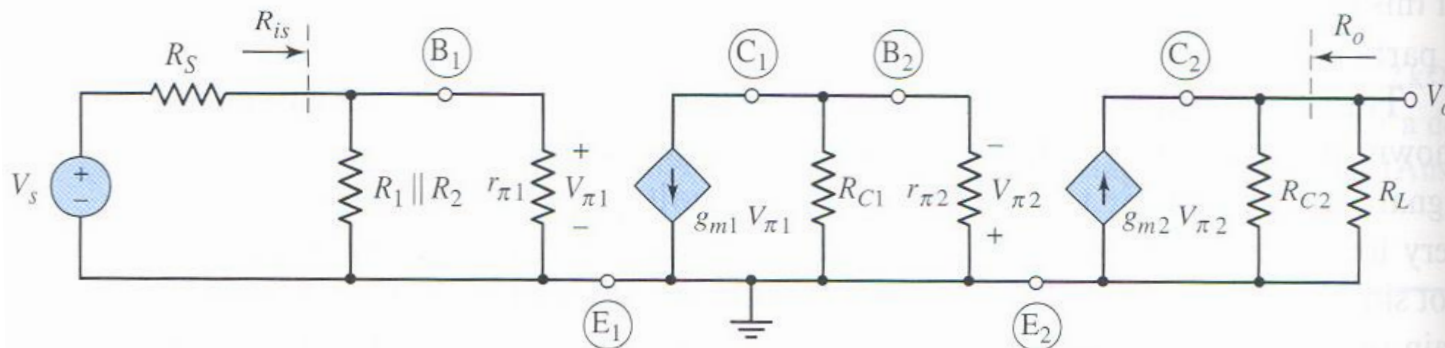Output resistance:  $V_S = 0 \quad v_{\pi1} = v_{\pi2} = 0 \quad R_0 = R_{C2}$



$$V_A = \infty$$

# Exercise


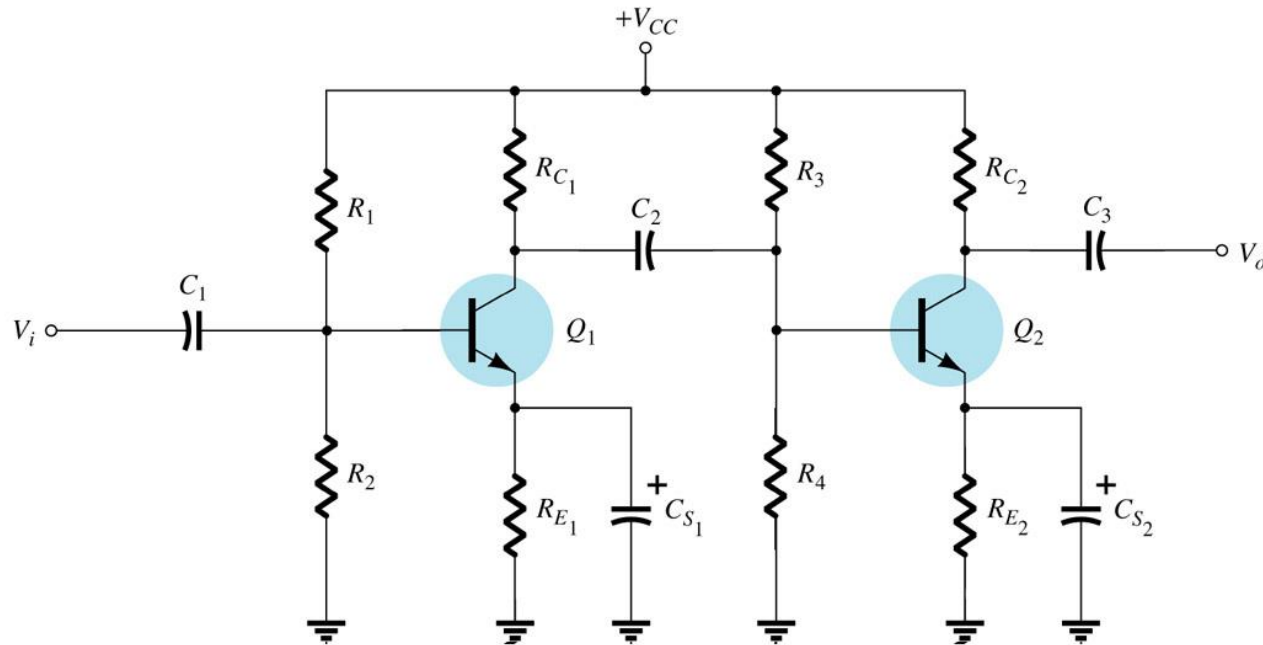


Draw the ac equivalent circuit and calculate the voltage gain, input resistance and output resistance for the cascode BJT amplifier in above Figure. Let the parameters are:

$$V_{CC} = 20V, \beta_{Q1} = \beta_{Q2} = 200, V_{BE(ON)} = 0.7V, r_0 = \infty$$

$$R_1 = R_3 = 15k\Omega, R_2 = R_4 = 4.7k\Omega, R_{C1} = R_{C2} = 2.2k\Omega, R_{E1} = R_{E2} = 1k\Omega$$

# Solution

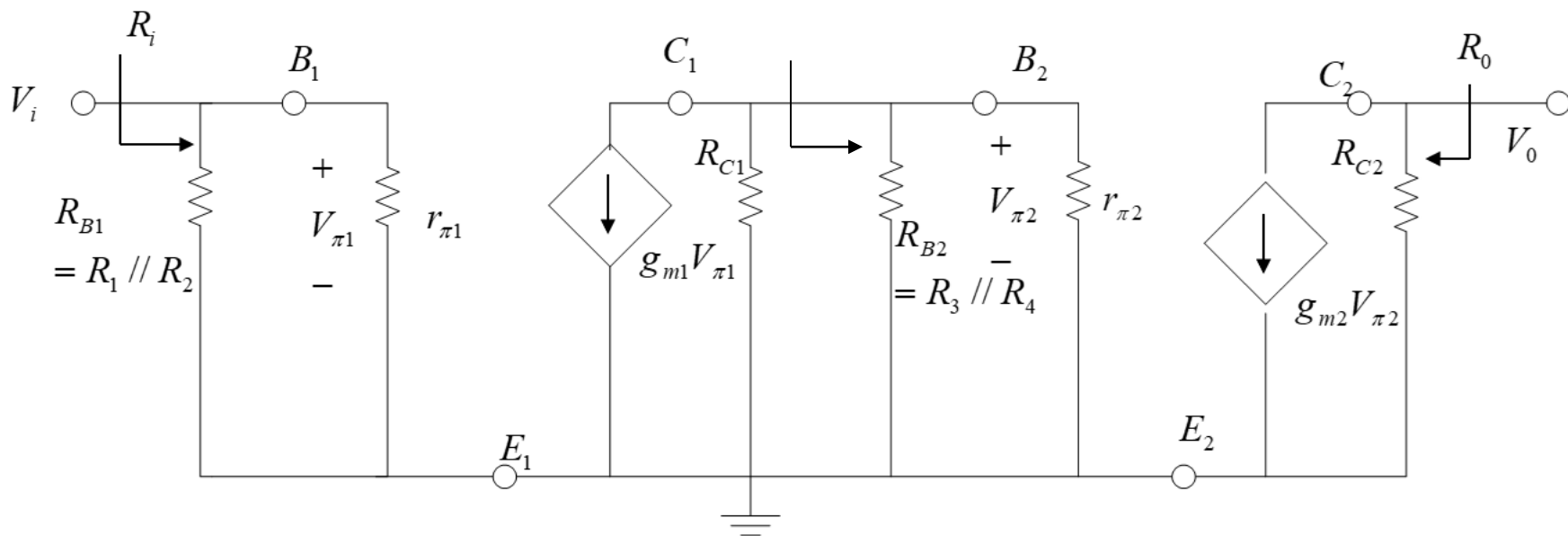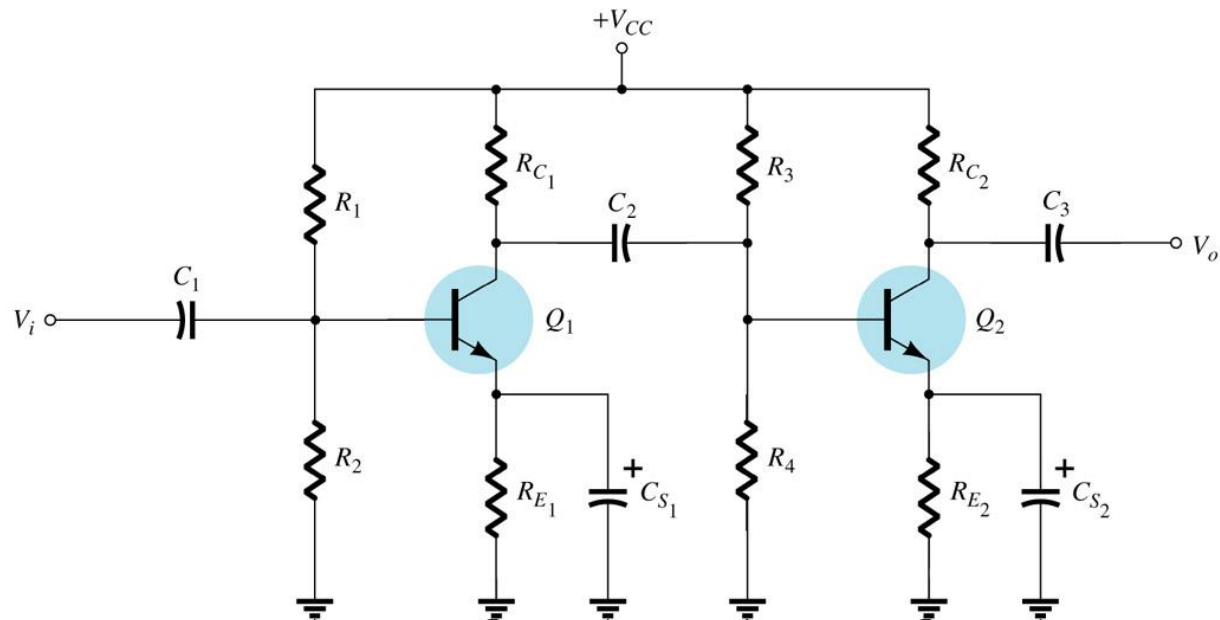

Ac equivalent circuit for cascade amplifier

# Solution:

DC analysis:

At Q1:

$$I_{BQ1} = 19.89 \mu A$$

$$I_{CQ1} = 3.979 mA$$

At Q2:

$$I_{BQ2} = 19.89 \mu A$$

$$I_{CQ2} = 3.979 mA$$

AC analysis:

At Q1:

$$r_{\pi 1} = 1.307 k\Omega$$

$$g_{m1} = 0.153 S$$

At Q2:

$$r_{\pi 2} = 1.307 k\Omega$$

$$g_{m2} = 0.153 S$$

# Solution:

From the ac equivalent circuit:

At Q1, the voltage gain is:  $A_{VQ1} = \frac{V_{0Q1}}{V_i} = -g_m (R_{C1} // R_{i2})$


Where  $V_{0Q1}$  is the voltage looking to the Q1 transistor

and  $R_{i2}$  is the resistance looking into Q2 transistor


$$R_{i2} = R_{B2} // r_{\pi2} = 15k // 4.7k // 1.307k = 957.36\Omega$$

The voltage gain at Q1 is:
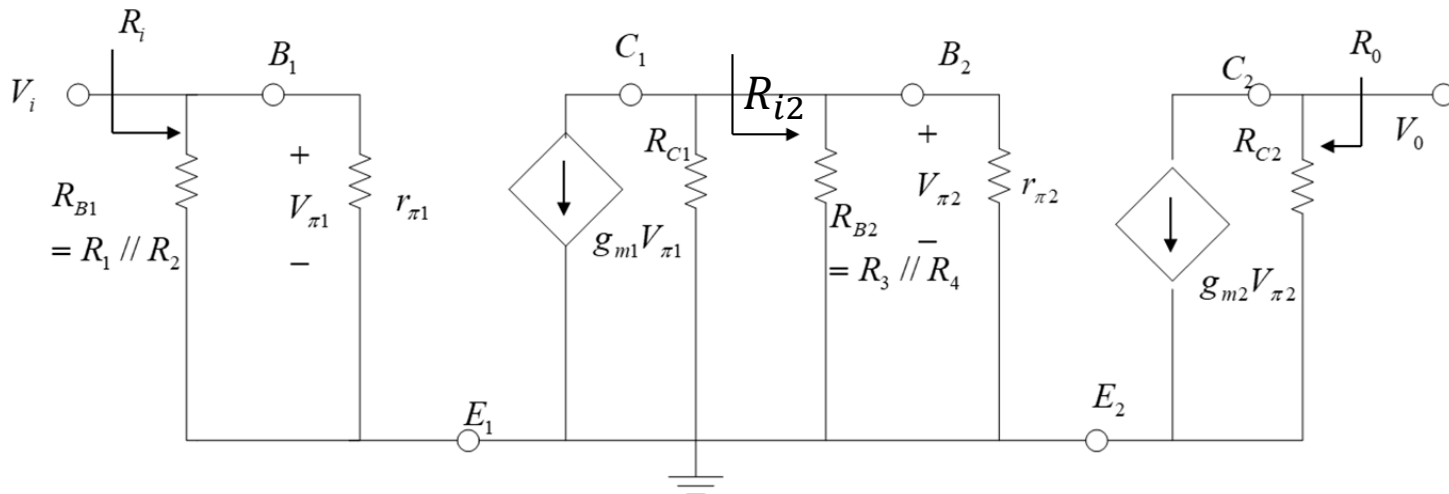
$$A_{VQ1} = -0.153(2.2k // 957.36) = -102.06$$



# Solution:

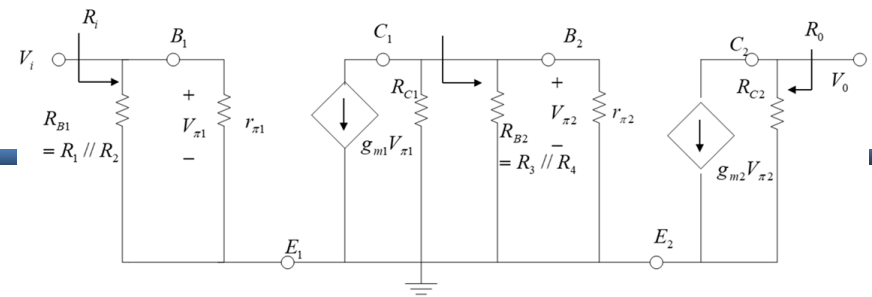

From the ac equivalent circuit:

At Q2, the voltage gain is:

$$A_{VQ2} = \frac{V_0}{V_{iQ2}} = -g_m (R_{C2})$$

Where  $V_{iQ2}$  is the voltage looking into the Q2 transistor

Therefore, the voltage gain at Q2 is:

$$A_{VQ2} = -0.153(2.2k) = -336.6$$

The overall gain is then,

$$A_V = A_{VQ1} A_{VQ2} = (-102.06)(-336.6) = 34,353$$

**\*\* The large overall gain can be produced by multistage amplifiers!!**  
So, the main function of cascade stage is to provided the larger overall gain

# Solution:

From the ac equivalent circuit:

The input resistance is:

$$R_i = R_1 // R_2 // r_{\pi 1} = 15k // 4.7k // 1.307k \\ = 957.36\Omega$$

The output resistance is:  $R_o = R_{C2} = 2.2k\Omega$

