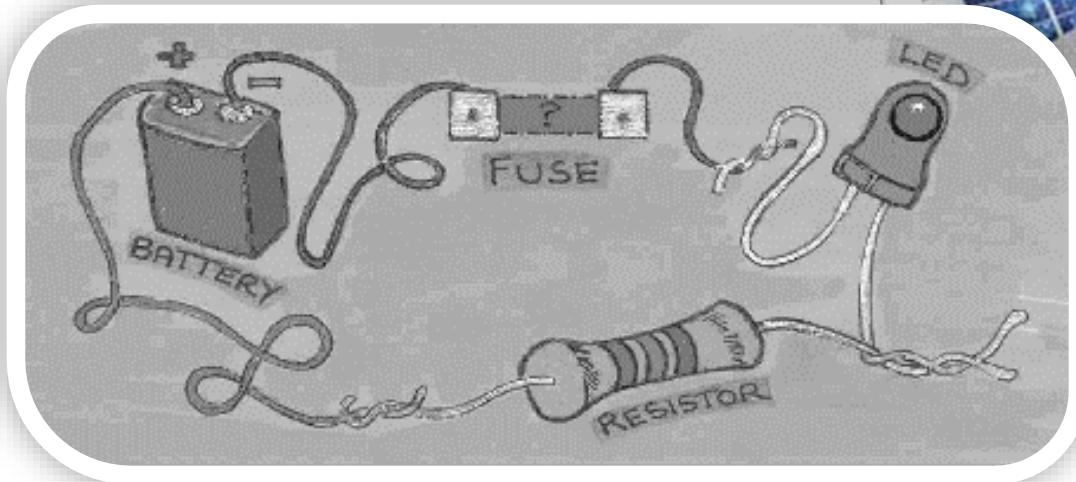


# EHB222E QUESTIONS


## 8<sup>th</sup> week




Consider the amplifier shown below. Use the following parameters for your calculations. Transistor parameters :  $\beta=200$ ,  $V_{BE}=0.7V$ ,  $V_T=25mV$ ,  $V_A=100V$

a. Find  $V_B$  and  $V_o$  of the transistor by performing DC analysis.

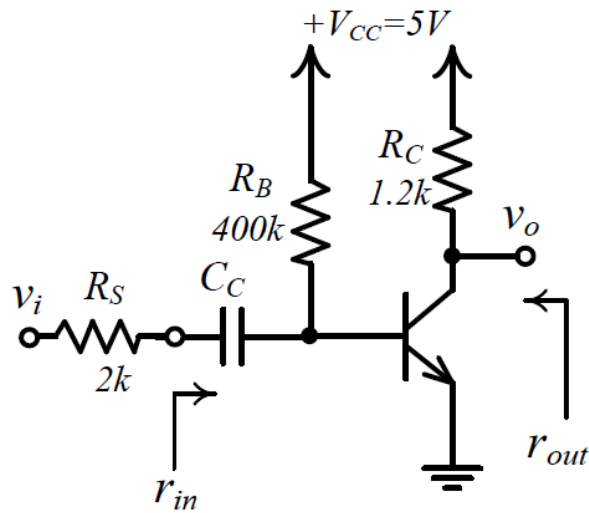b. Find the small signal values of  $r_{in}$ ,  $r_{out}$ , and  $v_o/v_{in}$ .



$$r_{\pi} = \frac{V_T}{I_{BQ}}$$

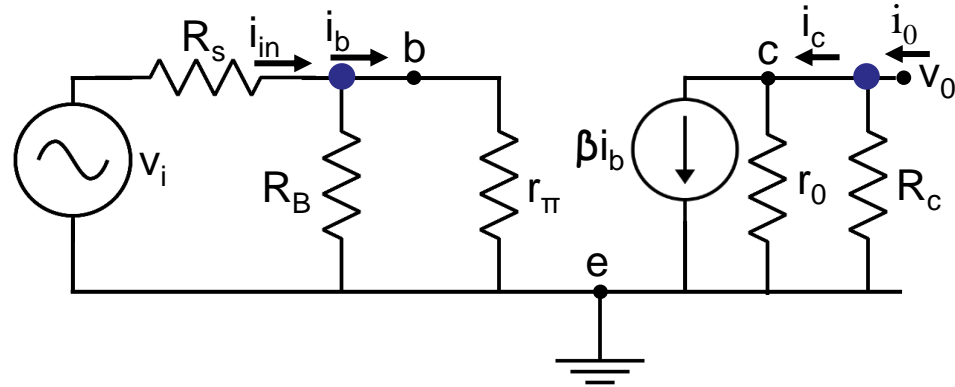

$$5V - I_B 400k\Omega - V_{BE} = 0 \Rightarrow I_B \text{ SOLVED}$$

$$V_{BE} = V_B = 0.7V$$


$$5V - \beta I_B 1.2k\Omega = V_o \Rightarrow V_o \text{ SOLVED}$$

$$v_{be} = \frac{R_B // r_{\pi}}{R_S + R_B // r_{\pi}} v_i = i_b r_{\pi}$$

$$r_{in} = \frac{v_i}{i_{in}} = R_B // r_{\pi} \quad r_o = \frac{V_A}{I_{CQ}}$$


$$v_o = -\beta i_b (r_o // R_C) \quad r_{out} = \frac{v_o}{i_o} = r_o // R_C \quad \frac{v_o}{v_i} = \frac{-R_B // r_{\pi}}{r_{\pi} (R_S + R_B // r_{\pi})} \beta (r_o // R_C)$$

Consider an amplifier shown below. "Cc" capacitor can be considered shorted in small signal analysis. Find the small signal values of  $r_{in}$  and  $v_{out}/v_{in}$ . PNP Transistor Parameters:  $|V_{BE}| = 0.7$ ,  $\beta = 100$ ,  $|V_A| = \infty$ ,  $V_T = 25 \text{ mV}$

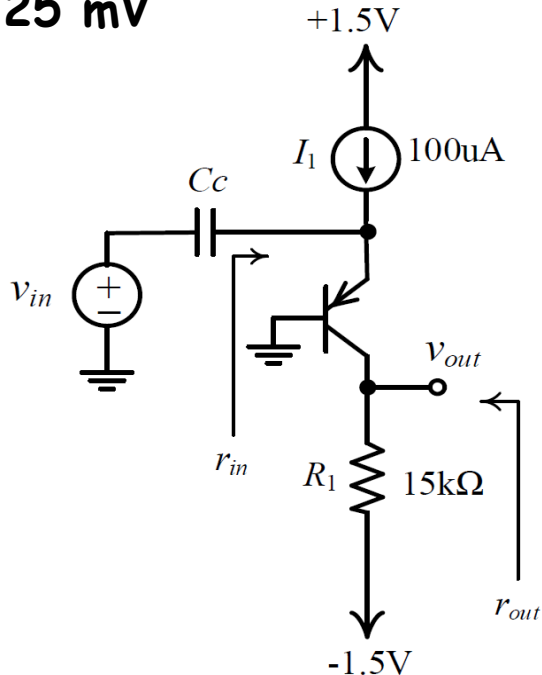

$$I_E = 100\mu A \quad I_B = \frac{I_E}{\beta + 1} = 1\mu A$$

$$I_C = 99\mu A$$


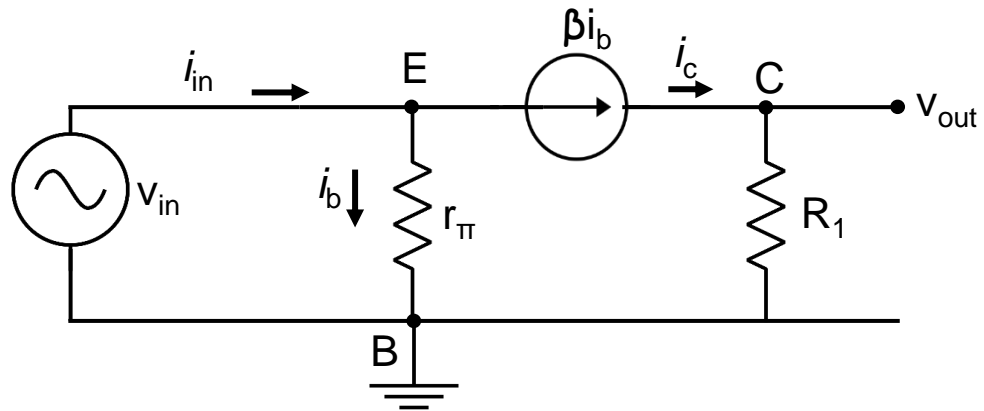


$$v_o = \beta i_b R_1 \quad v_{in} = r_{\pi} i_b \quad \frac{v_o}{v_{in}} = \frac{R_1 \beta}{r_{\pi}}$$

$$r_{in} = \frac{v_{in}}{i_{in}} = \frac{r_{\pi} i_b}{(\beta+1)i_b} = \frac{r_{\pi}}{(\beta+1)}$$

For the circuit shown, transistor parameters are  $V_A = \infty$ ,  $V_T = 25 \text{ mV}$ ,  $|V_{BE}| = 0,7 \text{ V}$ , and  $h_{fe} = h_{FE} = \beta = 100$ .

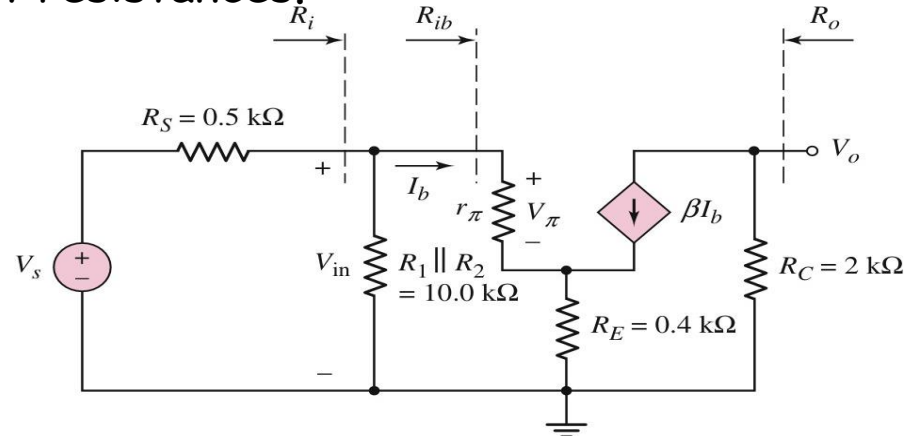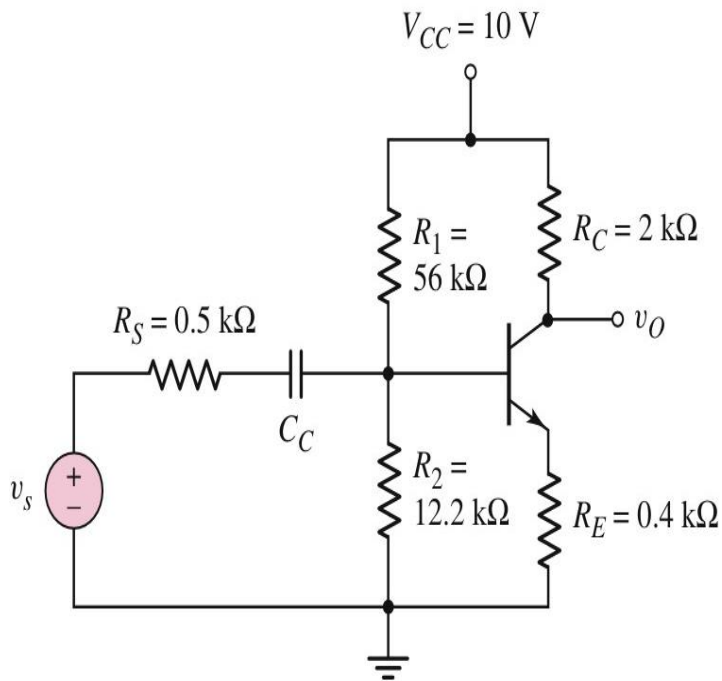- Determine DC collector currents.
- Find the small signal voltage gain  $v_o/v_{in}$ .
- Determine the input and output resistances.



Copyright © The McGraw-Hill Companies, Inc. All rights reserved. Permission is required to reproduce this content.

$$V_{in} = I_b r_{\pi} + (I_b + \beta I_b) R_E$$

$$V_o = -(\beta I_b) R_C$$

$$V_{in} = \left( \frac{R_i}{R_i + R_S} \right) V_s$$

$$A_v = \frac{V_o}{V_s} = \frac{-\beta R_C}{r_{\pi} + (1 + \beta) R_E} \left( \frac{R_i}{R_i + R_S} \right)$$


$$R_{ib} = \frac{V_{in}}{I_b} = r_{\pi} + (1 + \beta) R_E$$

$$R_i = R_1 \parallel R_2 \parallel R_{ib}$$

For the transistor shown below  $\beta = h_{fe} = h_{FE} = 200$ ,  $V_{BE} = 0.6V$ , and  $V_T = 25mV$ . All capacitors are ideal.


a) Find  $R_3$ ,  $R_4$  and  $R_5$  for  $I_C = 1mA$ ,  $V_{CE} = 4V$  and  $r_i = 10k\Omega$

b) Calculate  $v_o/v_i$ .

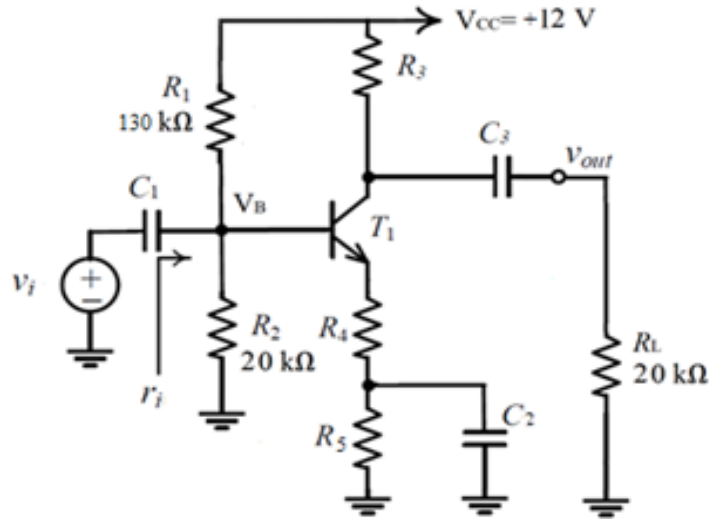

$$R_{th} = R_1 // R_2 = 17,3k$$

$$V_{th} = 1,6V$$

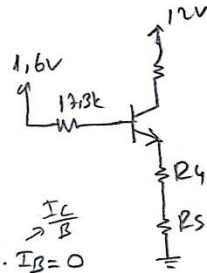

$$1,6 - 17,3k \cdot I_B - 0,6 - (R_4 + R_5) \cdot I_B = 0$$

$$1,6 - 17,3k \cdot 5\mu A - 0,6 - (R_4 + R_5) \cdot 5\mu A = 0$$

$$R_4 + R_5 = 182k$$

$$V_B = 1,51$$

$$V_E = 0,91$$


$$V_{CE} = 6V$$

$$V_C = 6,91V$$

(6)

$$12 - R_3 \cdot I_C = 4,91V$$

$$R_3 = 7k$$

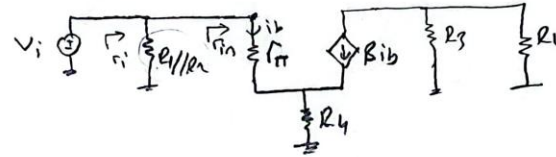

$$r_{in} = r_{\pi} + (\beta + 1) \cdot R_4$$

$$r_i = R_1 // R_2 // (r_{\pi} + (\beta + 1) \cdot R_4) \quad r_{\pi} = \frac{V_T}{I_B} = \frac{25mV}{5\mu A} = 5k$$

$$10k = 17,3k // (5k + 201 \cdot R_4)$$

$$10k = \frac{17,3k \cdot x}{17,3k + x} \rightarrow 170 \cdot 10^6 + 10k \cdot x = 17,3k \cdot x$$

$$170 \cdot 10^6 = 7,3k \cdot x$$

$$x = 23,3k$$

$$201 \cdot R_4 = 18,3k$$

$$R_4 = 91\Omega$$

$$R_5 \approx 181,9k$$

$$b) V_i = i_b \cdot r_{\pi} + (\beta + 1) \cdot i_b \cdot R_4$$

$$V_o = -\beta \cdot i_b \cdot (R_3 // R_L)$$

$$\frac{V_o}{V_i} = \frac{\beta \cdot (R_3 // R_L)}{(\beta + 1) R_4 + r_{\pi}} = \frac{200 \cdot 5,2k}{18,2k + 5k}$$

$$\frac{V_o}{V_i} \approx 44,8$$