



Node 1.

$$i_1 + i_2 = i_5 \rightarrow \frac{V_3 - V_1}{R_1} + \frac{V_2 - V_1}{R_2} - \frac{V_5}{R_5} = 0$$

Node 2

$$i_2 + i_4 = i_3 \rightarrow \frac{V_2 - V_1}{R_2} + \frac{V_2 - V_4}{R_4} - \frac{V_3 + V_2}{R_3} = 0$$

Node 3

$$i_6 = i_3 + i_1 \rightarrow \frac{V_6}{R_6} + \frac{V_3 - V_2}{R_3} + \frac{V_3 - V_1}{R_1} = 0$$

Node 4

$$i_4 + i_5 = i_6 \rightarrow \frac{V_2 - V_4}{R_4} + \frac{V_5}{R_5} - \frac{V_6}{R_6} = 0$$

$$\begin{bmatrix}
 \left(-\frac{1}{R_1} - \frac{1}{R_2}\right) & \frac{1}{R_2} & \frac{1}{R_1} & 0 & -\frac{1}{R_5} & 0 \\
 -\frac{1}{R_2} & \left(\frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_3}\right) & -\frac{1}{R_3} & 0 & 0 & 0 \\
 -\frac{1}{R_1} & -\frac{1}{R_3} & \left(\frac{1}{R_1} + \frac{1}{R_3}\right) & 0 & 0 & -\frac{1}{R_6} \\
 0 & \frac{1}{R_4} & 0 & 0 & \frac{1}{R_5} & -\frac{1}{R_6}
 \end{bmatrix}
 \begin{bmatrix}
 V_1 \\
 V_2 \\
 V_3 \\
 V_4 \\
 V_5 \\
 V_6
 \end{bmatrix}$$

$$\underline{\underline{A}} = \begin{bmatrix}
 0 \\
 \frac{e_2}{R_4} \\
 0 \\
 \frac{e_2}{R_4}
 \end{bmatrix}$$