

# Lecture 10

## Parallel Input/Output

1


### Topics

- Parallel Input/Output Interfacing
- 8086 Basic I/O Interfaces

2
 
# Input/Output Interfacing

- **Peripheral Devices** are I/O devices that exchange data with a CPU.
  - Examples : Switch, button, LED, monitor, LCD screen, printer, mouse, keyboard, disk drive, sensor, motor, audio, etc.
- **Interface Chips** are used to resolve the differences between CPU and I/O devices.



3

## I/O Interfacing Methods

- An interface chip is used as bridge between CPU and peripheral device.
- Data formats in peripherals may be different than CPU.
- Data transfer rate of peripherals are slower than CPU. A synchronization mechanism is used.
- Communication between CPU and Interface Chip is always parallel.
- Communication between Interface Chip and Peripheral Device can be either parallel or serial.
- There are two I/O interfacing methods:
  - Isolated I/O Method
  - Memory-Mapped I/O Method

4

## Isolated I/O Interfacing Method

- The  $M / \overline{IO}$  control signal of the CPU is used as a selector between Memory chips and Input/Output chips.
- Separate memory and I/O address spaces are used.
- There are distinct input and output instructions.
- Example 8086 Assembly language instructions : **IN , OUT**


5

## Using $M/\overline{IO}$ Signal for Isolated I/O Interfacing

The  $M / \overline{IO}$  control signal of the CPU is used as the Memory chip selection and also as the Input-Output Interface chip selection.

$M / \overline{IO} = 1$  means Memory chip is selected

 
$M / \overline{IO} = 0$  means Input-Output chip is selected



6
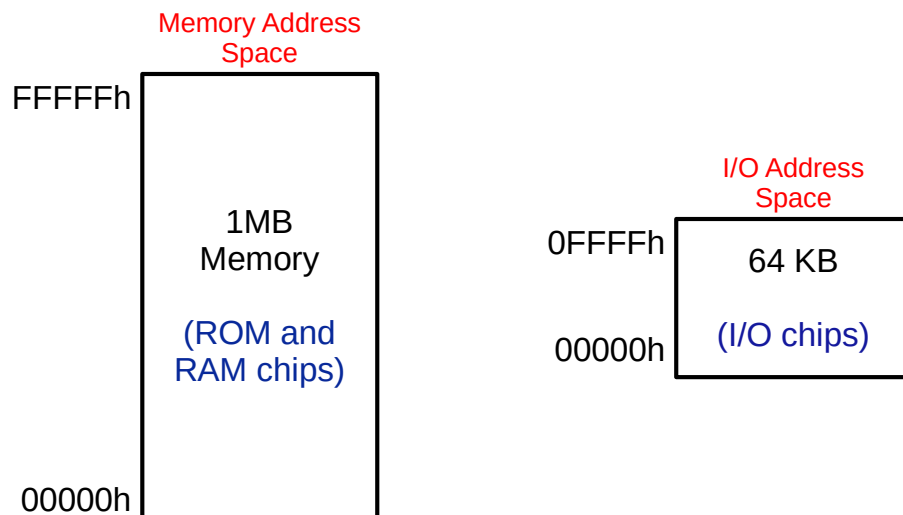
# Address Spaces in Isolated I/O Interfacing


- The entire memory address space is used by memory chips only.
- There are no reserved addresses for I/O chips in memory address space, because the I/O addresses are separated from memory addresses.



7
 
# I/O Address Space in Isolated I/O

- The bytes of data in two consecutive I/O addresses could be accessed as either byte data (8-bit), or as word data (16-bit).
- Example: I/O addresses 0000h, 0001h, 0002h, 0003h can be treated as independent byte ports 0, 1, 2 and 3.
- Or they can be treated as as word ports 0 and 1.



8


## Memory-Mapped I/O Interfacing Method

- The  $M / \overline{IO}$  control signal is not used in Memory-Mapped interfacing.
- Memory and I/O addresses share common address space.
- There are no specific input/output instructions.
- Usual memory load/store instructions are used.
- Example 8086 Assembly language instruction : **MOV**

9
 
## Address Spaces in Memory-Mapped I/O

- There is a reserved address range in the memory space for the I/O chips.
- I/O addresses are part of the main memory addresses.



10


## Differences Between Isolated I/O and Memory-mapped I/O

Isolated I/O	Memory-mapped I/O
I/O devices are treated separate from memory.	I/O devices are treated as part of memory.
Entire 1 MB address space is available for use as memory.	Entire 1 MB cannot be used as memory, since I/O devices use some addresses of memory.
Separate instructions (IN and OUT) are used for I/O.	No separate instructions are needed. The MOV instruction is used for I/O.
Data transfer takes place between I/O port and AL or AX register only.	Data transfer can take place between I/O port and any CPU register.

11
 
## Input/Output Transfer Synchronization

- The I/O interface chip has two set of signals.
- **Control signals:** Synchronize data transfer between CPU and Interface chip.
- **Handshaking signals:** Synchronize data transfer between Interface chip and I/O device.



12

# CPU and I/O Interfacing Methods

- **Programmed I/O (Polling method)**
  - CPU checks device status in a loop.
  - CPU waits for I/O module to complete operation.
  - Wastes CPU time.
- **Interrupt Driven I/O**
  - Overcomes CPU unnecessary waiting.
  - No repeated CPU checking of device.
  - I/O module interrupts when ready.
- **Direct Memory Access (DMA)**
  - Requires additional hardware module on system bus.
  - DMA controller takes over from CPU, for I/O operations.

13

## Programmed I/O (Polling method)

- **Input Operations :**  
CPU checks a status bit of the interface chip, to find out whether the interface has received new data from input device.
- **Output Operations :**  
CPU checks a status bit of the interface chip, to find out whether it can send new data to interface chip.

14


# Interrupt Driven I/O

- **Input Operations :**  
Interface chip interrupts the CPU, whenever it has received new data from input device.
- **Output Operations :**  
Interface chip interrupts the CPU, whenever it can accept new data from microprocessor.

15
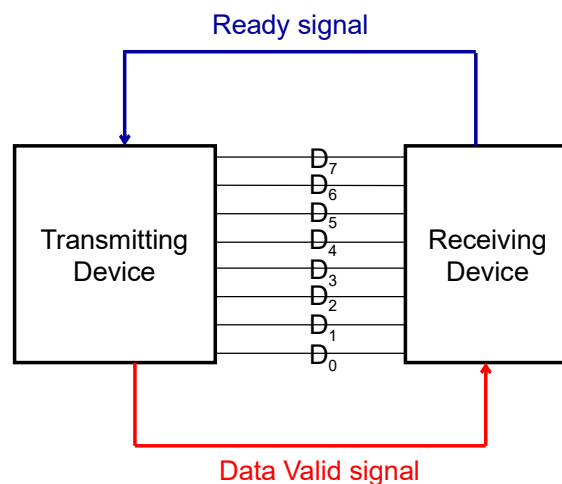
# Parallel Communication

- In parallel communication, all bits are transferred at the same time.
- Each bit is transferred along its own line.
- In addition to eight parallel data lines, other lines are used to read status information and send control signals.




16


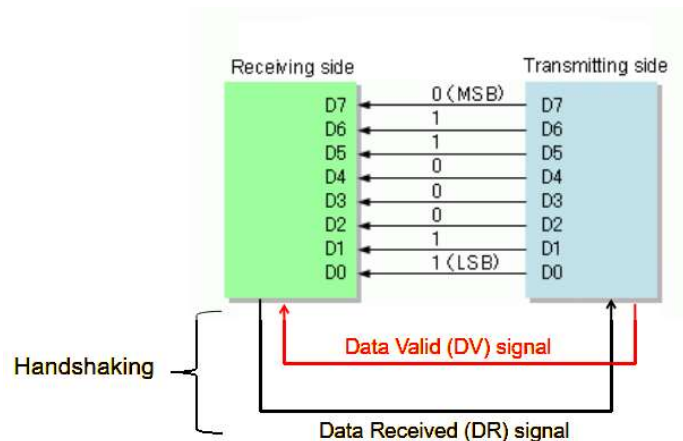
## Example: Synchronization of two parallel devices

- **Transmitter** and **receiver** interfaces use handshaking protocol.
- **Transmitter** initiates 2-wire handshaking
  - DV low indicates new data is available.
  - DR low indicates that receiver has read the data.




17

## Basic Parallel Input Interface

- The basic input device (to the microprocessor) is a set of tri-state buffers.
- When data is coming in by way of a data bus (either from port or memory) it must come in through a three-state buffer.
- **Tri-state buffer** chips can be used as input interface. (Example chip: 74244)
- Output pins of **interface** are connected to **Data Bus** of CPU (as the inputs of CPU).
- Input pins of **interface** are connected to an input device.

18

# Basic Parallel Input Interface

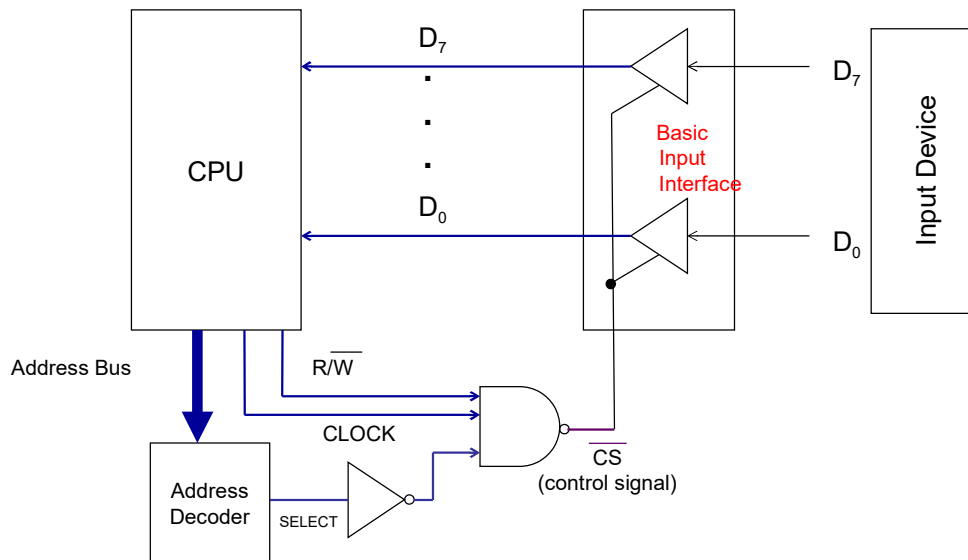


19

## Basic Input Interface Timing Diagram

- 1) Address is placed on address bus at the falling edge of clock.



 - 2) Address is decoded, in order to form the CS (Chip Select) (Enable) signal.



- 3)  $\text{NAND} \{ \text{CLK}, \text{M}/\overline{\text{IO}}, \overline{\text{READ}} \}$  is applied, in order to form CS signal.




20

## Basic Parallel Output Interface

- The basic output device (from the microprocessor) is a set of latches.
- Since the data provided by the CPU to an output port is on the system data bus for a limited amount of time (nano seconds), it must be latched before it is lost.
- **D-Latches** (Data Latches) can be used as output interface. (Example chip: 74374)
- Inputs of **interface** are connected to the **Data Bus** of CPU.
- Outputs of **interface** are connected to an output device.

21

## Basic Parallel Output Interface

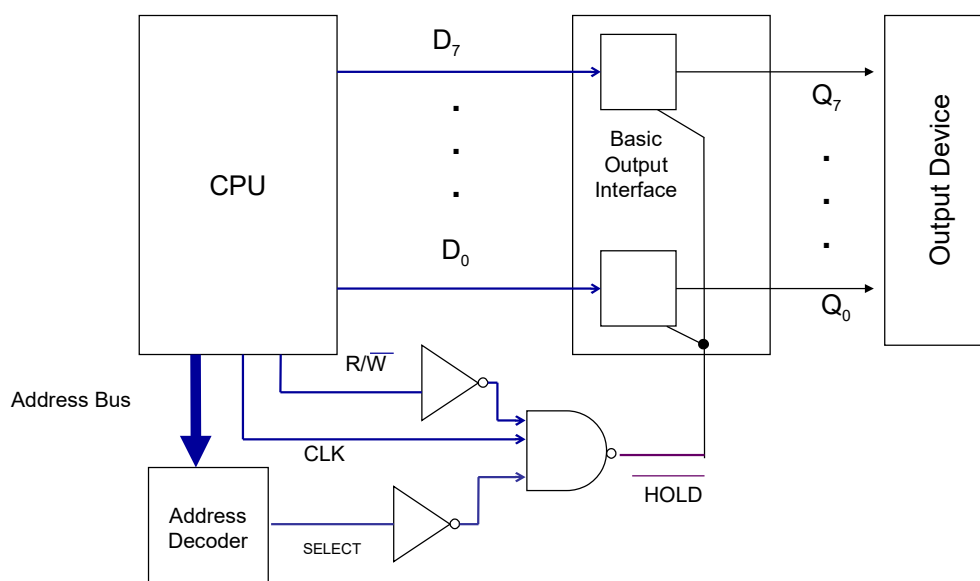

22

# Basic Output Interface Timing Diagram


- 1) Address is placed on address bus at the falling edge of clock.



- 2) Data is placed on the data bus.



 - 3) Address is decoded, in order to form the Select signal.
- 4)  $\text{NAND}\{\text{CLK}, \text{SELECT}, \text{R}/\overline{\text{W}}\}$  is applied, in order to form HOLD.



23

## Topics


- Parallel Input/Output Interfacing
- 8086 Basic I/O Interfaces

24
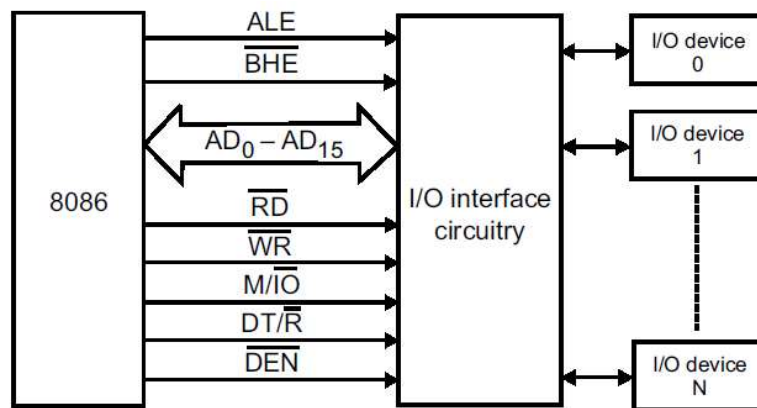
# 8086 Minimum Mode I/O Interface

The I/O interface circuitry performs the following tasks.

- Selecting the particular I/O port
- Synchronizing data transfer
- Writing the output data
- Reading the input data



25

## Parallel I/O Interface Chips used with 8086 CPU

Chip Number	Chip Name	I/O Direction
<b>74373, 74374</b>	Latch	Output only
<b>74244, 74245</b>	Buffer	Input / Output
<b>8255</b>	Programmable Peripheral Interface	Input / Output

26

# 8086 Assembly Instructions for I/O

- The 8086 CPU can access data from I/O ports as well as from the memory.
- 8086 can be used with isolated I/O, or memory-mapped I/O interface methods.
- In isolated method, the IN and OUT instructions are used between CPU and I/O interface for data transfers.
- Any I/O port in the interface chip can be used for either 8-bit or 16-bit data transfer.

Addressing Method	Port Address	Input Instruction	Output Instruction	Description
Direct	Fixed	IN AL, port	OUT port, AL	Port addresses between 00-FF are written with instruction.
		IN AX, port	OUT port, AX	
Indirect	Variable	IN AL, DX	OUT DX, AL	Port addresses between 100h-FFFFh should be loaded to DX register first.
		IN AX, DX	OUT DX, AX	

27

## Input / Output Ports

I/O devices are connect to the CPU through the I/O interface chip ports.

Ports are:

- Registers (part of the I/O interface chip)
- Can be 8, 16, or 32 bits
- Addressed in the range 0000-FFFFh
- Accessed with Assembly instructions IN, OUT

28

# IN Instruction

- The IN instruction copies data from a peripheral device port to the AL or AX register.
- If an 8-bit port is read, the data will go to AL.
- If a 16-bit port is read, the data will go to AX.
- IN instruction does not change any flag.
- IN instruction has two formats, fixed port and variable port.
- **FIXED PORT FORMAT:** The 8-bit address of a port is specified directly in the instruction. Up to 256 possible ports can be addressed.

General Syntax

**IN Accumulator, PortNumber**

## Examples: 8 bit fixed port address

**IN AL, 0C8h**      Input a byte from port C8h to AL

**IN AX, 34h**      Input a word from port 34h to AX

29

# IN Instruction

- **VARIABLE-PORT FORMAT:** The port address is loaded into the DX register (Indirect Addressing) before the IN instruction.
- Since DX is a 16-bit register, the port address can be any number between 0000H and FFFFH.
- Therefore, up to 65,536 ports are addressable.
- The variable-port IN instruction has advantage that the port address can be computed, or dynamically determined in the program.

## Examples: 16 bit variable port address

**MOV DX, 0FF78h**      Initialize DX to point to port  
**IN AL, DX**      Input a byte from 8-bit port FF78h to AL  
**IN AX, DX**      Input a word from 16-bit port FF78h to AX

30


# Input Buffering

- Input devices must be isolated from the system data bus.
- Otherwise unwanted data may be transferred on to the data bus.
- When data comes in from a port or memory, data must be input through a tri-state buffer.
- Tri-state buffers are used which provide isolation as well as strengthen the signal.
- Example: Interfacing the input devices such as switches, or buttons require buffers.

31

## Example: Address Decoding Circuit for Input Port 9Ch

Example instruction:  
**IN AL, 9Ch**

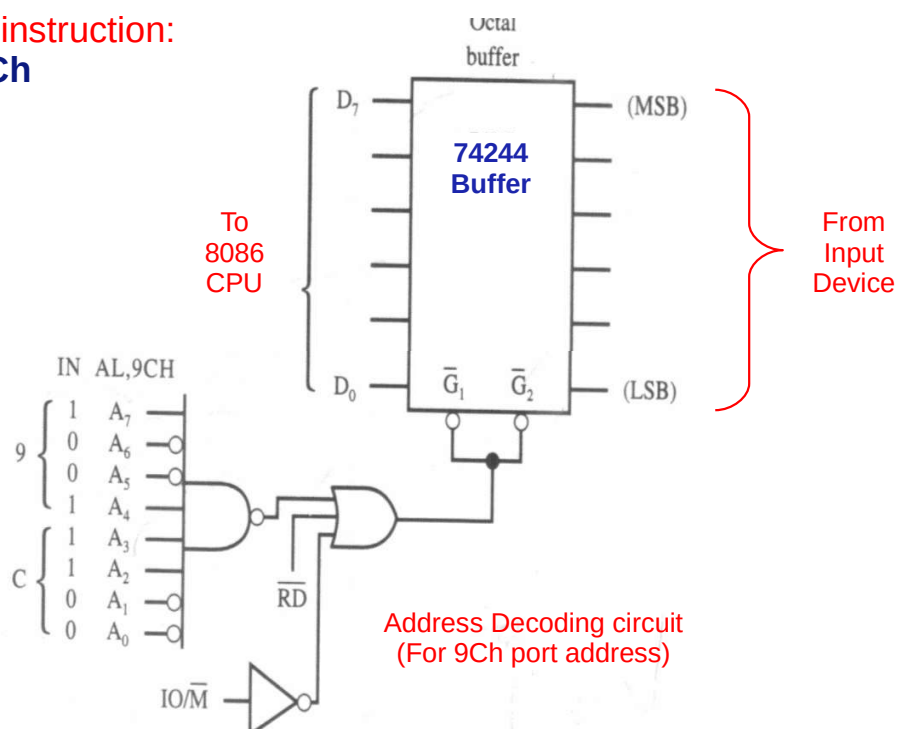

32



# OUT Instruction

- The OUT instruction copies a byte from AL or a word from AX to the specified port.
- OUT instruction does not change any flag.
- Similarly to IN instruction, the OUT instruction has two forms, fixed port and variable port.
- **FIXED PORT FORMAT:** The 8-bit port address is specified directly in the instruction.
- Up to 256 possible ports can be addressed.

General Syntax

**OUT PortNumber, Accumulator**

## Examples: 8 bit fixed port address

**OUT 3Bh, AL** Copy the content of AL to port 3Bh

**OUT 2Ch, AX** Copy the content of AX to port 2Ch

33

# OUT Instruction

- **VARIABLE PORT FORMAT:** The OUT instruction copies , content (data) of AL or AX to the port at an address contained in DX.
- The DX register must be loaded with the desired port address, before this form of the OUT instruction is used.

## Examples: 16 bit variable port address

**MOV DX, 0FFF8h** Load a port address (16 bit) in DX

**OUT DX, AL** Copy content of AL to port FFF8h

**OUT DX, AX** Copy content of AX to port FFF8h

34


# Output Latching

- When data is sent out by CPU, the data on the data bus must be latched.
- Memory chips have internal latches to store data.
- A latching system must be designed for I/O ports.
- Data provided by the processor is available only for short period of time.
- Data must be latched, otherwise it will be lost.
- Example: Interfacing output devices like LEDs require latches.

35

## Example: Address Decoding Circuit for Output Port 9Ch

Example instruction:  
**OUT 9Ch, AL**

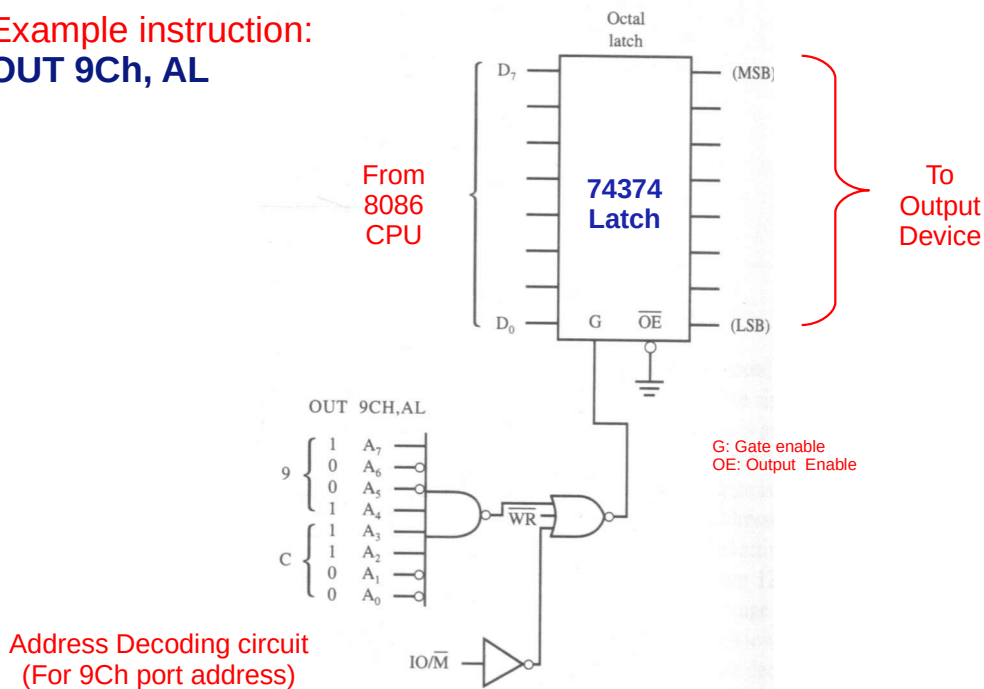

36


## Example: Output Interface with 74374 Latch chip

- The **74374** chip is a three-state Octal (8 bit) D-type Latch.
- It can be used for output.
- Suppose **8 LEDs** (Light Emitting Diodes) are connected to the latch chip.
- The latch chip is connected to the 8086 CPU.
- Isolated I/O interface method will be used.
- Suppose the fixed port address of the 74374 latch chip is 00004h.
- Block diagram of 74374 chip and the LEDs are shown below.

37
 
## Application Example1: LEDs Blinking Program


- 74374 Latch chip is used to drive 8 LEDs (supplying the +5V).
- Resistors are required for limiting the electric current on each LED.



38
 
# LEDs Blinking (Flashing) Program

- Write an Assembly program that turns all LEDS on and off continuously in endless loop.
- There should be some waiting time between each on and off operation.



39

## LEDs Blinking Program

```
; Program for Blinking (Flashing) all LEDs.
; (With 74374 Latch chip)
; In Emu8086, all 12 traffic lights are turned on and off.

.model small
.code
MainDongu:      ; Endless main loop
mov ax, 0FFFh   ; Turn on all 12 LEDs
out 4, ax       ; Fixed address of output port is 4 (in Emu8086)

; Wait for 1 second.
mov cx, 255
bekle1: loop bekle1 ; CX is implicit counter operand

mov ax, 0       ; Turn off all 12 LEDs
out 4, ax       ; Output port address is 4

; Wait for 1 second again.
mov cx, 255
bekle2: loop bekle2 ; CX is implicit counter operand

JMP MainDongu   ; Goto endless loop
END             ; End of file
```

40

## Testing the LEDs Blinking Program (Using Emu8086 Emulator)

- Run the LEDs program in Emu8086 emulator.
- Open the Virtual Devices --> Traffic\_Lights.exe program.
- By default, Emu8086 uses the **port address at 4** for LED outputs.
- Emu8086 enumerates the 12 LEDs as 0,1,2,3,...,A,B.
- The following is the emulation screen for the LED blinking application, by using the 12 traffic lights as LEDs.



41


## Example: Input Interface with 74244 Data Buffer chip

- The **74244** chip is a Octal (8 bit) 3-state Buffer (Line Driver / Line Receiver).
- The block diagram below shows an example design with the connection signals and the address decoding circuit.
- Suppose **8 Buttons** are connected to the 74244 data buffer chip.
- The buffer chip is connected to 8086 CPU.
- Suppose the port address of the buffer chip will be stored in DX register as **0001h**.
- Block diagram of 74244 chip and the buttons are shown below.

42
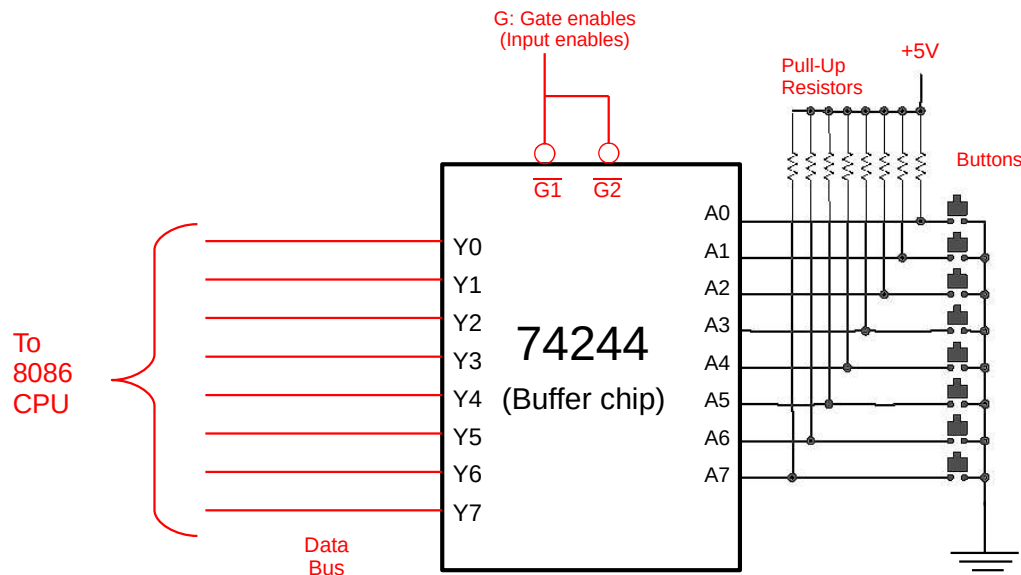
## Application Example2: Buttons Input Program


- The Buffer chip has 8 inputs (A1-A8), and 8 outputs (Y1-Y8).
- Each of the  $\overline{G1}$  and  $\overline{G2}$  pins controls 4 input bits.





43
 
## Switch Bounce Problem

- When a switch (or button) is closed, it may cause multiple ON and OFF signals lasting several milliseconds.
- The multiple switch closing/opening problem is called as Switch Bounce problem. (Also called as Contact Noise problem)
- **Software solution:** Detect the first key-press, wait for a short time, then read again.
- **Hardware solution:** Use a Pull-Up or Pull-Down resistor with the switch (or button).



  
If switch is open, the output is 0V (Low, Logic 0)  
If switch is closed, the output is 5V (High, Logic 1)



44
 
## Switch with Pull-Up Resistor


- The pull-up resistor pulls a pin of a chip up to a HIGH state.
- Input of the buffer chip is normally HIGH.
- When the switch is closed, input of the chip drops to LOW.



45
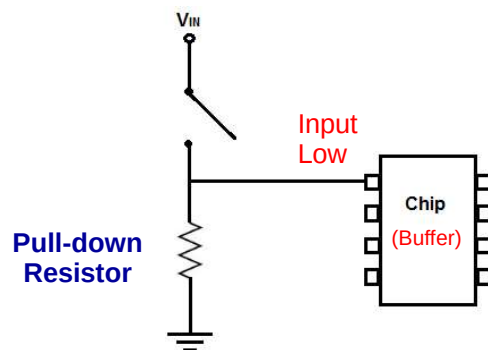
## Switch with Pull-Down Resistor

- It is the opposite of Pull-Up resistor.
- The pull-down resistor pulls a pin of a chip down to a LOW state.
- Input of the buffer chip is normally LOW.
- When the switch is closed, input of the chip becomes HIGH.



46

## Buttons Input Program

- Write an Assembly program to continuously read the 8 buttons connected to the 74244 buffer chip.
- Program should stop when user presses any of the buttons.

```
; Program for reading Buttons.
; ( With 74244 Buffer chip )
.model small
.code

mov dx, 0001h    ; Address of input port is 01h.

Dongu:           ; Endless loop
in AL, dx        ; Read all 8 button inputs
cmp AL, 0FFh     ; FF means all inputs are high (No button is pressed).
                ; When a button is pressed, its input drops to low.
JNE Son          ; Goto label if not equal (Any button is pressed)
JMP Dongu        ; Go to endless loop (No button is pressed).

Son:
.EXIT           ;Program stops
END            ;End of file
```