



$$i_1 = \frac{-10}{15k\Omega} = -10^{-3}A$$

$$V_a = -i_1 \cdot 6k\Omega$$

$$V_a = -6V$$

$$\frac{-V_0}{9} = i_2$$

$$\frac{V_0}{i_2} = -9V$$