



ELK 331E/331



Power Electronic Circuits/Güç Elektroniği Devreleri

The Three Phase Half-Wave Uncontrolled Rectifier

Üç Fazlı Yarım Dalga Kontrolsüz Doğrultucular

Assoc. Prof. Dr. Mehmet Onur GÜLBAHÇE

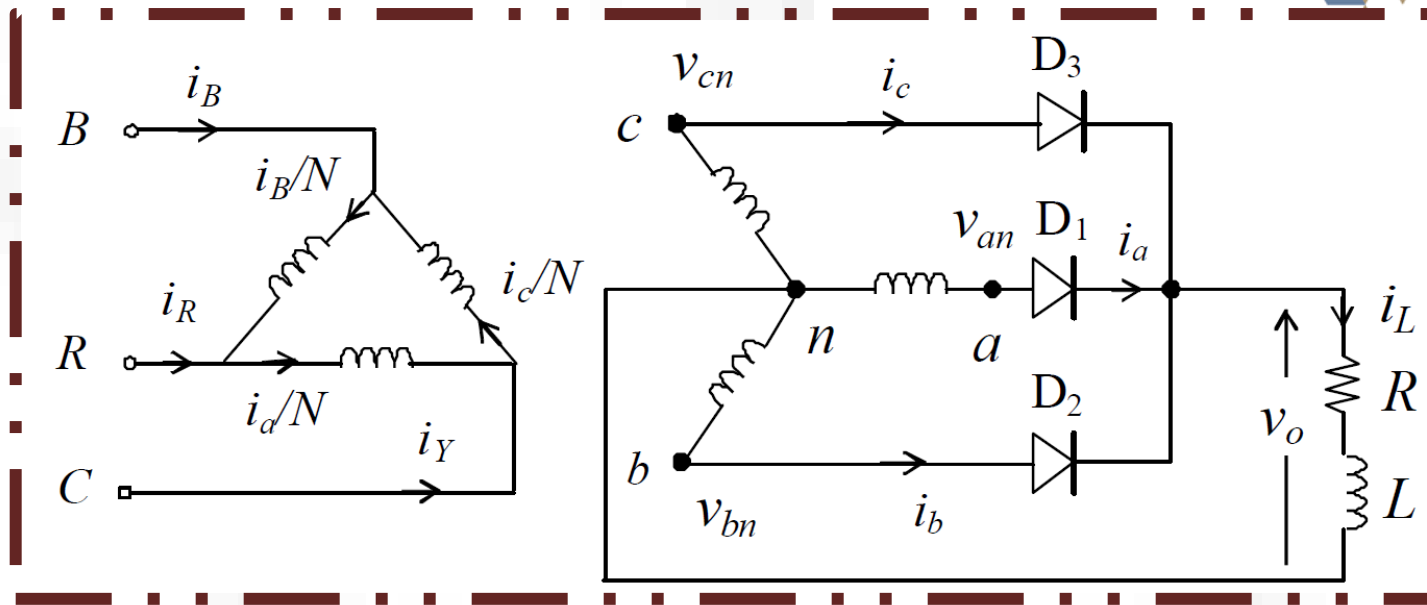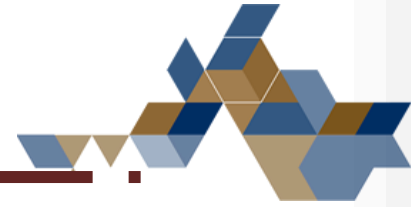Uncontrolled Three-phase Half-wave Rectifier



❖ The diode in a particular phase conducts during the period when the voltage on that phase is higher than that on the other two phases.

❖ The conduction angle of each diode is $2\pi/3$

❖ Applications:

- Battery charging
- Electrolytic processes
- Simple DC supply circuits where low cost is prioritized over performance


Advantages:

- Simple design and easy to implement
- Fewer components (only three diodes)


Disadvantages:

- High ripple in the output voltage
- Limited to low and moderate power app. due to the neutral return path requirement
- Diodes must handle high peak currents

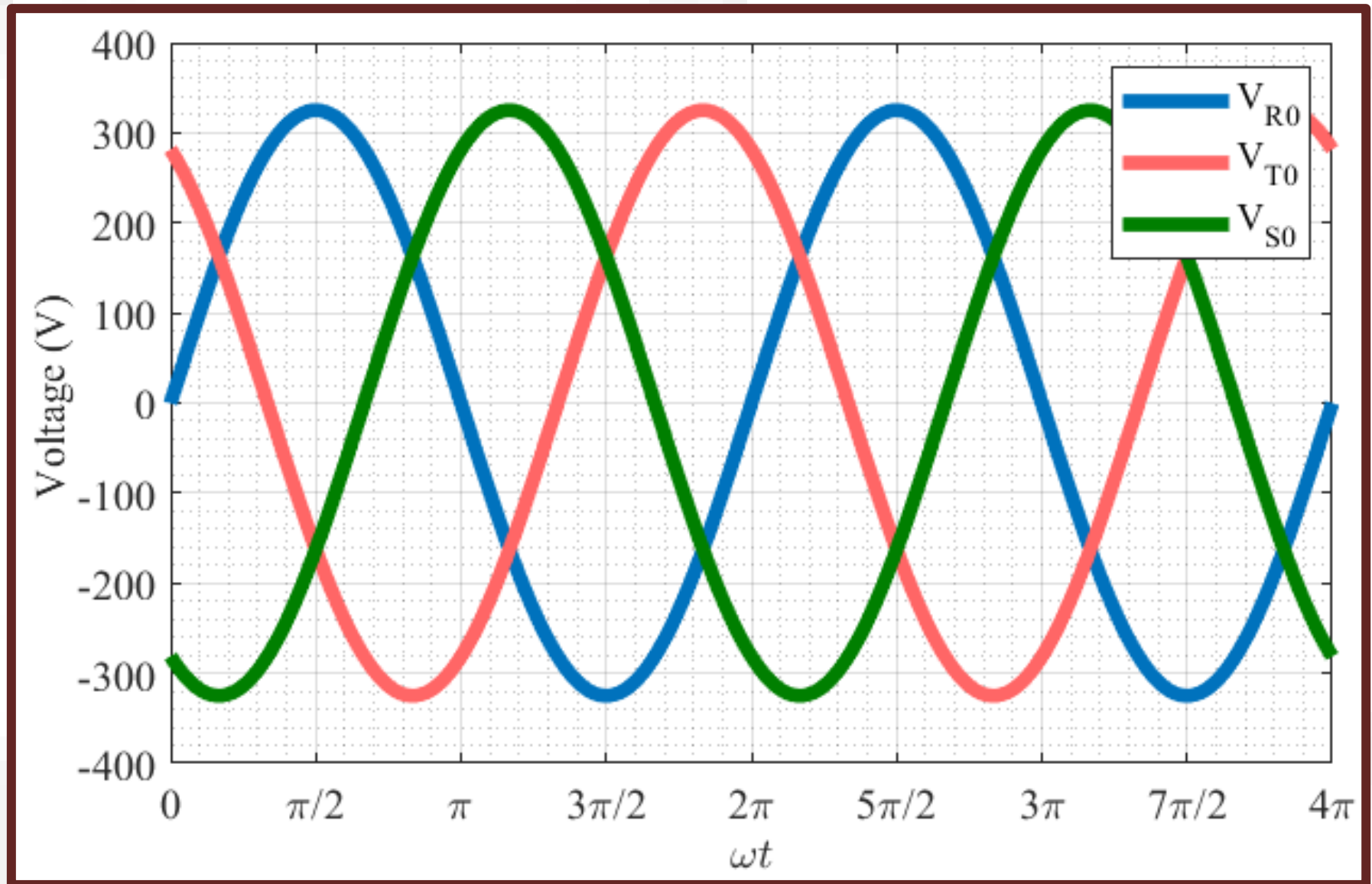
Uncontrolled Three-phase Half-wave Rectifier





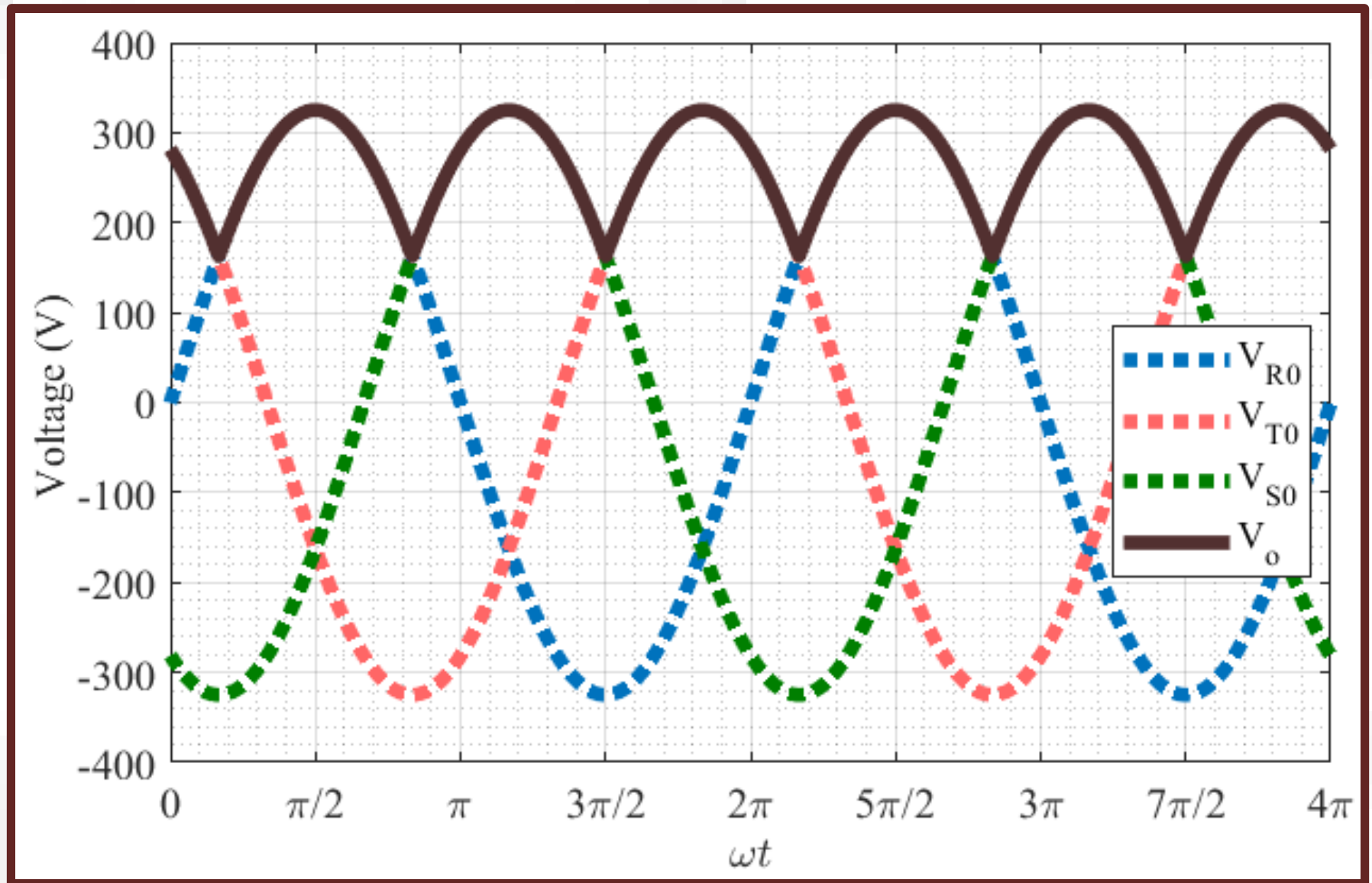
Uncontrolled Three-phase Half-wave Rectifier



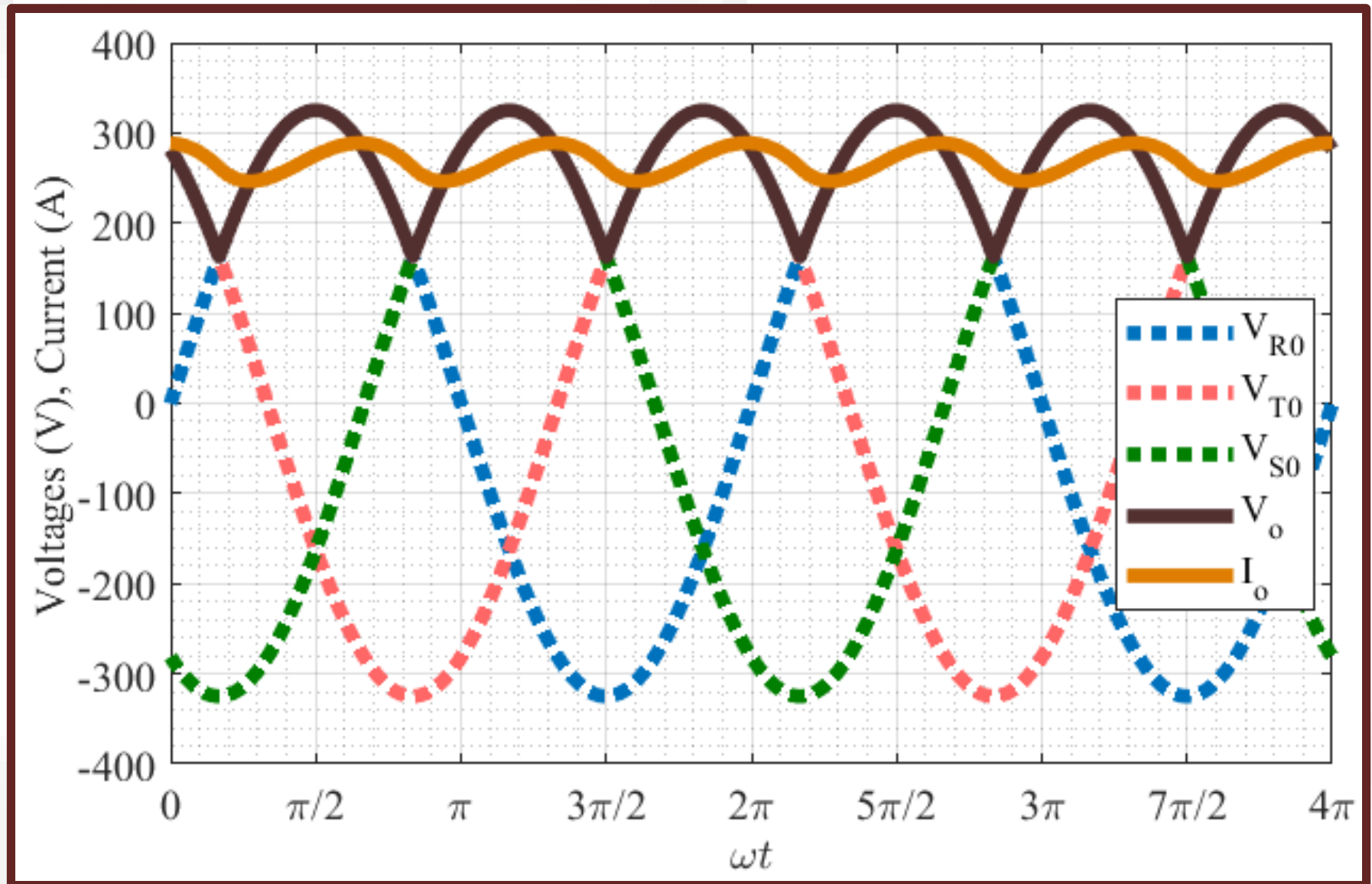
Uncontrolled Three-phase Half-wave Rectifier



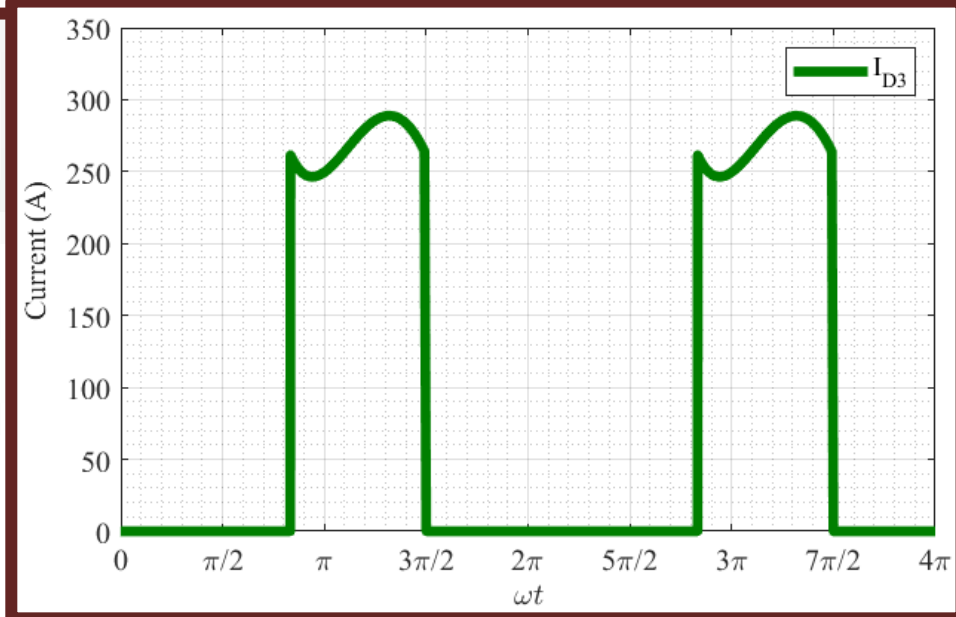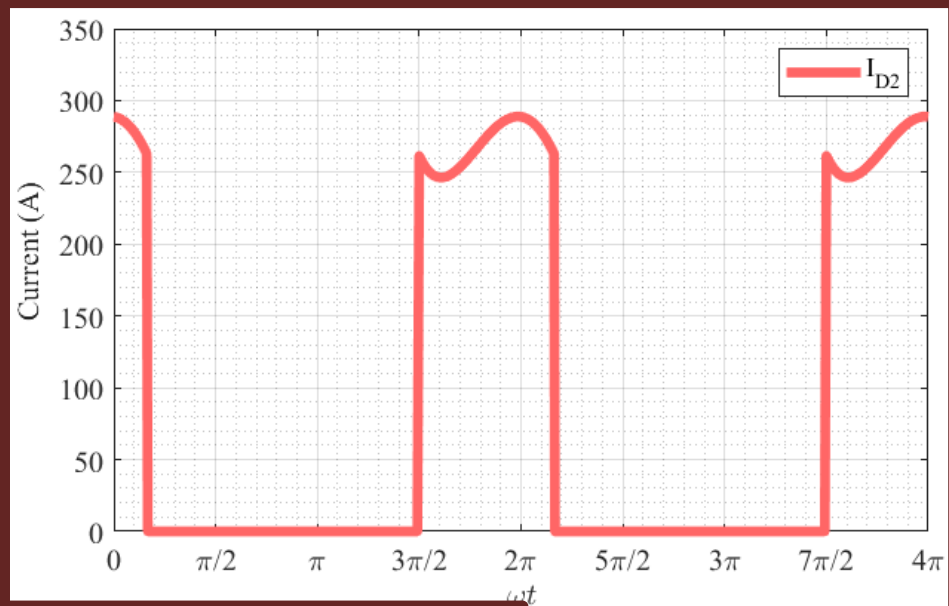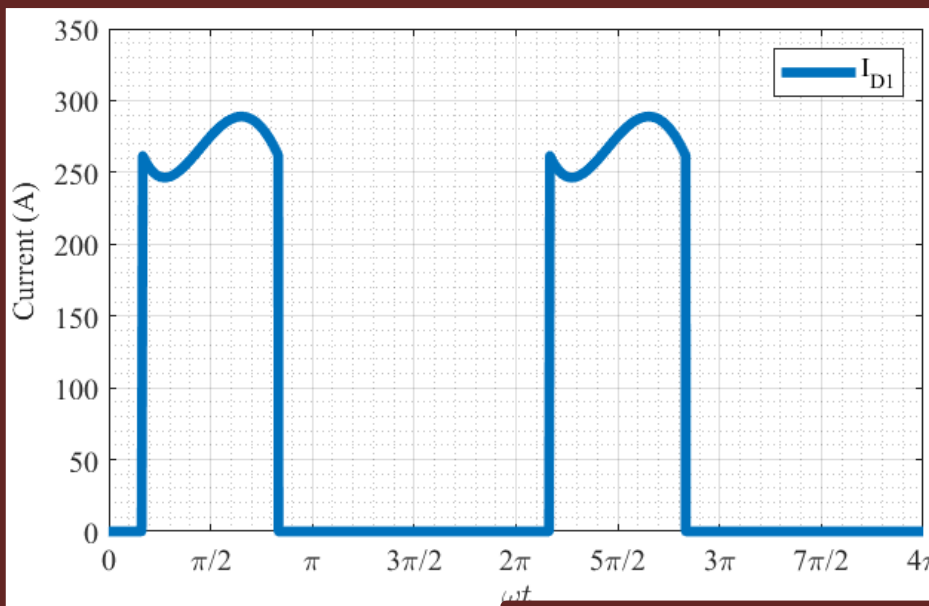Uncontrolled Three-phase Half-wave Rectifier




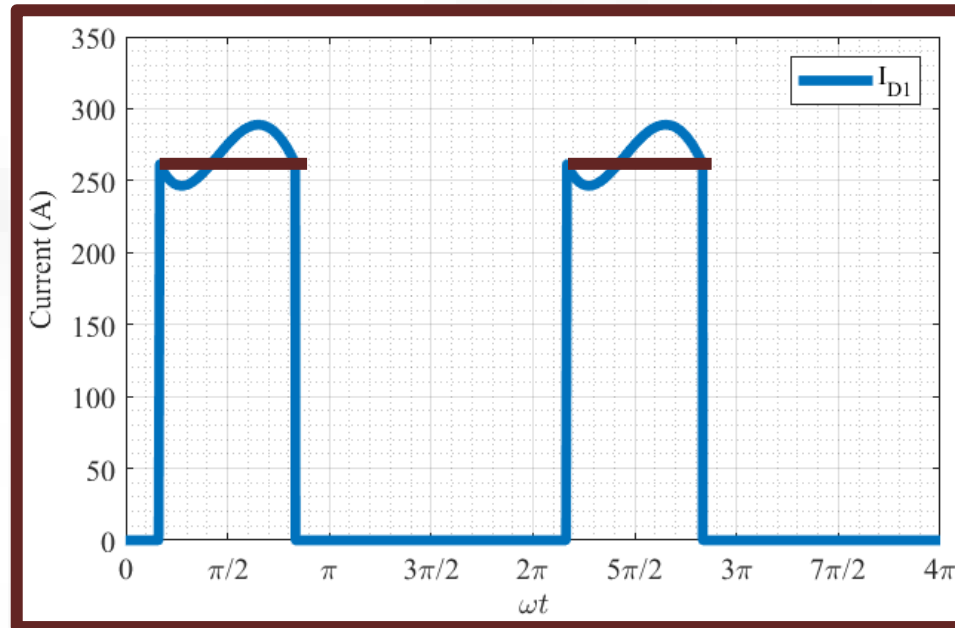Uncontrolled Three-phase Half-wave Rectifier




If we assume that the load is highly inductive, the load current can be taken to be smooth and ripple free.

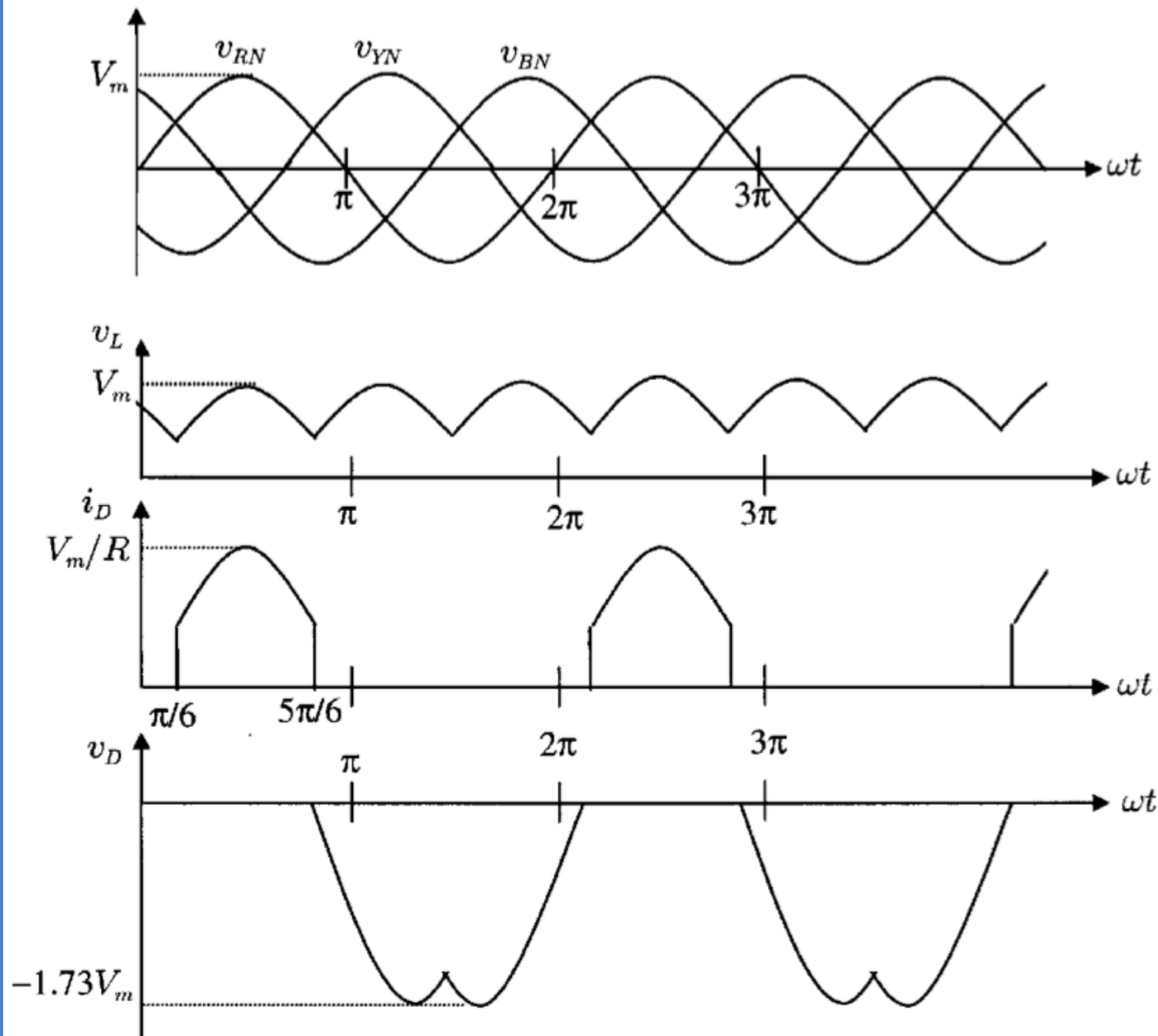Uncontrolled Three-phase Half-wave Rectifier



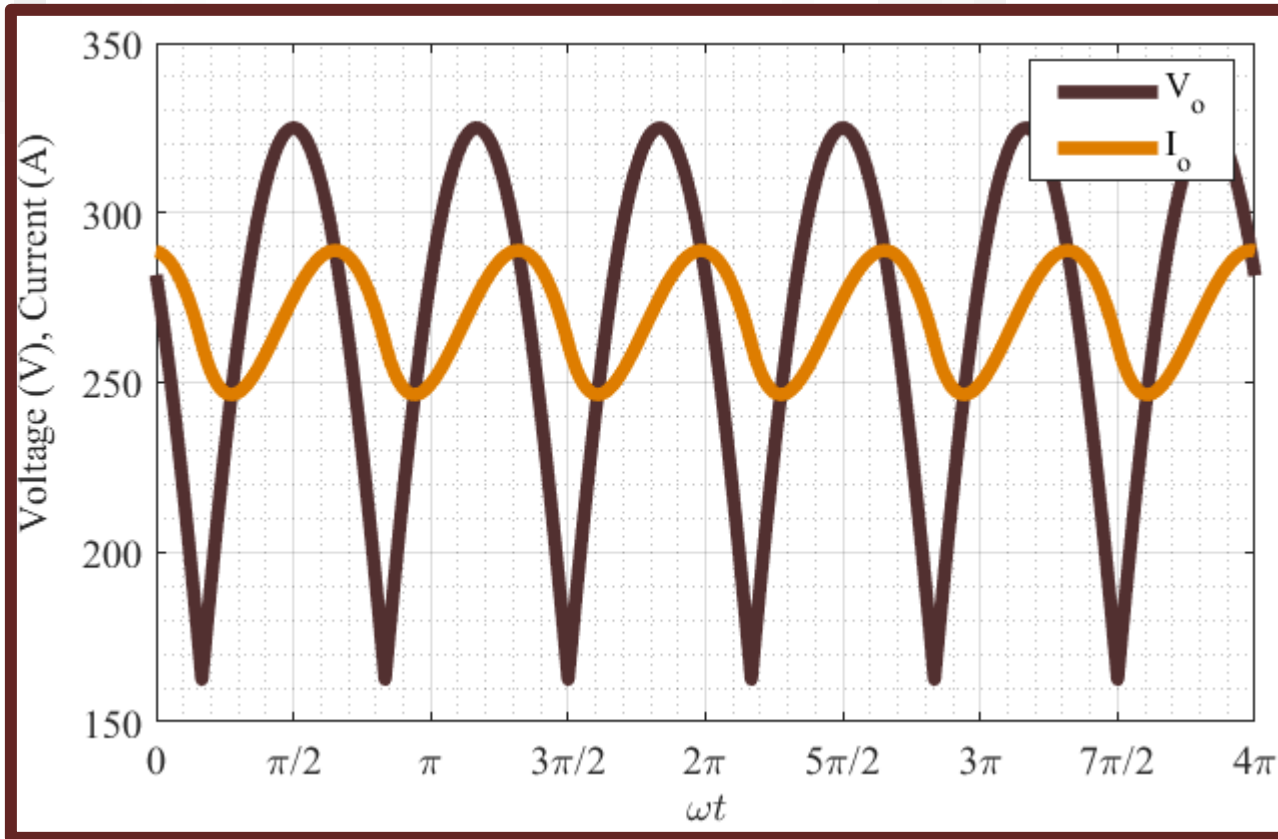Uncontrolled Three-phase Half-wave Rectifier




$$V_{R0} = V_m \sin(\omega t)$$

$$V_{S0} = V_m \sin(\omega t - \frac{2\pi}{3})$$

$$V_{T0} = V_m \sin(\omega t - \frac{4\pi}{3})$$

$$V_o (AVG) = \frac{1}{2\pi/3} \int_{\pi/6}^{\frac{5\pi}{6}} V_m \sin(\omega t) d(\omega t) = \frac{3\sqrt{3}V_m}{2\pi} = 0.827V_m$$

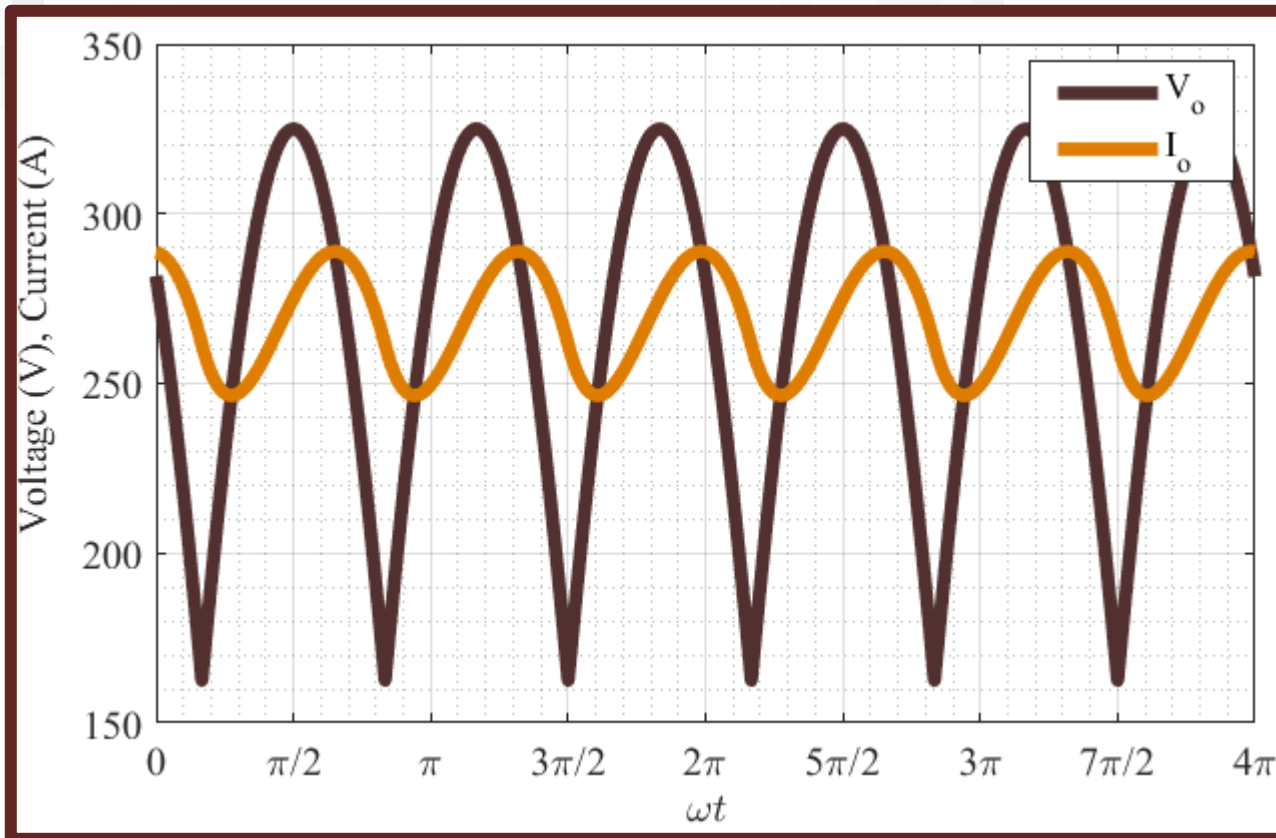
Uncontrolled Three-phase Half-wave Rectifier



$$I_o (AVG) = \frac{V_o (AVG)}{R}$$

$$V_o (RMS) = \sqrt{\frac{1}{2\pi/3} \int_{\pi/6}^{5\pi/6} [V_m \sin(\omega t)]^2 d(\omega t)} = 0.84V_m$$

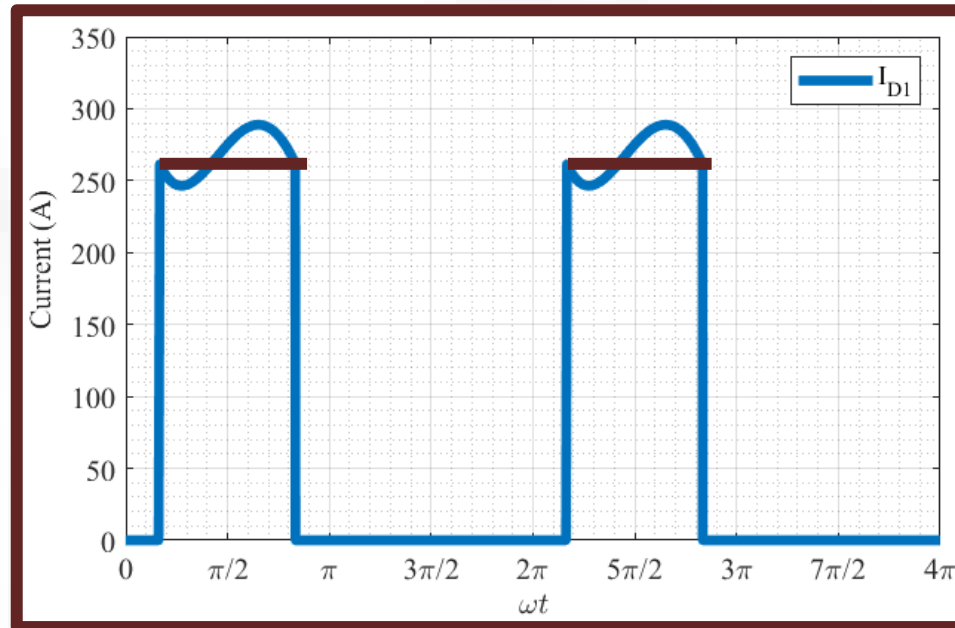Uncontrolled Three-phase Half-wave Rectifier



The rms current in each transformer secondary winding can also be found as:

$$I_s = I_m \sqrt{\frac{1}{2\pi} \left(\frac{\pi}{3} + \frac{\sqrt{3}}{4} \right)} = 0.485 I_m \quad I_m = \frac{V_m}{R}$$