
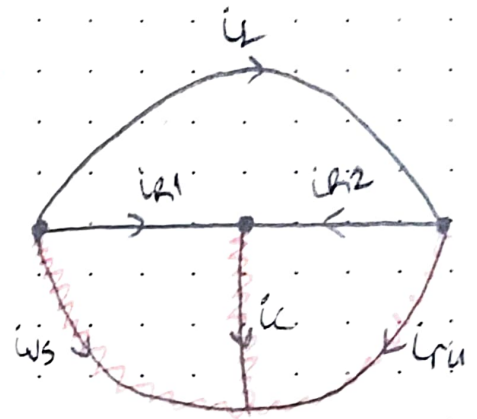


HW 3

Sena ERSOY
06020024
Sena

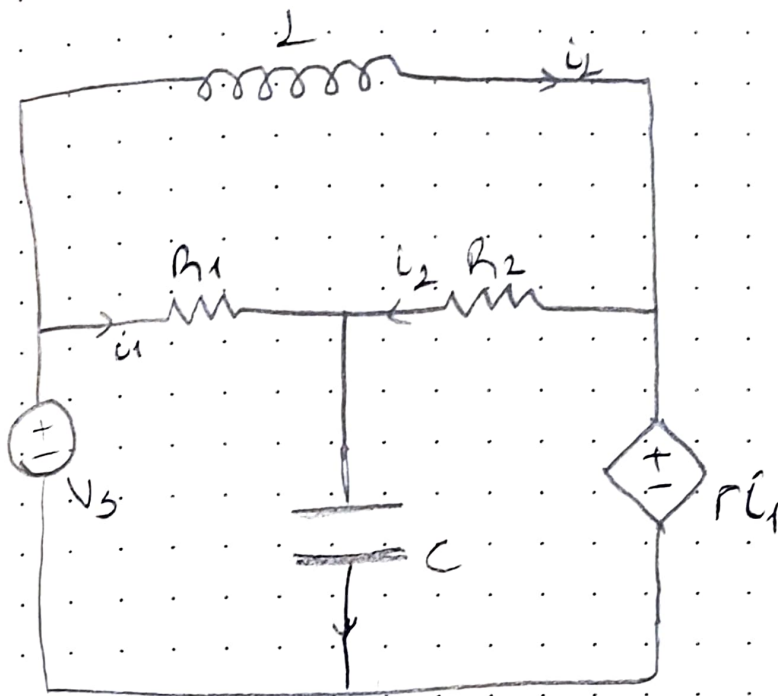

state variables:

$$[V_C, i_L]$$

$$\textcircled{1} i_L + i_2 - i_C = 0$$

$$i_C = C \frac{dV_C}{dt}, i_1 = \frac{V_3 - V_C}{R_1}, i_2 = \frac{r i_1 - V_C}{R_2}$$

$$\frac{V_3 - V_C}{C R_1} + \frac{r i_1 - V_C}{C R_2} = \frac{dV_C}{dt}$$

$$\frac{1}{C R_1} V_3 - \frac{R_2}{C R_1 R_2} V_C + \frac{r}{C R_1 R_2} V_3 - \frac{r}{C R_1 R_2} V_C - \frac{R_1}{C R_1 R_2} V_C = \frac{dV_C}{dt}$$

$$-\frac{(R_1 + R_2 + r)}{C R_1 R_2} V_C + \frac{R_2 + r}{C R_1 R_2} = \frac{dV_C}{dt}$$

$$\textcircled{2} V_L + V_{R2} - V_{A1} = 0$$


$$L \frac{di_L}{dt} = - (r i_1 - V_C) + V_3 - V_C$$

$$\frac{di_2}{dt} = -\frac{1}{L} \left(\frac{r(V_S - V_C)}{R_1} - V_C \right) + \frac{V_S - V_C}{L}$$

$$\frac{di_2}{dt} = -\frac{r V_S}{L R_1} + \frac{r V_C}{L R_1} + \cancel{\frac{V_C}{L}} + \frac{V_S}{L} - \cancel{\frac{V_C}{L}}$$

$$\frac{di_2}{dt} = \frac{R_1 - r}{L R_1} V_S + \frac{r}{L R_1} V_C$$
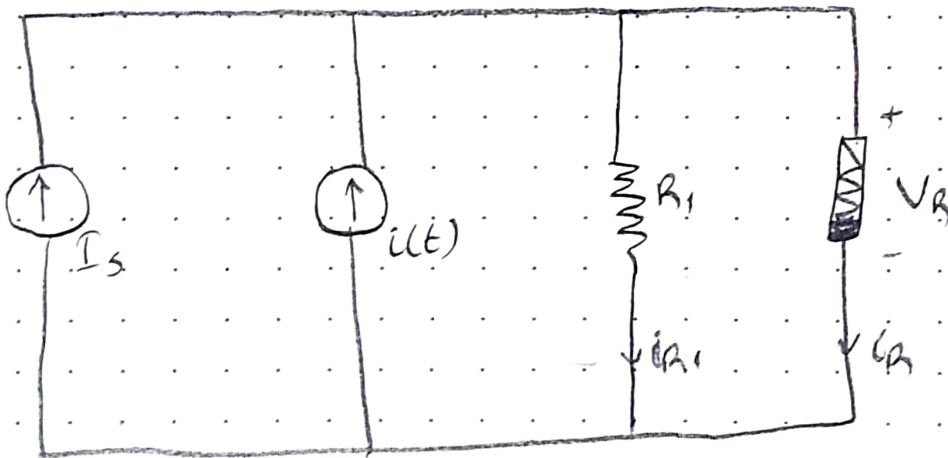
$$\begin{bmatrix} \dot{V}_C \\ \dot{i}_2 \end{bmatrix} = \begin{bmatrix} -\frac{(R_1 + R_2 + r)}{C R_1 R_2} & 0 \\ \frac{r}{L R_1} & 0 \end{bmatrix} \begin{bmatrix} V_C \\ i_2 \end{bmatrix} + \begin{bmatrix} \frac{R_2 + r}{C R_1 R_2} \\ \frac{R_1 - r}{L R_1} \end{bmatrix} V_S$$



$$R_1 = 1/2 \Omega$$

$$I_S = 8 \text{ A}$$

$$i(t) = 0.1 \sin(10t)$$


$$i_R = \sqrt{V_R^2 + V_{R1}^2}$$

First, DC Analysis

$$I_S - i_{R1} = i_R \quad i_{R1} = \frac{V_R}{1/2} = 2 V_R$$

$$8 - 2 V_R = i_R$$

Sen ERSOY
01020034
SMA

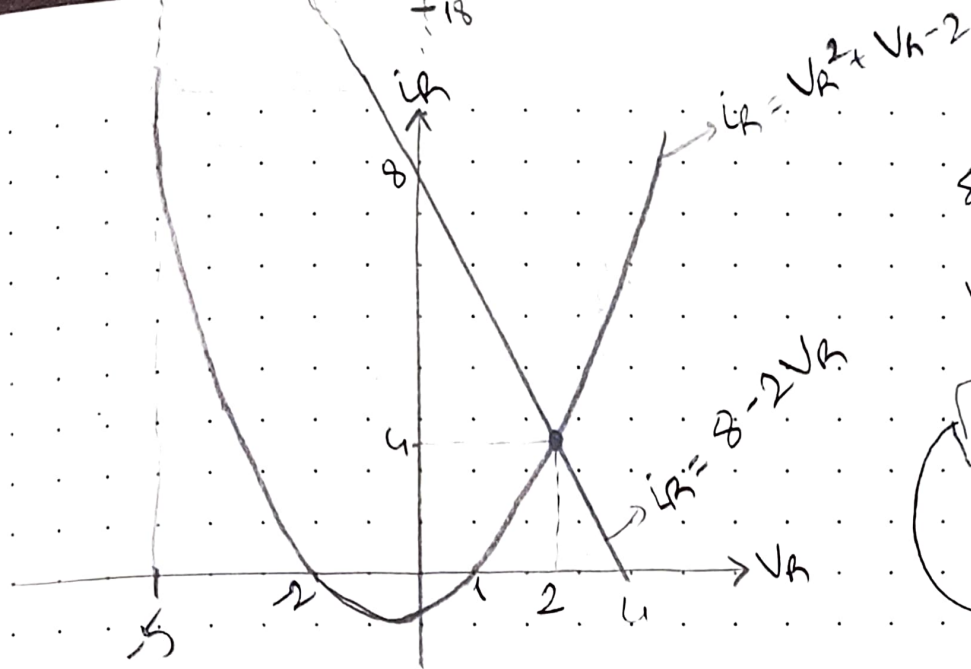

$$8 - 2V_R = V_R^2 + V_R - 2$$

$$V_R^2 + 3V_R - 10 = 0$$

$$V_R = -5, i_R = 18$$

$$V_R = 2, i_R = 4$$

neglected due to small signal

$$1/R_{Q1} = \left. \frac{di_R}{dV_R} \right|_{V_R=2} = 2V_R + 1 \Big|_2 = 5, \quad R_{Q1} = \frac{1}{5}$$


$$1/R_{Q2} = \left. \frac{di_R}{dV_R} \right|_{V_R=-5} = 2V_R + 1 \Big|_{-5} = -9, \quad R_{Q2} = -\frac{1}{9}$$

Second, small signal analysis

$$\tilde{V}(t) = 0.1 \sin(10t) \cdot R_{Q1} // \frac{1}{2} = \frac{0.1}{7} \sin(10t)$$

$$\tilde{i}(t) = 0.1 \sin(10t) - \frac{\tilde{V}(t)}{1/2} = \frac{0.5}{7} \sin(10t)$$
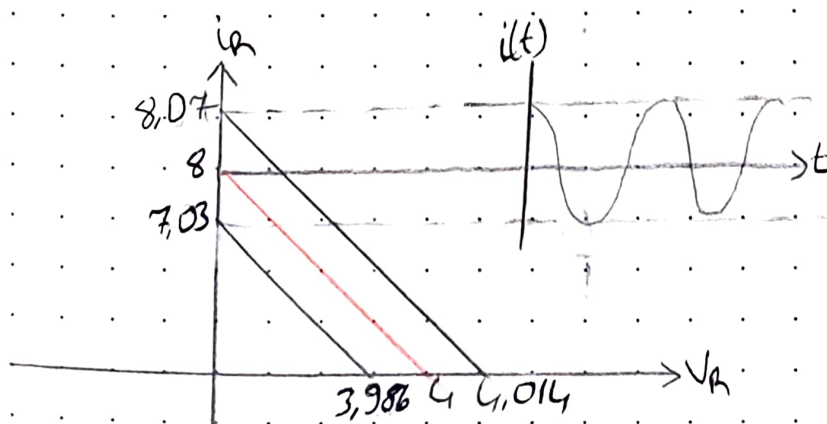
$$V_R = V_Q + \tilde{V}(t) \quad i_R = i_Q + \tilde{i}(t)$$




$$V_R = 2 + \frac{0.1}{7} \sin(10t)$$

$$i_R = 4 + \frac{0.5}{7} \sin(10t)$$

Sem EAS04
040200434

slm

Sens IHS04
040200434
Mina

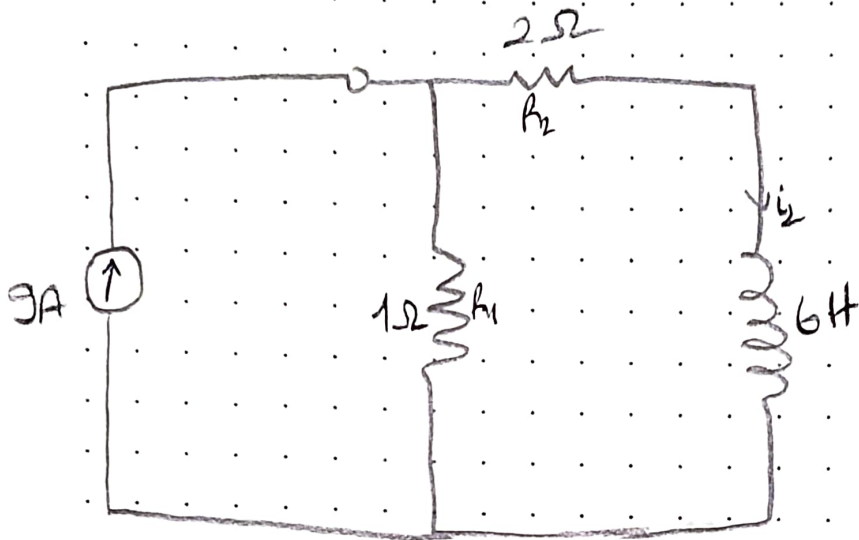

$$V_L = 0 \quad \text{for } t < 0 \quad 2 \cdot I_0 = 1 \cdot I_{R1}, \quad I_{0 \text{ through } R1} = 9A$$

$$1 // 2 = \frac{2}{3} \Omega = R_{eq} \quad I_0 = 3[A]$$

$$\tau = \frac{L}{R} = 2[s]$$

$$i(t) = 3e^{-t/2} [A]$$

$$V_L = L \cdot \frac{di(t)}{dt} = -6 \cdot \frac{3}{2} e^{-t/2} = -9e^{-t/2}$$

