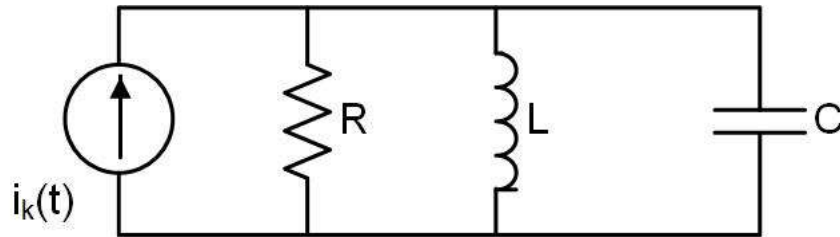


2023-2024 Spring semester, CSA, CRN:22167, Exercise 2


The circuits for questions 1 – 4 are in sinusoidal steady state.

1) Find the resonance frequency for the parallel resonance circuit.



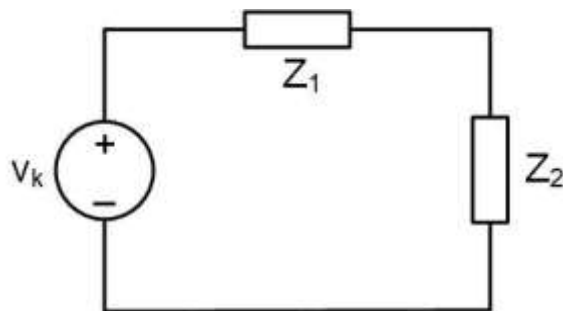2) Find the complex power of Z_1 , Z_2 and the voltage source. What are power factors of Z_1 and Z_2 ?


$v_k(t) = 10 \cos(20t)$, $Z_1 = (1 + j2) \Omega$, $Z_2 = (1 - j3) \Omega$



3-a) Make generalized nodal analysis and write the equations in matrix form. (use phasors)

3-b) Find the current, voltage and average power of the dependent source.

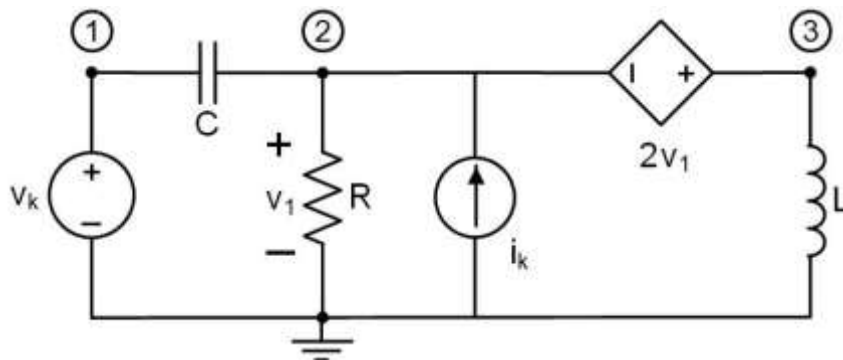$C = 1F$, $L = 1H$, $R = 1\Omega$, $v_k = \cos(t)$, $i_k(t) = 2 \cos(t)$



4) Make generalized mesh analysis and write the equations in matrix form. (use phasors)

$v_k(t) = 34 \cos(2t + 60^\circ)$

