
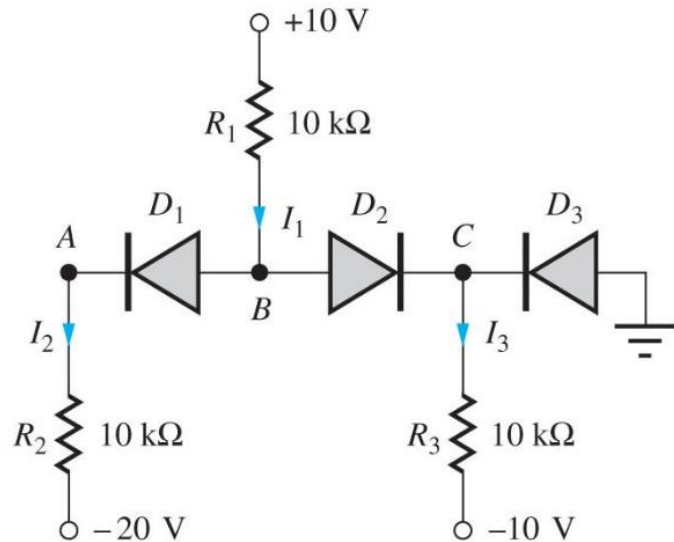


EHB222E INTRODUCTION TO ELECTRONICS (11128, 11129, 11131, 15436)

Midterm Exam 1 1 December 2020 12.15-14.30 (upload time included)


Bora DÖKEN, Bülent YAĞCI, İbrahim ÇATALKAYA, İnci ÇİLESİZ

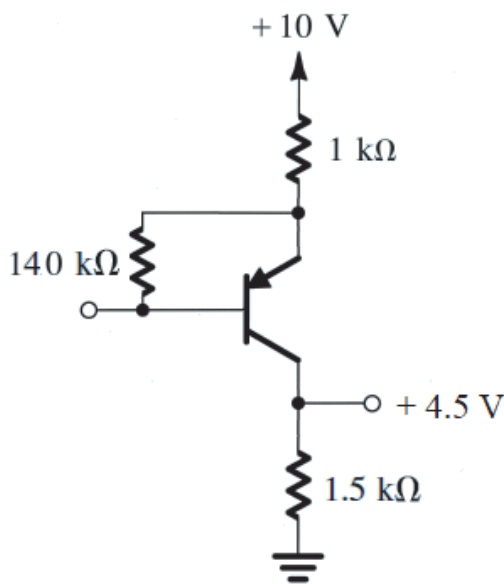1. Use modified diode model ($V_D = 0,7V$) for the diodes on the right. Calculate I_1 , I_2 , and I_3 currents. (25p)



2. Measurements on the circuit above left produced labelled voltages as indicated. Find the values of I_B , I_E , I_C and β for the transistor. ($|V_{BE}| = 0,7 V$) (25p)
3. Junction area of a Si diode is $0,25 \text{ mm}^2$ with doping concentrations of $N_D = 10^{17} / \text{cm}^3$, and $N_A = 10^{15} / \text{cm}^3$, respectively. $n_i = 1,5 \cdot 10^{10} / \text{cm}^3$, $q = 1,602 \cdot 10^{-19} \text{ C}$, $V_T = 25 \text{ mV}$, $\epsilon_r = 12$, $\epsilon_o = 8,85 \cdot 10^{-14} \text{ F/cm}$, $\mu_n = 1350 \text{ cm}^2/\text{Vs}$, $\mu_p = 480 \text{ cm}^2/\text{Vs}$, $\tau_n = \tau_p = 1 \mu\text{sec}$.
- Find minority and majority carrier concentrations in p and n-typed doped regions. (6)
 - Find Barrier potential. (3p)
 - Find depletion width. How much of w is in the n-type doped area, how much in p-typed?. (6p)
 - Find either specific conductances or specific resistances of both typed doped regions. (6p)
 - Find saturation or dark current. (3p)
 - Find junction capacitance when the diode is (6p)
 - Unbiased
 - Reverse biased with 3,5 V
 - Forward biased with 0,2 V.

GOOD LUCK EVERYONE

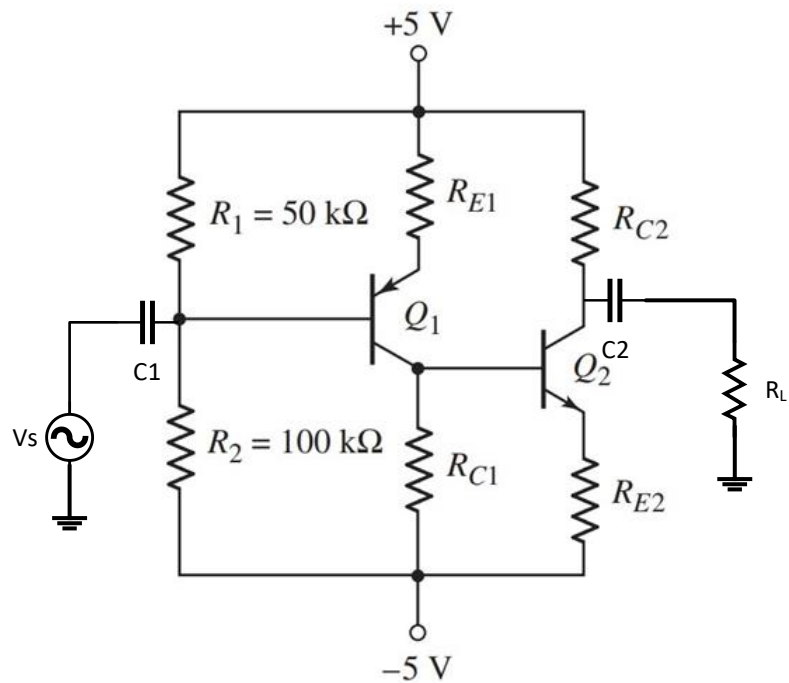

4. For the transistor given in the circuit above, parameters are:

- $\beta = 100$
- $|V_{BE}| = 0,7 \text{ V}$
- $I_{C1} = I_{C2} = 0,8 \text{ mA}$
- $V_{EC,Q1} = 3,5 \text{ V}$
- $V_{CE,Q2} = 4,0 \text{ V}$

Determine R_{C1} , R_{E1} , R_{C2} and R_{E2} . (30p)

SOLUTIONS:

1.

Let's assume Q_1, Q_3 are on and Q_2 is off.

$$V_C = -0.7V \Rightarrow I_3 = \frac{-0.7V - (-10V)}{10k\Omega} = 993\mu A$$

$$10V - R_1 \cdot I_1 - 0.7V - I_2 \cdot R_2 = -20V ; I_1 = I_2$$

$$29.3V = (R_1 + R_2)I_1 \Rightarrow I_1 = \frac{29.3V}{20k\Omega} = 1.465mA$$

$$V_B = 10V - R_1 I_1 = -4.65V \Rightarrow V_B < V_C$$

If $V_B < V_C$ assumption for Q_2 is correct.

The direction of current flows of I_3 and I_2 are correct. So, assumptions for Q_1 and Q_3 are correct.

2.

$$I_C = \frac{4.5V}{1.5K} = 3mA \quad (5p)$$

$$I = I_C = I_E - I_B$$

$$V_E = 10V - I \cdot 1K$$


$$V_E = 10V - 3V = 7V \quad (5p)$$

$$I_B = \frac{7V - 0.7V}{140K} = 45\mu A \quad (5p)$$

$$I_E = 3mA + 45\mu A$$

$$I_E = 3.045mA \quad (5p)$$

$$\beta = \frac{I_C}{I_B} = \frac{3mA}{0.045mA} = 66.67$$
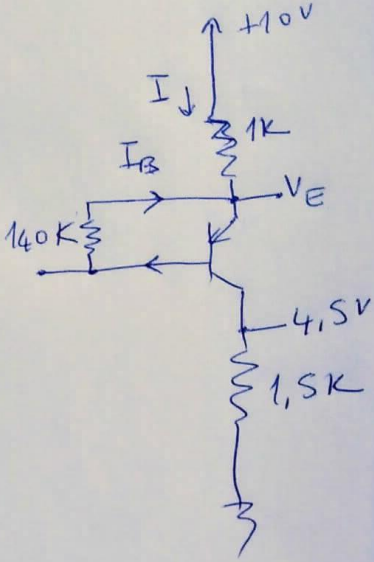
$$\beta \approx 67 \quad (5p)$$


3. Step by step (a) through (f)

| doping | Majority carriers | Minority carriers |
|--------|-------------------------------------|---|
| n | $n_n = N_D = 10^{17} / \text{cm}^3$ | $p_n = n_i^2 / N_D = 2,25 \cdot 10^3 / \text{cm}^3$ |
| p | $p_p = N_A = 10^{15} / \text{cm}^3$ | $n_p = n_i^2 / N_A = 2,25 \cdot 10^5 / \text{cm}^3$ |

$$V_B = -V_T \cdot \ln \left[\frac{n_i^2}{N_A N_D} \right] = 671 \text{ mV}$$

$$w = \sqrt{\frac{2\epsilon_0 \epsilon_r V_B}{q} \left(\frac{1}{N_A} + \frac{1}{N_D} \right)} = 9,48 \cdot 10^{-5} \text{ cm} = 948 \text{ nm.}$$

Since $N_D/N_A = 100/1$ thus $x_p/x_n = 100/1$ and therefore

$$x_p = (100/101) w = 939 \text{ nm} \text{ and } x_n = (1/101) w = 9 \text{ nm}$$

Majority carriers considered $\sigma_n = \mu_n n_n q = 21,6 \text{ } 1/\Omega \text{cm}$ and $\sigma_p = \mu_p p_p q = 0,07 \text{ } 1/\Omega \text{cm}$

$$I_s = -q \left[\frac{D_n n_i^2}{L_n N_A} + \frac{D_p n_i^2}{L_p N_D} \right] = 5,27 \text{ fA, from } V_T = \frac{D}{\mu}, \text{ you can find } D_n = 33,8, \text{ and } D_p = 12,0 \text{ (guess your units!!!)}$$

And from $L = \sqrt{D\tau}$ you can find $L_n = 5,81 \cdot 10^{-3} \text{ cm} = 0,58 \text{ } \mu\text{m}$ and $L_p = 3,46 \cdot 10^{-3} \text{ cm} = 0,35 \text{ } \mu\text{m}$


Junction capacitance can be found from $C_j = \epsilon \frac{A}{w}$

That means you need to find w in all three cases:


$$w(\text{unbiased}) = \sqrt{\frac{2\epsilon_0 \epsilon_r V_B}{q} \left(\frac{1}{N_A} + \frac{1}{N_D} \right)} = 948 \text{ nm} \text{ Thus } C_j = 256 \text{ fF}$$

$$w(-3,5V) = \sqrt{\frac{2\epsilon_0 \epsilon_r (V_B + 3,5V)}{q} \left(\frac{1}{N_A} + \frac{1}{N_D} \right)} = 2,36 \text{ } \mu\text{m} \text{ Thus } C_j = 103 \text{ fF}$$
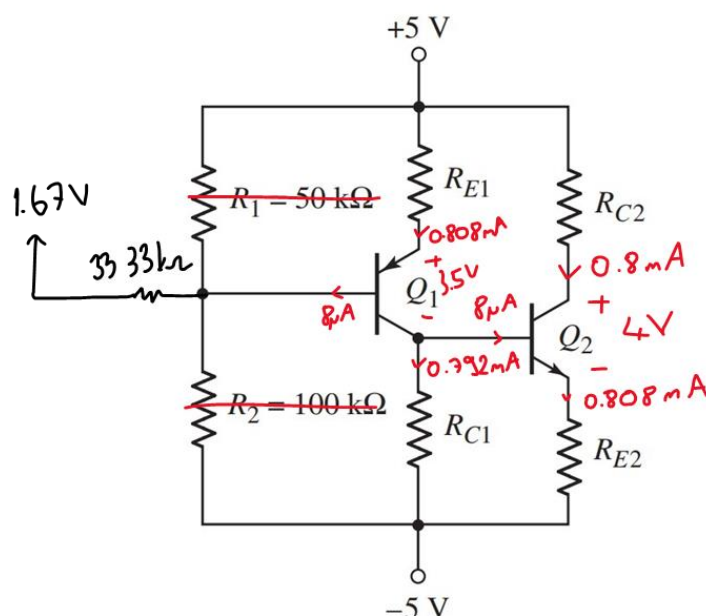
$$w(+0,2V) = \sqrt{\frac{2\epsilon_0 \epsilon_r (V_B - 0,2V)}{q} \left(\frac{1}{N_A} + \frac{1}{N_D} \right)} = 794 \text{ nm} \text{ Thus } C_j = 306 \text{ fF}$$



4.

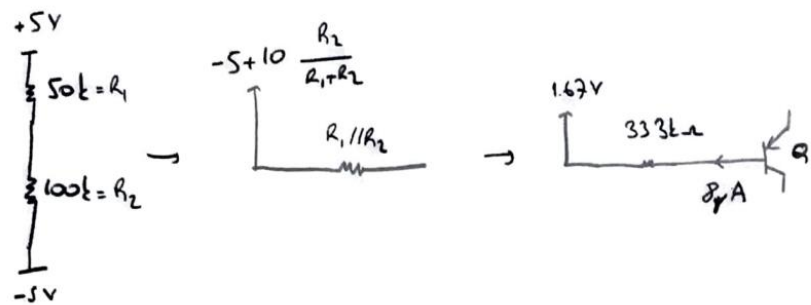

$$\frac{V_{B1} - 1.67V}{33.3k\Omega} = 80\mu A \rightarrow V_{B1} \approx 1.936V$$

$$V_{E1} \approx 2.636V \approx V_{B1} + 0.7V$$

$$V_{C1} \approx V_{E1} - 3.5V \approx -0.864V \approx V_{B2}$$

$$V_{E2} = V_{B2} + 0.7V = -0.164V$$

$$V_{C2} = V_{E2} + 4V = 3.836V$$

$$R_{E1} = \frac{(5 - 2.636)V}{0.808mA} = 2.93k\Omega$$

$$R_{C1} = \frac{-0.864V + 5V}{0.792mA} = 5.22k\Omega$$

$$R_{C2} = \frac{5 - 3.836}{0.8} = 1.455k\Omega$$

$$R_{E2} = \frac{(-0.164 + 5)V}{0.808mA} = 5.985k\Omega$$