

ELK343E - Electromechanical Energy Conversion

Lale ERGENE
HOMEWORK 2

Sena ERSOY - 040200434

09.01.2025



I pledge on my honor that: I have completed all steps of the attached HW on my own, I have not used any unauthorized materials while completing it, and I have not given anyone else access to my work on this HW.

Sena

1 Calculations

1.1 Calculation of a (Transformation Ratio)

The primary and secondary phase voltages were calculated by dividing the given line-to-line voltages by $\sqrt{3}$:

$$V_{1,\text{phase}} = \frac{36 \text{ kV}}{\sqrt{3}} = 20.78 \text{ kV}, \quad V_{2,\text{phase}} = \frac{0.4 \text{ kV}}{\sqrt{3}} = 230.94 \text{ V}.$$

The transformation ratio a was then calculated as:

$$a = \frac{V_{1,\text{phase}}}{V_{2,\text{phase}}} = \frac{20780}{230.94} = 89.98.$$

1.2 Calculation of R'_2 (Referred Secondary Resistance)

The referred secondary resistance R'_2 was calculated using the transformation ratio a :

$$R'_2 = a^2 R_2.$$

Given $R_2 = 1.7 \text{ m}\Omega$, the referred resistance becomes:

$$R'_2 = (89.98)^2 \times 1.7 \times 10^{-3} = 13.76 \Omega.$$


1.3 Calculation of $X'_{2\sigma}$ (Referred Secondary Reactance)

Similarly, the referred secondary reactance $X'_{2\sigma}$ was calculated as:

$$X'_{2\sigma} = a^2 X_{2\sigma}.$$

Given $X_{2\sigma} = 3.6 \text{ m}\Omega$, the referred reactance becomes:
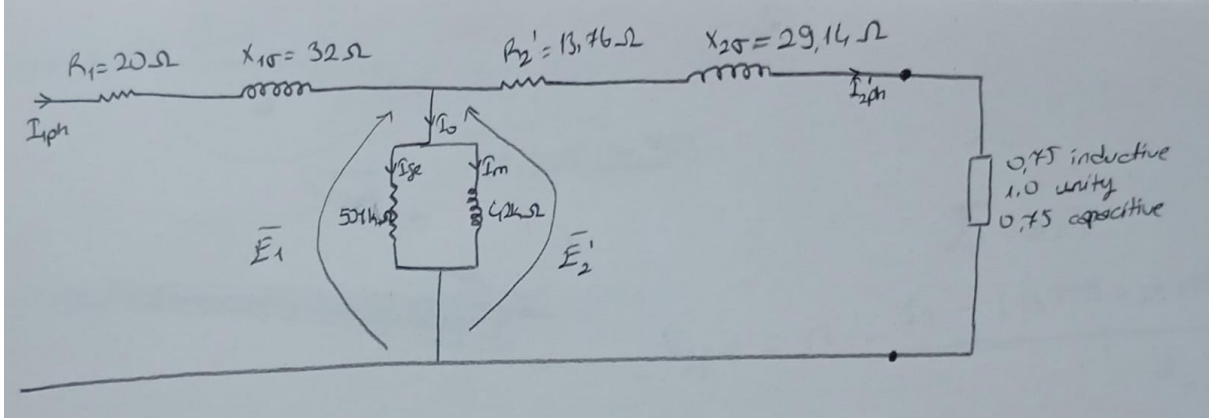
$$X'_{2\sigma} = (89.98)^2 \times 3.6 \times 10^{-3} = 29.14 \Omega.$$



1.4 Calculation of Input Line Current

The apparent power S was calculated using the formula:

$$S = \sqrt{3} \cdot V_{1,\text{p-p}} \cdot I_{1,\text{p-p}}.$$

Rearranging for $I_{1,\text{p-p}}$:

$$I_{1,\text{p-p}} = \frac{S}{V_{1,\text{p-p}} \cdot \sqrt{3}}.$$

Due to the wye connection, $I_{\text{p-p}} = I_{\text{ph}}$, so the input line current $I_{1,\text{ph}}$ can be calculated as:

$$I_{1,\text{ph}} = \frac{S}{\sqrt{3} \cdot 36000},$$

with varying S values.

1.5 Calculation of E_1 (Primary Phase Voltage)

The primary phase voltage E_1 was calculated by considering the voltage drop ΔV_1 :

$$E_1 = V_{1,\text{phase}} - \Delta V_1.$$

The voltage drop ΔV_1 was calculated as:

$$\Delta V_1 = I_{1,\text{ph}}(R_1 + jX_{1\sigma}).$$

Given $R_1 = 20\ \Omega$ and $X_{1\sigma} = 32\ \Omega$, the expression becomes:

$$E_1 = 20780 - I_{1,\text{ph}}(20 + j32).$$

1.6 Calculation of $I'_{2,\text{ph}}$ (Referred Secondary Current)

The referred secondary current $I'_{2,\text{ph}}$ was calculated as:

$$I'_{2,\text{ph}} = I_{1,\text{ph}} - I_0,$$

where I_0 represents the no-load current consisting of the iron loss component I_{fe} and the magnetizing current jI_m . The no-load current I_0 was calculated as:

$$I_0 = \frac{E_1}{R_{\text{fe}}//X_m}.$$

Using the equivalent parallel impedance $R_{\text{fe}}//X_m = 3496.4339 + 41706.8855j$, the expression for $I'_{2,\text{ph}}$ becomes:

$$I'_{2,\text{ph}} = I_{1,\text{ph}} - \frac{E_1}{3496.4339 + 41706.8855j}.$$

1.7 Calculation of Secondary Phase-to-Phase Voltage $V_{2,\text{p-p}}$

The secondary phase-to-phase voltage $V_{2,\text{p-p}}$ was calculated as:

$$V_{2,\text{p-p}} = \sqrt{3} \cdot \frac{E_1 - \Delta V'_{2,\text{ph}}}{a}.$$

The referred secondary phase voltage drop $\Delta V'_{2,\text{ph}}$ was calculated as:

$$\Delta V'_{2,\text{ph}} = (13.7599 + 29.1395j)I'_{2,\text{ph}}.$$

Substituting into the equation for $V_{2,\text{p-p}}$, we get:

$$V_{2,\text{p-p}} = \sqrt{3} \cdot \frac{E_1 - (13.7599 + 29.1395j)I'_{2,\text{ph}}}{89.98}.$$

1.8 Calculation of Copper and Iron Losses

The copper losses P_{cu} were calculated as:

$$P_{\text{cu}} = 3 \cdot (I_{1,\text{ph}})^2 \cdot R_1 + (I'_{2,\text{ph}})^2 \cdot R'_2.$$

Substituting the given values:

$$P_{\text{cu}} = 3 \cdot (I_{1,\text{ph}})^2 \cdot 20 + (I'_{2,\text{ph}})^2 \cdot 13.76.$$

The iron losses P_{fe} were calculated as:

$$P_{\text{fe}} = 3 \cdot (I_{\text{fe}})^2 \cdot R_{\text{fe}},$$

where I_{fe} is the real part of I_0 :

$$P_{\text{fe}} = 3 \cdot \text{Re}(I_0)^2 \cdot 501000.$$

1.9 Calculation of Efficiency

The efficiency of the transformer was calculated using the formula:

$$\text{Efficiency} = \frac{P_{\text{out}}}{P_{\text{in}}} \times 100.$$

The output power P_{out} and input power P_{in} were defined as:

$$P_{\text{out}} = S \cdot \cos(\phi) - (P_{\text{cu}} + P_{\text{fe}}), \quad P_{\text{in}} = S \cdot \cos(\phi).$$

Substituting these into the efficiency equation:

$$\text{Efficiency} = \frac{S \cdot \cos(\phi) - (P_{\text{cu}} + P_{\text{fe}})}{S \cdot \cos(\phi)} \times 100.$$

2 Code and Plotting

```
import pandas as pd
import numpy as np
import matplotlib.pyplot as plt

# Constants
a = 89.98
S_max = 400 * 1e3 # 400 kVA converted to VA
phi_values = {
    "0.75 Inductive": np.arccos(0.75),
    "1.0 Unity": np.arccos(1.0),
    "0.75 Capacitive": np.arccos(-0.75)
}

# Function to calculate parameters with debugging
def calculate_parameters(S_values, phi_values):
    results = {
        "Case": [],
        "S (kVA)": [],
        "I1ph (A)": [],
        "E1 (V)": [],
        "I0 (A)": [],
        "I0_reel (A)": [],
        "I2ph (A)": [],
        "V2p-p (V)": [],
        "Pcu (W)": [],
        "Pfe (W)": [],
        "Efficiency (%)": []
    }

    for phi_name, phi in phi_values.items():
        for S in S_values:
            # Step 1: Calculate Input Line Current
            I1ph = (S / 62353.829)

            # Step 2: Calculate Induced Voltage
            E1 = 20780 - I1ph * (20 + 32j)

            # Step 3: Calculate Iron Loss Current
            I0 = E1 / (3496.4339 + 41706.8855j)

            # Step 4: Calculate Secondary Phase Current
            I2ph = I1ph - I0
```

```

# Step 5: Calculate Phase-to-Phase Voltage
V2p_p = np.sqrt(3) * (E1 - (13.7599 + 29.1395j) * I2ph) / a

# Step 6: Copper and Iron Losses
Pcu = 3 * ((abs(I1ph) ** 2) * 20 + (abs(I2ph) ** 2) * 13.76)
Pfe = 3 * (I0.real ** 2) * 501000

# Step 7: Output Power and Efficiency
P_in = abs(S * np.cos(phi))
P_out = P_in - (Pcu + Pfe)
efficiency = (P_out / P_in) * 100

# Append to Results
results["Case"].append(phi_name)
results["S (kVA)"].append(S / 1e3) # Convert back to kVA for display
results["I1ph (A)"].append(abs(I1ph))
results["E1 (V)"].append(abs(E1))
results["I0 (A)"].append(abs(I0))
results["I0_reel (A)"].append(I0.real) # Real part of I0
results["I2ph (A)"].append(abs(I2ph))
results["V2p-p (V)"].append(abs(V2p_p))
results["Pcu (W)"].append(Pcu)
results["Pfe (W)"].append(Pfe)
results["Efficiency (%)"].append(efficiency)

return pd.DataFrame(results)

# S values as a percentage of S_max (10% to 100% in 1% increments)
percentages = np.arange(10, 101, 1) # Percentages from 10% to 100%
S_values = (percentages / 100) * S_max

# Calculate results
results_df = calculate_parameters(S_values, phi_values)

# Function to plot individual results
def plot_individual_results(results_df):
    cases = results_df["Case"].unique()
    for case in cases:
        df_case = results_df[results_df["Case"] == case]
        print(f"Plotting graphs for {case}...")

        # Plot I1ph vs S
        plt.figure(figsize=(8, 6))
        plt.plot(df_case["S (kVA)"], df_case["I1ph (A)"], label="I1ph")
        plt.xlabel("S (kVA)")
        plt.ylabel("I1ph (A)")
        plt.grid(True)
        plt.legend()
        plt.show()

        # Plot E1 vs S
        plt.figure(figsize=(8, 6))
        plt.plot(df_case["S (kVA)"], df_case["E1 (V)"], label="E1")
        plt.xlabel("S (kVA)")
        plt.ylabel("E1 (V)")
        plt.grid(True)
        plt.legend()

```

```

plt.show()

# Plot V2p-p vs S
plt.figure(figsize=(8, 6))
plt.plot(df_case["S (kVA)"], df_case["V2p-p (V)"], label="V2p-p")
plt.xlabel("S (kVA)")
plt.ylabel("V2p-p (V)")
plt.grid(True)
plt.legend()
plt.show()

# Plot Pcu vs S
plt.figure(figsize=(8, 6))
plt.plot(df_case["S (kVA)"], df_case["Pcu (W)"], label="Pcu")
plt.xlabel("S (kVA)")
plt.ylabel("Pcu (W)")
plt.grid(True)
plt.legend()
plt.show()

# Plot Pfe vs S
plt.figure(figsize=(8, 6))
plt.plot(df_case["S (kVA)"], df_case["Pfe (W)"], label="Pfe")
plt.xlabel("S (kVA)")
plt.ylabel("Pfe (W)")
plt.grid(True)
plt.legend()
plt.show()

# Plot Efficiency vs S
plt.figure(figsize=(8, 6))
plt.plot(df_case["S (kVA)"], df_case["Efficiency (%)"], label="Efficiency")
plt.xlabel("S (kVA)")
plt.ylabel("Efficiency (%)")
plt.grid(True)
plt.legend()
plt.show()




# Plot results individually for each case
plot_individual_results(results_df)




# Save to Excel
file_path = 'Calculations.xlsx'
results_df.to_excel(file_path, index=False)

print(f"Results saved to: {file_path}")




```




Plots for Inductive Load

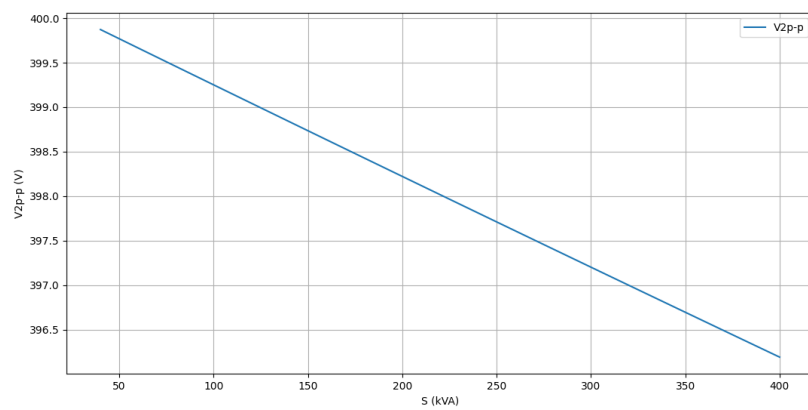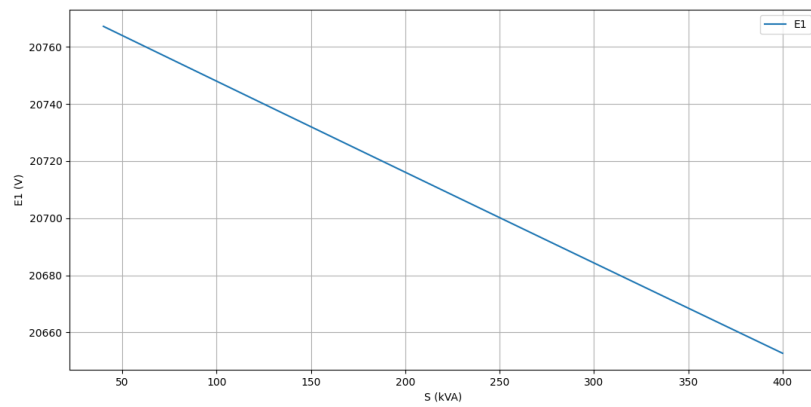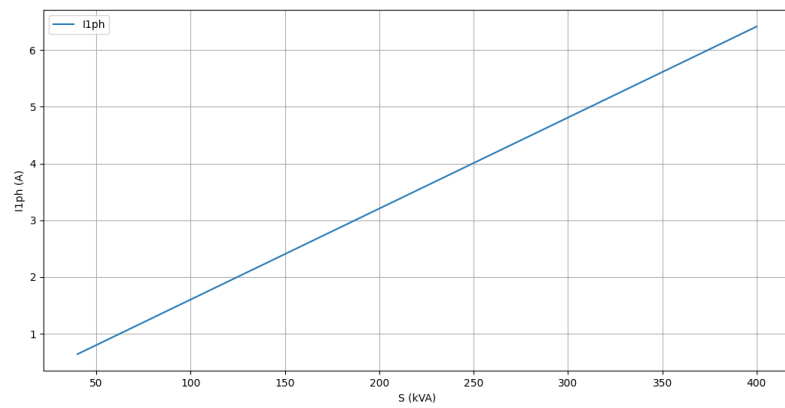

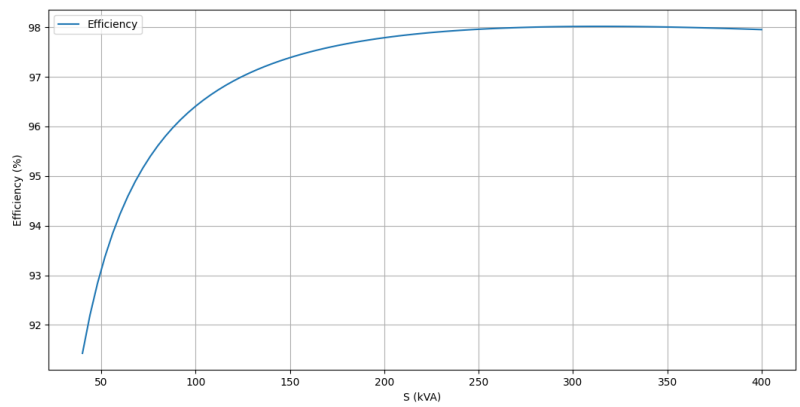
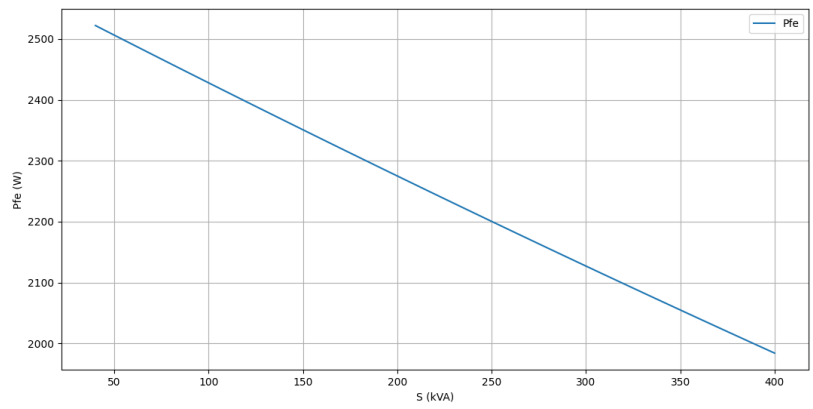
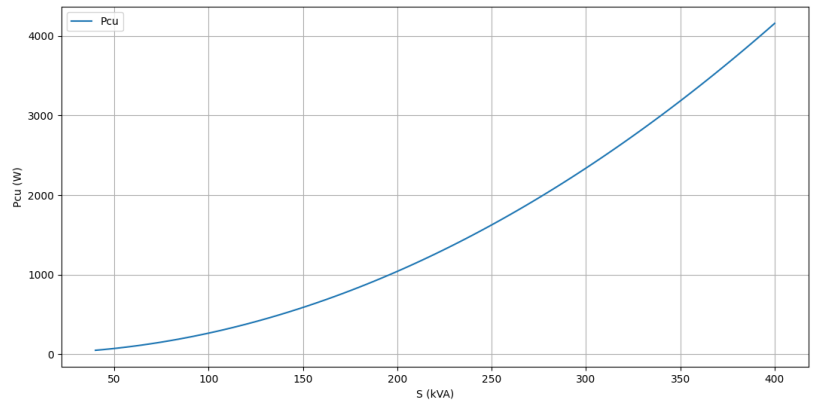





Plots for Unity Case

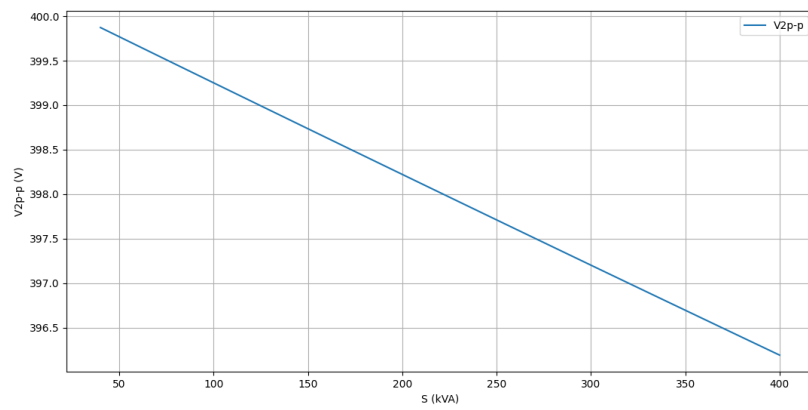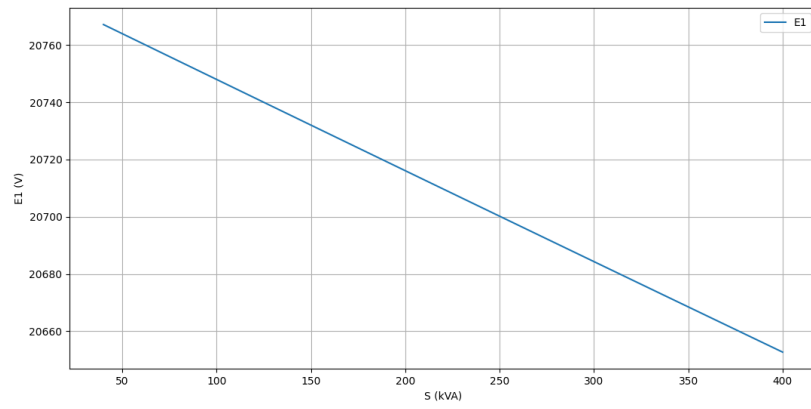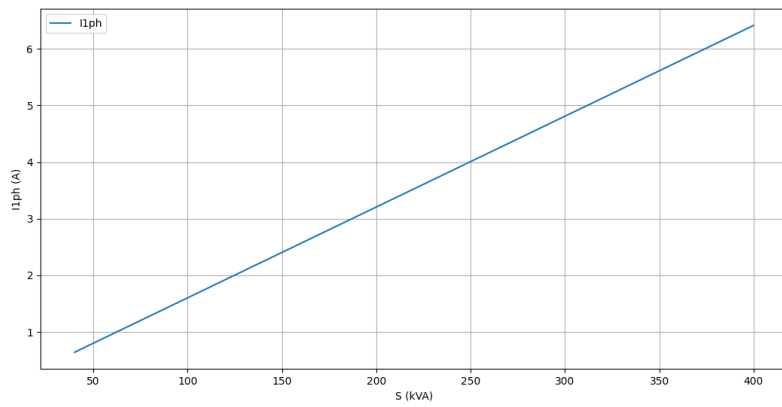

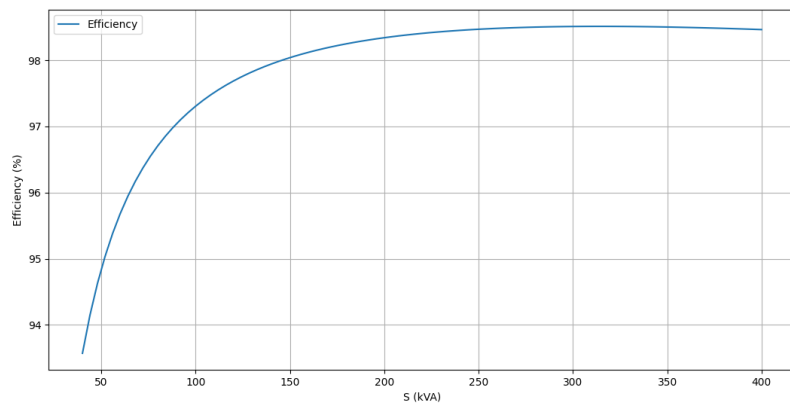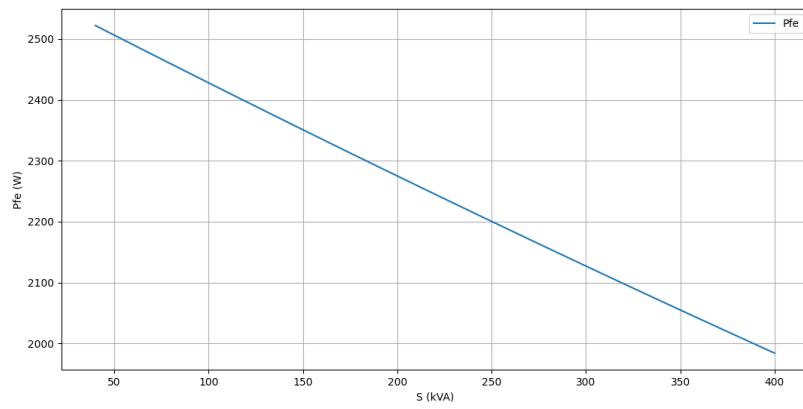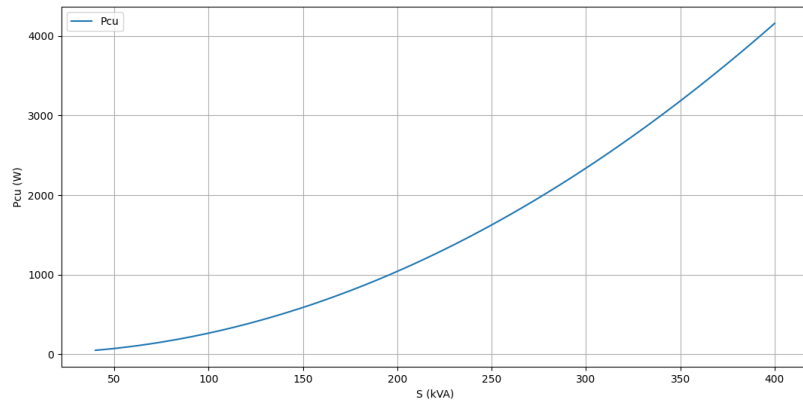

Plots for Capacitive Load

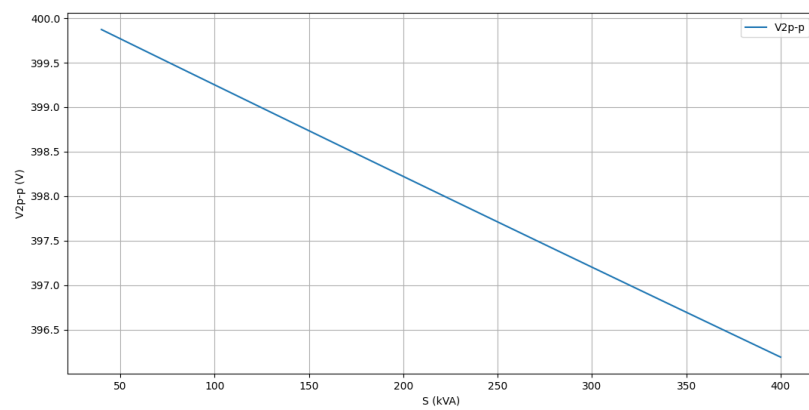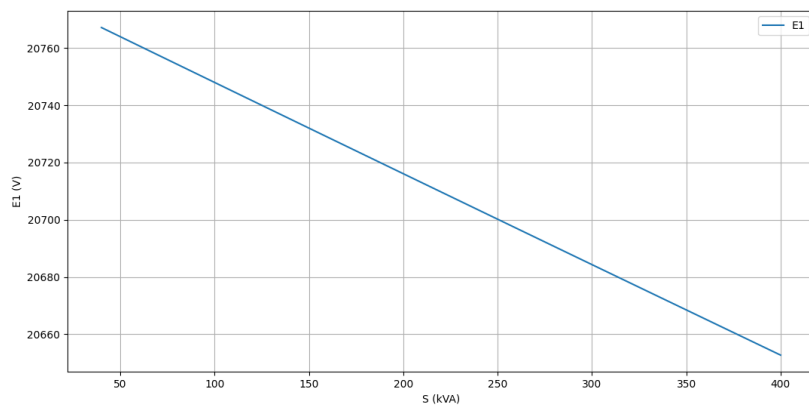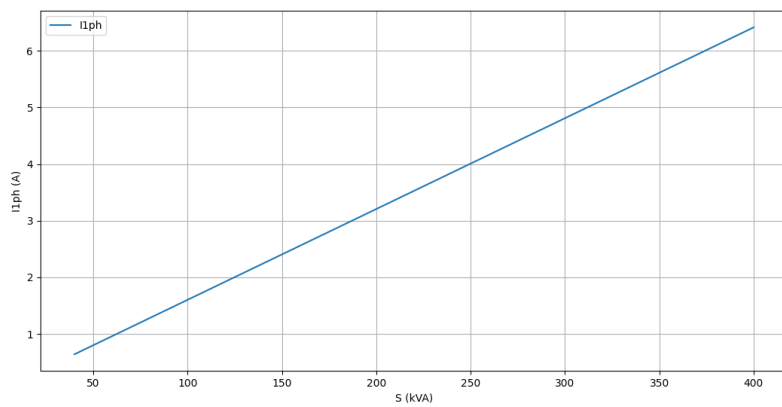

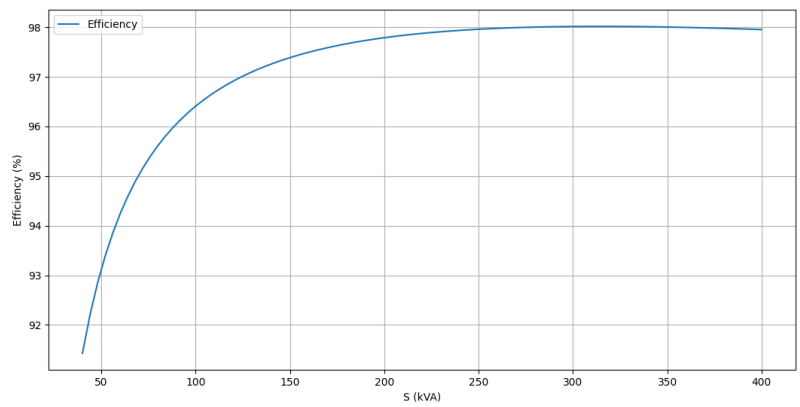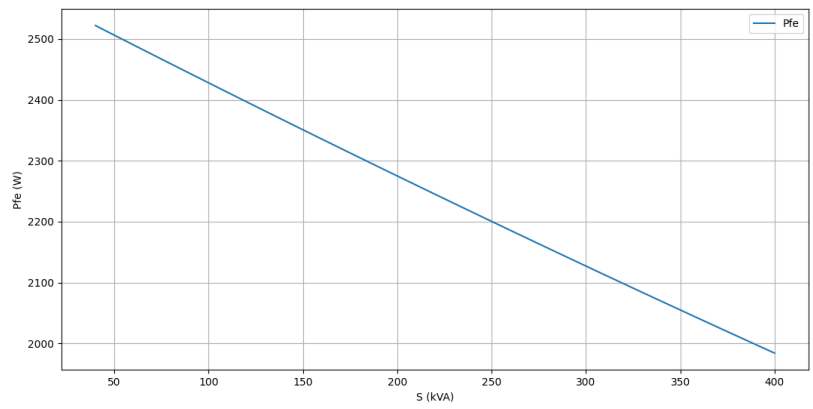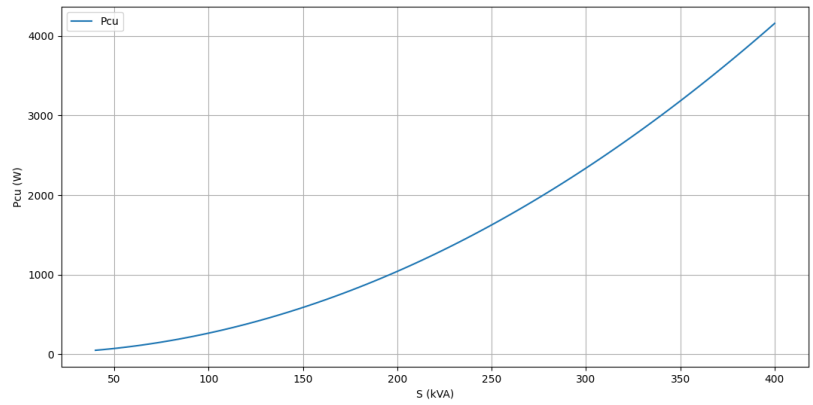

Analysis of Transformer Performance

The analysis of the transformer performance under varying load conditions was conducted by evaluating the trends of primary induced voltage (E_1), secondary phase-to-phase voltage (V_{2pp}), and iron losses (P_{fe}) across different load types (0.75 inductive, unity, and 0.75 capacitive) from 10% to 100% of the maximum load (S_{max}). The results demonstrate expected and realistic behavior of transformer performance under these conditions.

The primary induced voltage (E_1) consistently decreases with increasing load across all load types. This is attributed to the increased current flow causing larger voltage drops across the transformer's internal impedance. Inductive loads show the steepest decline due to the lagging power factor and higher reactive current, while capacitive loads exhibit a smaller initial decrease because the leading current partially compensates for the reactance at lower load levels. Unity power factor loads present a moderate and balanced decline, aligning with theoretical expectations.

Similarly, the secondary phase-to-phase voltage (V_{2pp}) follows a decreasing trend as the load increases. The voltage drop is most significant for inductive loads due to their higher reactive component, whereas capacitive loads mitigate the decrease at lighter loads owing to their leading power factor. The voltage trend for unity loads remains consistent with a moderate drop, reflective of an ideal power factor of 1.

Iron losses (P_{fe}), which are primarily dependent on core flux density and applied voltage, show a marginal decrease as load increases. This behavior is due to the slight reduction in the applied voltage under heavier loads. While inductive loads cause a slightly faster reduction in P_{fe} due to larger voltage drops, capacitive loads exhibit a slower rate of decrease at lighter loads due to the compensatory effect of the leading current. Unity loads display a consistent and moderate reduction, as expected.

These trends validate the theoretical expectations and highlight the importance of load characteristics in transformer performance. Understanding these behaviors is essential for optimizing transformer design and ensuring reliable operation under varying load conditions.

Research on Windings

Power transformer windings play a critical role in determining the efficiency, performance, and reliability of transformers. The two primary types of windings are cylindrical windings and disc windings, which are chosen based on the voltage level, current capacity, and thermal requirements. Cylindrical windings are typically used for low-voltage (LV) sides due to their simplicity and cost-effectiveness. These windings are suitable for handling high currents and provide efficient cooling when paired with forced-air or oil-based cooling systems. On the other hand, disc windings are commonly used for high-voltage (HV) sides because they are better suited for managing higher voltages and reducing insulation stress. They consist of multiple discs separated by spacers, allowing for improved cooling and greater dielectric strength.

When designing windings, key factors such as current density, voltage level, insulation requirements, and thermal dissipation must be considered. For LV windings, materials such as copper or aluminum with thicker conductors are chosen to handle high currents, while HV windings often use finer conductors and enhanced insulation systems to withstand high electrical stresses. Additionally, the design must minimize eddy current losses, optimize the magnetic flux distribution, and ensure mechanical stability under short-circuit conditions. Advanced techniques, such as finite element analysis (FEA), are often employed to refine the winding design and ensure the transformer meets operational and safety standards.

References

- [1] A. E. Fitzgerald, C. Kingsley, and S. D. Umans, *Electric Machinery*, 6th ed. New York: McGraw-Hill, 2003.
- [2] D. K. Cheng, *Field and Wave Electromagnetics*, 2nd ed. Boston: Addison-Wesley, 1989.
- [3] W. M. Flanagan, *Handbook of Transformer Design and Applications*. McGraw-Hill, 1992.
- [4] K. Karsai, D. Kerényi, and L. Kiss, *Large Power Transformers*. Elsevier Science, 1987.
- [5] IEEE, *IEEE Std C57.12.90-2010: Standard Test Code for Liquid-Immersed Distribution, Power, and Regulating Transformers*, 2010.
- [6] S. V. Kulkarni and S. A. Khaparde, "Transformer Engineering: Design, Technology, and Diagnostics," *Power Systems Series*, CRC Press, 2004.
- [7] EEP, "Types of Transformer Windings and Their Applications," Electrical Engineering Portal, 2019. [Online]. Available: <https://electrical-engineering-portal.com/>
- [8] ABB Transformers, "Transformer Basics and Windings Design," ABB Official Website, 2020. [Online]. Available: <https://new.abb.com/>