



ELK406E



Distribution of Electrical Energy

Prof.Dr. Mustafa BAĞRIYANIK

E-mail: bagriy@itu.edu.tr


Voltage Drop

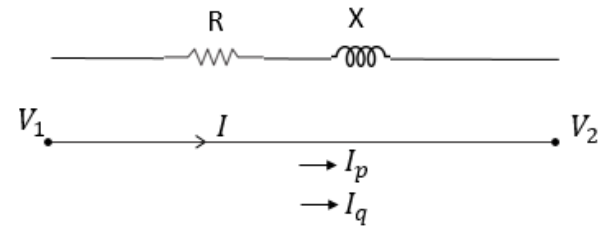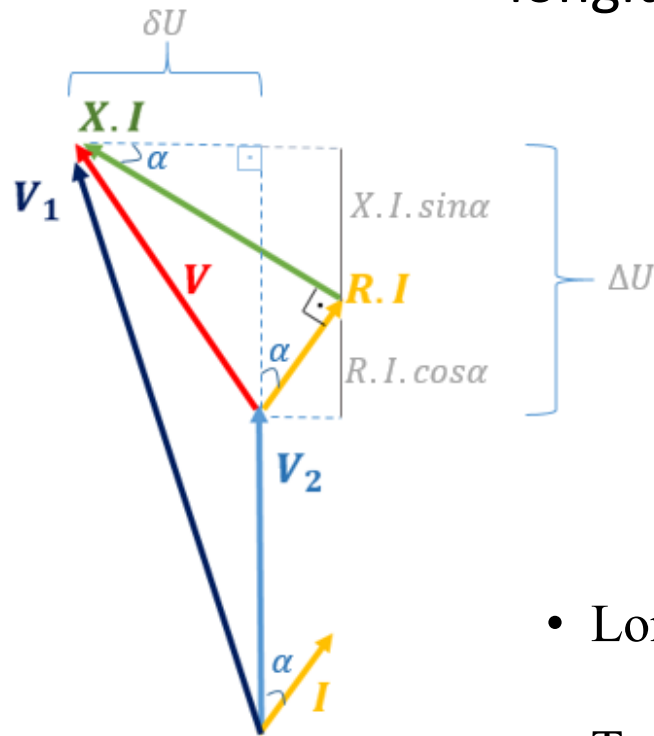- Voltage drop has two components, a longitudinal and a transversal component



- Longitudinal *Voltage Drop*, $\Delta U = R I_p + X I_q$
- Transversal *Voltage Drop*, $\delta U = X I_p - R I_q$

Closed Loop VD

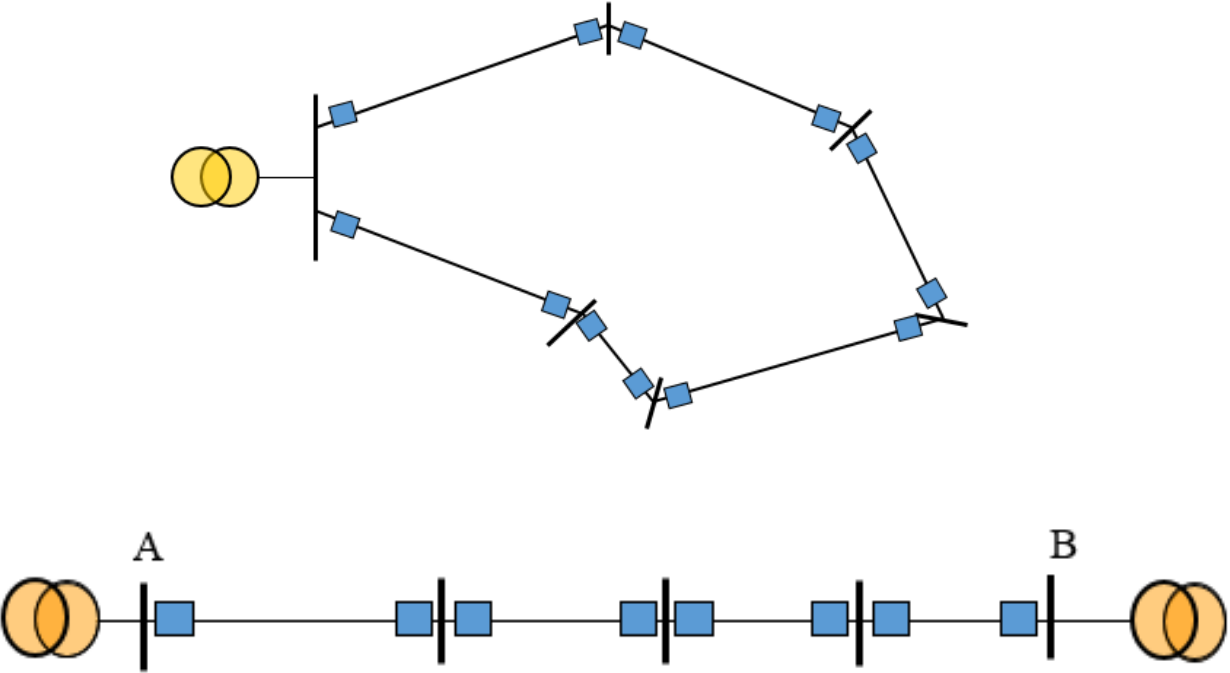



Closed loop systems

1

In closed loop systems, the feeders are fed at both ends.

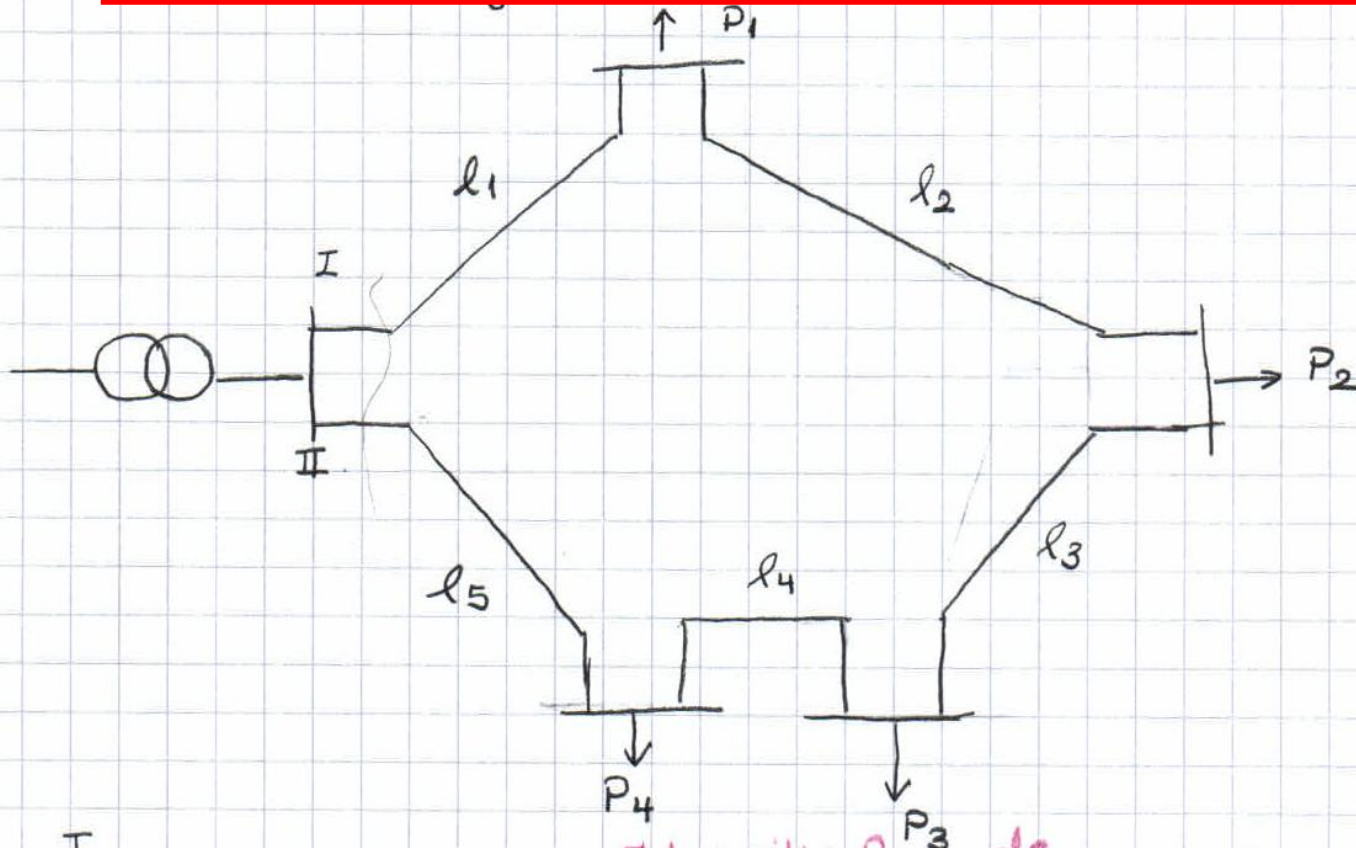— Feeders being fed at both ends with equal voltage.




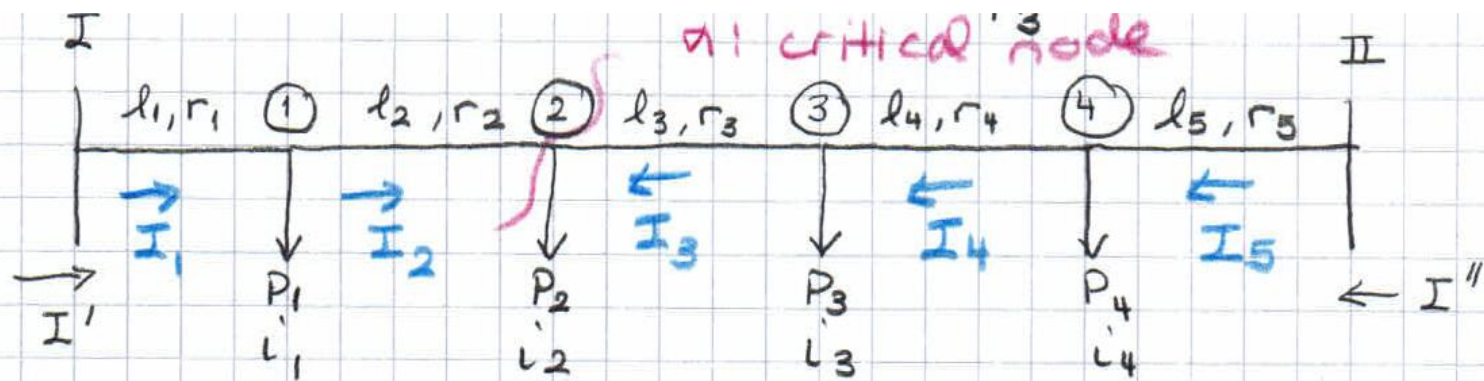

I' : current supplied from I.


I'' : current supplied from II

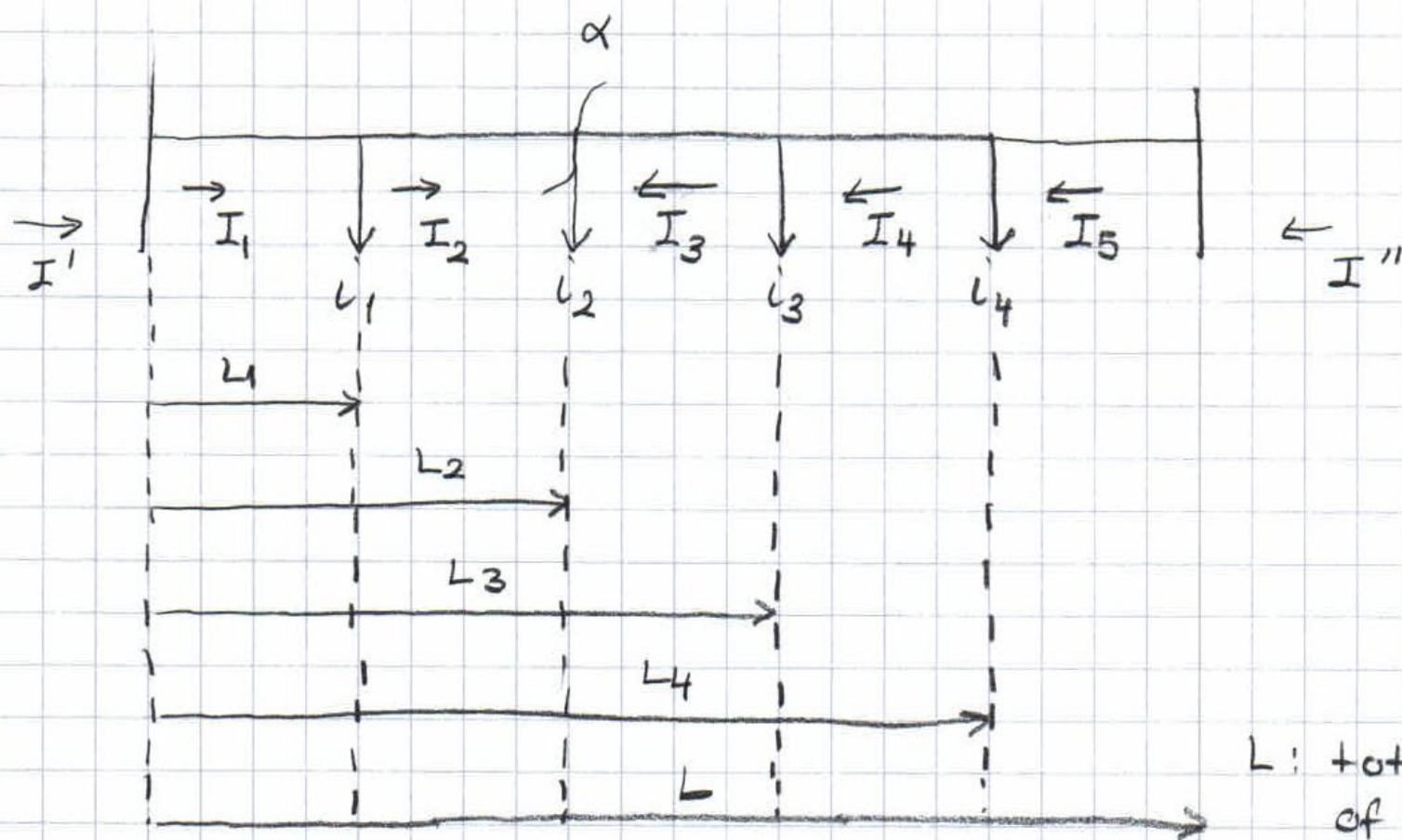Since $V_I = V_{II}$, total voltage drop along the feeder is zero ($\Delta V = 0$). That means, there's a critical node α where the potential is minimum or in other words, the voltage drop is maximum. At the critical node α , the line current changes direction.





L : total length of the feeder.

current
diagram

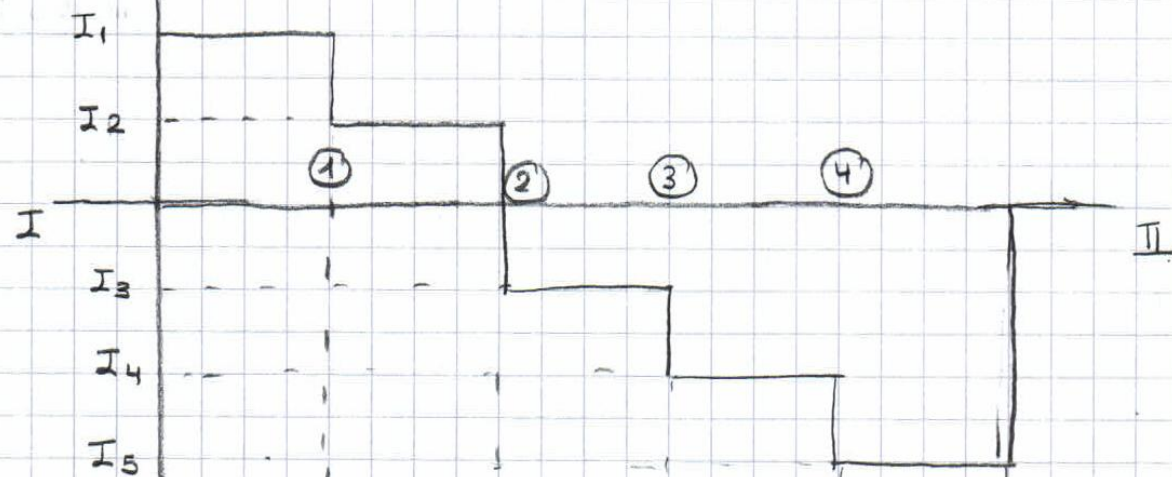

voltage
diagram

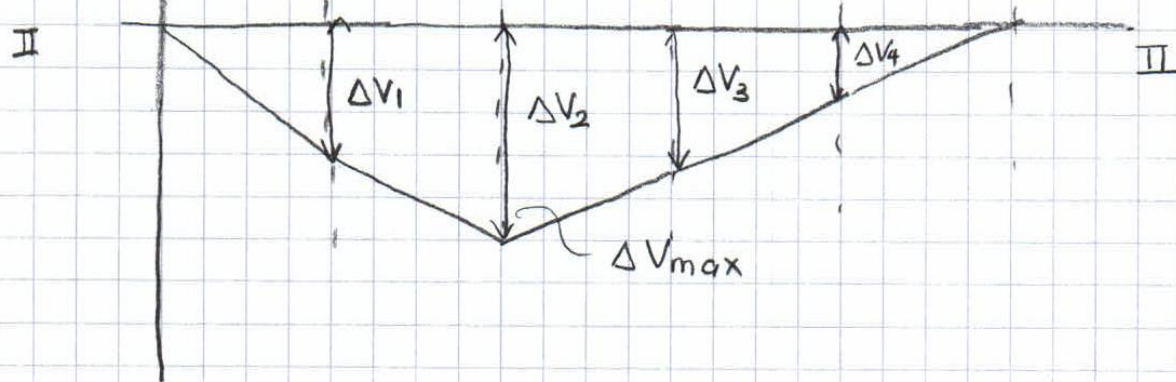

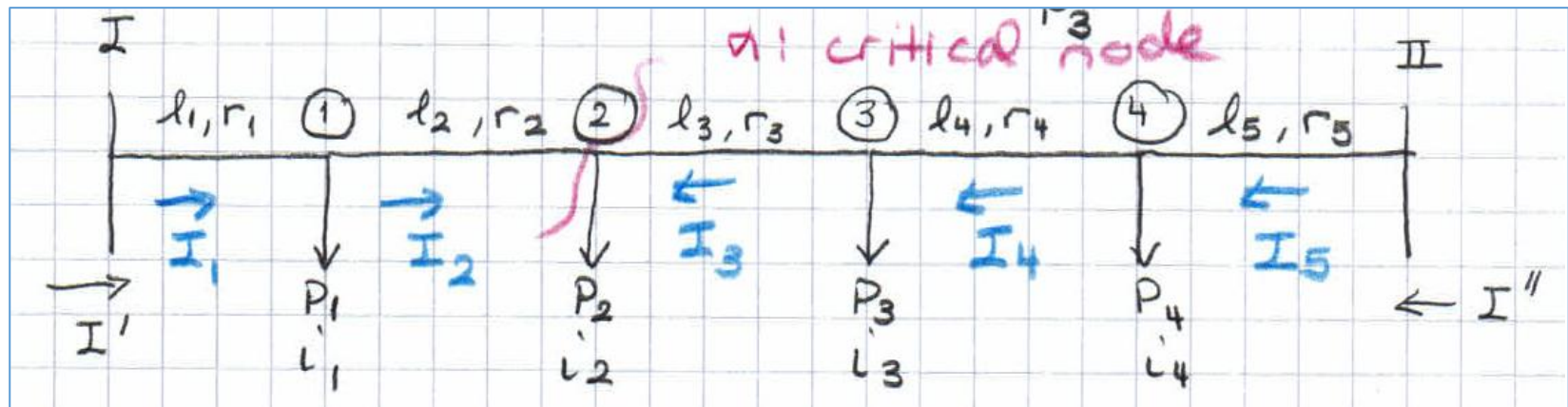

The aim is to find the current distribution (line currents) along the feeder and the critical node

✓ Total voltage drop along the feeder;

$$r_1 I_1 + r_2 I_2 + r_3 I_3 + r_4 I_4 + r_5 I_5 = 0$$

Let's express each line current in terms of I_5 .

$$r_1 (I_5 - i_4 - i_3 - i_2 - i_1) + r_2 (I_5 - i_4 - i_3 - i_2) + r_3 (I_5 - i_4 - i_3) + r_4 (I_5 - i_4) + r_5 I_5 = 0$$

$$I_5 \underbrace{(r_1 + r_2 + r_3 + r_4 + r_5)}_{L \cdot r} = i_4 \underbrace{(r_1 + r_2 + r_3 + r_4)}_{L_4 \cdot r} + i_3 \underbrace{(r_1 + r_2 + r_3)}_{L_3 \cdot r}$$

$$+ i_2 \underbrace{(r_1 + r_2)}_{L_2 \cdot r} + \underbrace{r_1 i_1}_{L_1 \cdot r} \quad r: \text{resistance per unit length}$$

$$I_5 \cdot L \cdot r = i_4 \cdot L_4 \cdot r + i_3 L_3 \cdot r + i_2 L_2 \cdot r + i_1 L_1 \cdot r$$


$$I_5 \cdot L = i_4 \cdot L_4 + i_3 L_3 + i_2 L_2 + i_1 L_1$$

$$= \sum_{n=1}^4 i_n L_n \quad \because \text{sum of the moments of load currents about feeding pt. I.}$$

$$I'' = I_5 = \frac{\sum_{n=1}^4 i_n L_n}{L}$$

$$\Delta V_{I-\alpha} = \Delta V_{II-\alpha}$$

Closed Loop VD

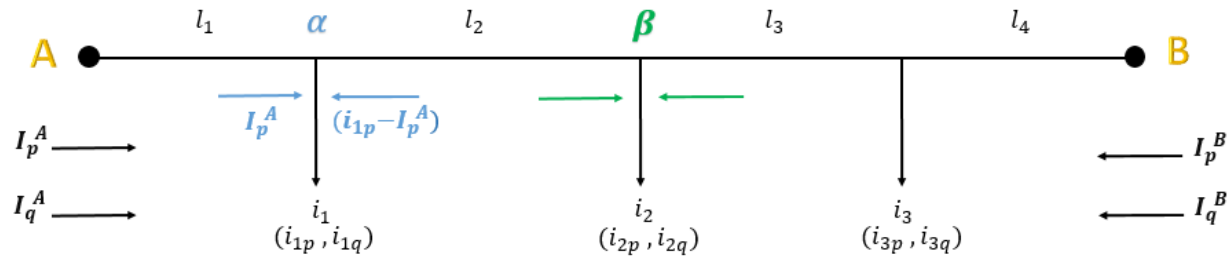


$$I_p^B = \frac{(i_{1p} \times l_1) + i_{2p} \times (l_1 + l_2) + i_{3p} \times (l_1 + l_2 + l_3)}{l_1 + l_2 + l_3 + l_4}$$

$$I_q^B = \frac{(i_{1q} \times l_1) + i_{2q} \times (l_1 + l_2) + i_{3q} \times (l_1 + l_2 + l_3)}{l_1 + l_2 + l_3 + l_4}$$



$$I_p^A = (i_{1p} + i_{2p} + i_{3p}) - I_p^B$$
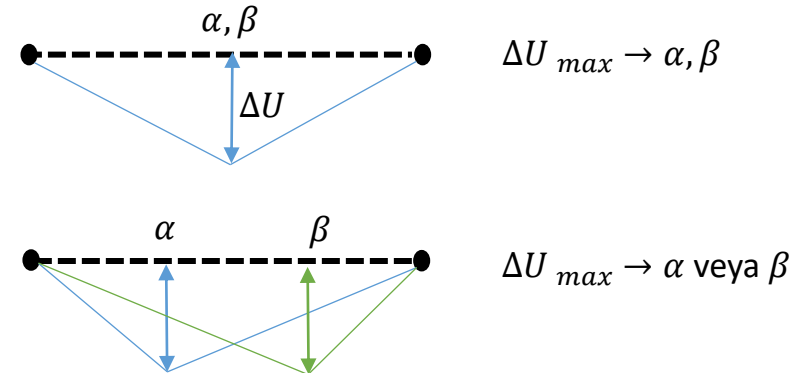
$$I_q^A = (i_{1q} + i_{2q} + i_{3q}) - I_q^B$$



α : The node where the direction of active current flow changes
 β : The node where the direction of reactive current flow changes

Örnek

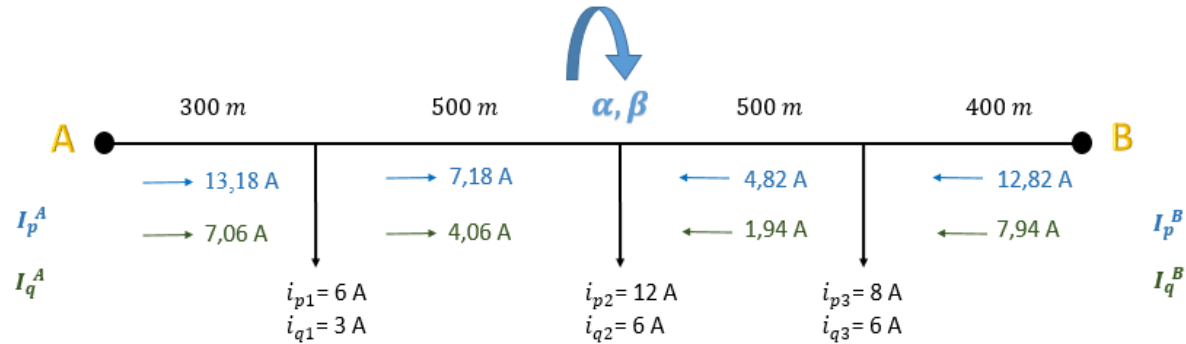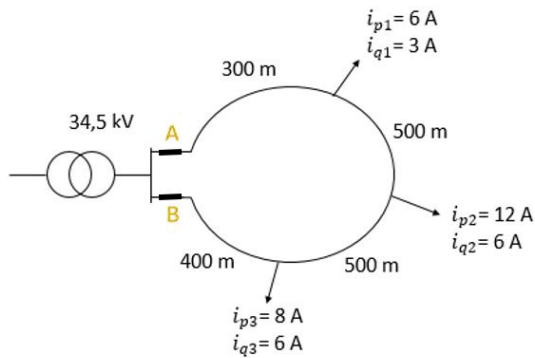

a) Calculate maximum VD.

b) Calculate total losses.

$$K = 44,4 \text{ m}/\Omega \text{mm}^2$$

$$q = 35 \text{ mm}^2$$


$$L = 0,51 \text{ mH/km}$$

$$I_p^B = \frac{\sum_{i=1}^L L_i \times i_{pi}}{L} = \frac{(300 \times 6) + (800 \times 12) + (1300 \times 8)}{1700} = 12,82 \text{ A}$$

$$I_p^A = (6 + 12 + 8) - 12,82 = 13,18 \text{ A}$$

$$I_q^B = \frac{\sum_{i=1}^L L_i \times i_{qi}}{L} = \frac{(300 \times 3) + (800 \times 6) + (1300 \times 6)}{1700} = 7,94 \text{ A}$$
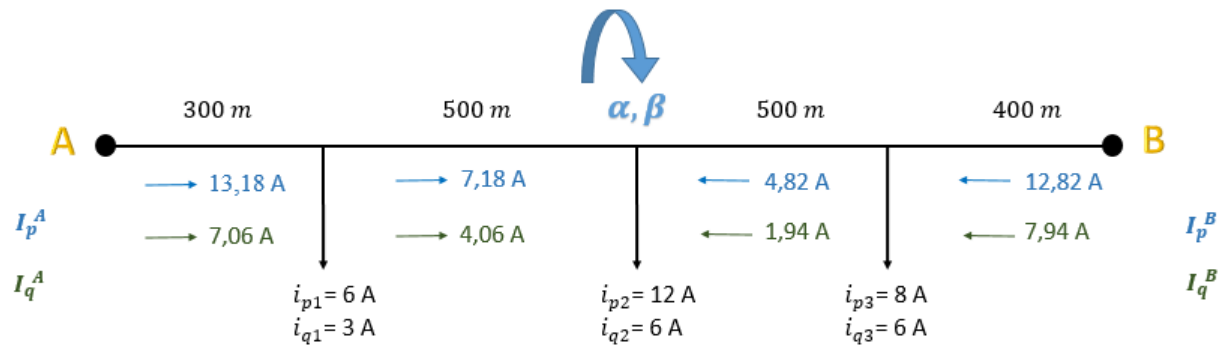
$$I_q^A = (3 + 6 + 6) - 7,94 = 7,06 \text{ A}$$



$$X' = \omega \times L = 2 \times \pi \times f \times L = 2 \times \pi \times 50 \times \frac{0,51}{1000} = 0,16 \frac{\Omega}{km}$$

$$X = X' \times l$$

$$\Delta U = R I_p + X I_q = \frac{1}{44,4 \times 35} (300 \times 13,18 + 500 \times 7,18) + (0,16 \times 0,3 \times 7,06) + (0,16 \times 0,5 \times 4,06) = 5,52 V$$

$$\delta U = X I_p - R I_q = (0,16 \times 0,3 \times 13,18) + (0,16 \times 0,5 \times 7,18) - \frac{1}{K.q} (300 \times 7,06 + 500 \times 4,06) = -1,46 V$$

$$\sqrt{\Delta U^2 + \delta U^2} = 5,7 V \text{ (VDmax)}$$

$$P_k = 3 R I^2 = 3 \frac{l}{K.q} (i_p^2 + i_q^2) = 397 W \quad (\text{total losses})$$

REFERENCES

- T. Gönen “Electric Power Distribution System Engineering”
- Venkata, Lecture Notes
- Electric Power Distribution Handbook